

FIND  $P_{avg}$  delivered  
by the current source.

$$Z_{cap} = \frac{1}{j\omega C} = -1250j$$

$$Z_{ind} = j\omega L = 500j \Omega$$

$$Z_{eq} = 500 + \left[ \frac{(-1250j)(1K + 500j)}{-1250j + 500j + 1000} \right]$$

$$= 500 + (1000 - 500j)$$

$$= 1500 - 500j \Omega$$

$$= 1581.14 \angle -18.435^\circ$$

$$V_z = I_z Z = 4 \angle 0 (1581.14 \angle -18.435^\circ) \text{ mV}$$

$$= 6.325 \angle -18.435^\circ \text{ V}$$

$$P_{load} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$


$$= \frac{(6.325)(4)}{2} \cos(-18.435 - 0)$$

$$= 12 \text{ mW}$$

Therefore the current source generates 12 mW of power on

$$P_{source} = -12 \text{ mW}$$

10.6

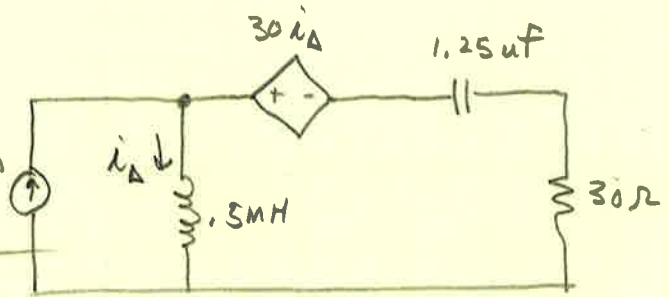N/ISSON 10 <sup>th</sup>FIND  $P_{avg}$  dissipatedin the  $30\Omega$  resistor.  $6\cos 20,000t$  A

$$\sum i_{in} = \sum i_{out}$$

$$\sum i_{in} = \sum i_{out}$$

$$6 \angle 0^\circ = \frac{V_A}{10j} + \frac{V_A - 30i_D}{30 - 40j}$$

$$i_D = \frac{V_A}{10j}$$


$$6 \angle 0^\circ = V_A \left[ \frac{1}{10 \angle 90^\circ} + \frac{1}{30 - 40j} - \frac{30}{10j(30 - 40j)} \right]$$

$$V_A = 100 \angle 126.87^\circ \text{ V}$$

$$i_D = 10 \angle 36.87^\circ \text{ A}$$

$$i_1 = i - i_D = 6 \angle 0^\circ - 10 \angle 36.87^\circ = 6.32 \angle -108.43^\circ \text{ A}$$
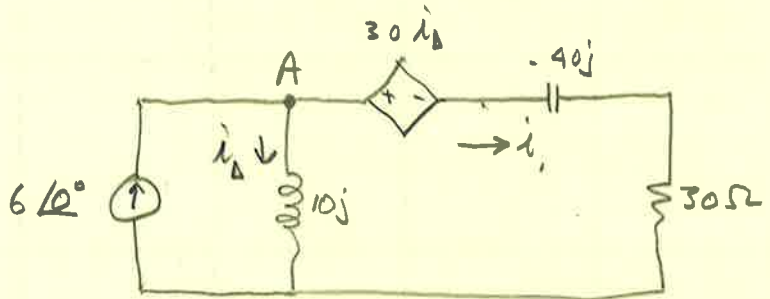
$$P_{avg} = \frac{1}{2} I^2 R = \frac{1}{2} (6.32)^2 30 = \boxed{600 \text{ W}}$$




a) Find the RMS value of the waveform shown.

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

$$= \left[ \frac{1}{100 \mu s} \left( \int_0^{25 \mu s} (10)^2 dt + \int_{25 \mu s}^{50 \mu s} (20)^2 dt + \int_{50 \mu s}^{75 \mu s} (-20)^2 dt + \int_{75 \mu s}^{100 \mu s} (-10)^2 dt \right) \right]^{1/2}$$

$$= \left[ \frac{1}{100 \mu s} \left[ 100(25 \mu s)(2) + 400(25 \mu s)(2) \right] \right]^{1/2}$$

$$V_{RMS} = 15.81 V$$

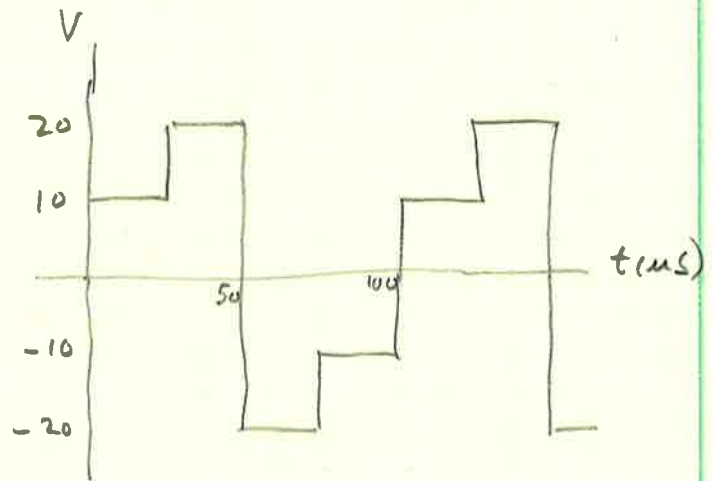

b) If this value is applied to a  $4 \Omega$  resistor, what is the average power dissipated?

$$P = \frac{V^2}{R} = 62.5 W$$


L1: absorbs 10kW  
delivers 4KVAR

L2:  $Z = 60 + j80$

$$V_L = 1000\sqrt{2} \cos(100\pi t) \text{ V}$$


$$= 1000 \cos(100\pi t) \text{ V}_{RMS}$$

a) Find  $V_g$

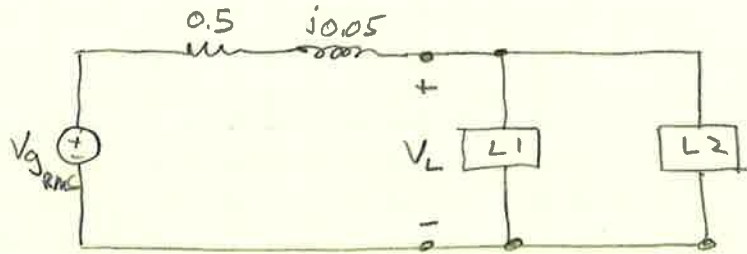

$$S_1 = 10,000 - j4000$$
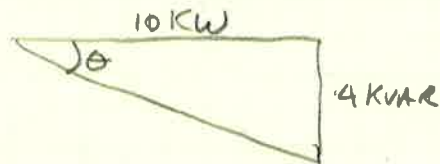
$$= 10.77 \text{ k} \angle -21.8^\circ \text{ VA}$$



$$V_{I_1}^* = S_1 = 10.77 \text{ k} \angle -21.8^\circ \text{ VA}$$

$$I_1^* = \frac{S_1}{V} = 10.77 \angle -21.8^\circ$$

$$= 10 - 4j \text{ A}$$

$$I_{L1} = 10 + 4j \text{ A}$$

$$I_{L2} = \frac{V_{L2}}{Z_{L2}} = \frac{1000 \angle 0^\circ}{60 + j80} = 10 \angle -53.13^\circ = 6 - 8j \text{ A}$$

$$I_{\text{total}} = I_{L1} + I_{L2} = 16 - 4j \text{ A} = 16.49 \angle -14.04^\circ$$

$$V_g = V_L + I_{\text{TOT}} (0.5 + j0.05)$$

$$= 1000 \angle 0^\circ + (16.49) \angle -14.04^\circ (0.5025 \angle 5.71^\circ)$$

$$= 1000 + 8.286 \angle -8.33^\circ = 1000 + 8.12 - 1.2j$$

$$V_g = 1008.12 - 1.2j = 1008.2 \angle -0.0682^\circ \text{ V}_{RMS}$$


b)  $T = \frac{L}{f} = \left( \frac{100\pi}{2\pi} \right)^{-1} = \frac{L}{50} = 20 \text{ ms}$

$$\frac{-0.0682^\circ}{360^\circ} = \frac{t}{20 \text{ ms}} \Rightarrow t = -3.79 \mu\text{s}$$

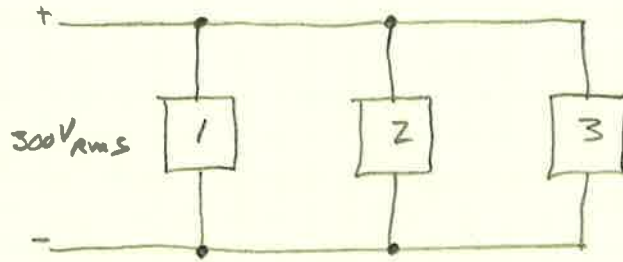c) Does the load voltage lead or lag the source voltage?

$$V_L \text{ leads } V_g \text{ by } 0.0682^\circ$$

- Load 1: absorbs 3 kW  
PF = 1
- Load 2: absorbs 5 kVA  
PF = 0.8 leading
- Load 3: absorbs 5 kW  
delivers 6 kvars




a) Find  $Z$  of combined load

$$S_1 = 3 + 0j \text{ kVA}$$

$$S_2 = 4 - 3j \text{ kVA}$$

$$S_3 = 5 - j6 \text{ kVA}$$

$S_2$ :

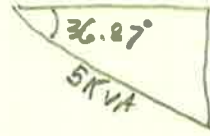

$$S_{\text{TOTAL}} = 12 - 9j \text{ kVA} = VI^*$$

$$I^* = 40 - 30j$$

$$I = 40 + 30j = 50 \angle 36.87^\circ \text{ A}$$

$$Z = \frac{V}{I} = \boxed{6 \angle -36.87^\circ \Omega = 4.8 - j3.6 \Omega = Z}$$


b) Find power factor of combined load

$$PF = \cos^{-1} \angle Z$$

$$\boxed{PF = 0.8 \text{ leading}}$$

FIND  $P_{AVG}$ ,  $P_{REAC}$ ,  $P_{APP}$  absorbed by the load

Do source transform

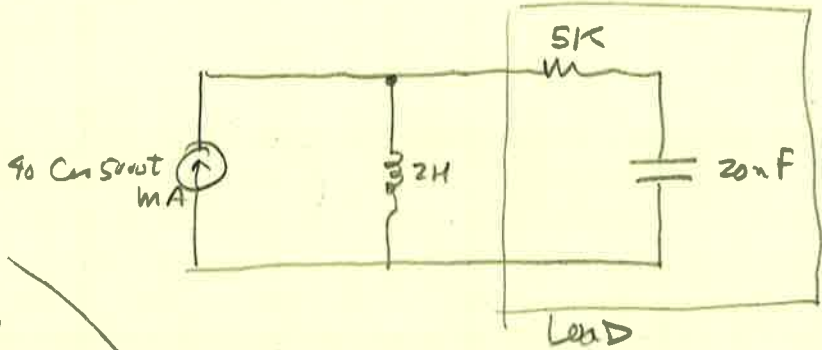

$$V = I Z$$


$$= 40 \angle 0 (10,000 \angle 90^\circ) \text{ mV}$$

$$= 400 \angle 90^\circ \text{ V}$$

$$i = \frac{V}{Z}$$

$$= \frac{400 \angle 90^\circ}{5 \text{ k}}$$

$$= 0.08 \text{ A} \angle 90^\circ$$

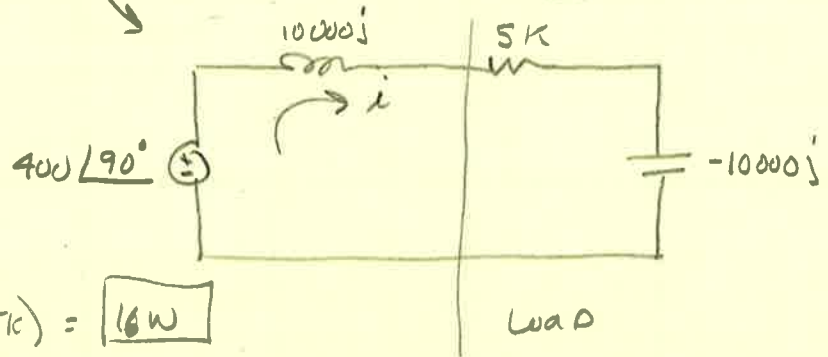

$$P_{AVG} = \frac{1}{2} I^2 R = \frac{1}{2} (0.08)^2 (5 \text{ k}) = \boxed{16 \text{ W}}$$

$$V_L = \frac{400 \angle 90^\circ (5 \text{ k} - 10,000j)}{5 \text{ k}} = 894.422 \angle 26.565^\circ$$

$$PF_{load} = \cos(\theta_V - \theta_i) = \cos(26.565^\circ - 90^\circ) = .4472$$

(also  $PF_{load} = \cos \angle Z$ )

$$= \cos^{-1} \left( \frac{5000}{5000} \right)$$

$$= -63.435^\circ$$

$$\cos 63.4349 = \frac{16}{P_{APP}}$$

$$\boxed{P_{APP} = 35.78 \text{ VA}}$$

$$\sin 63.4349^\circ = \frac{VAR}{P_{APP}}$$

$$\boxed{VAR = \text{reactive power} = -32 \text{ VAR}}$$

