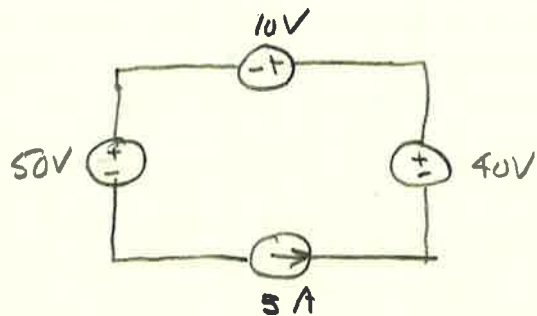


Is the interconnected circuit valid?

yes




Find total Power developed in the circuit.

5A flows through every element.

50V	:	$P = (50)(5) = 250\text{W}$
10V	:	$P = (10)(5) = 50\text{W}$
40V	:	$P = (40)(-5) = -200\text{W}$
5A	:	$P = (50+10-40)(-5) = -100\text{W}$

total = 0 ✓

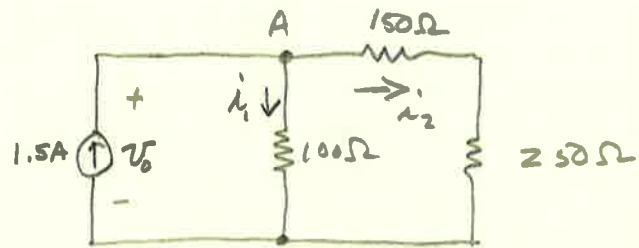

a) Find $i_1 + i_2$

KCL at node A: $1.5 = i_1 + i_2$

KVL around right loop: $150i_2 + 250i_2 = 100i_1$

$$\begin{aligned} i_1 + i_2 &= 1.5 \\ 100i_1 - 400i_2 &= 0 \end{aligned}$$

Solving, $\boxed{\begin{aligned} i_1 &= 1.2 \text{ A} \\ i_2 &= 0.3 \text{ A} \end{aligned}}$

b) Find V_0

$$V_0 = i_1(100) = \boxed{120 \text{ V} = V_0}$$

c) Show $P_{\text{gen}} = P_{\text{abs}}$

1.5A source: $P = -1.5(120) = -180 \text{ W}$


100Ω resistor: $P = i^2 R = (1.2)^2 100 = 144 \text{ W}$

150Ω resistor: $P = i^2 R = (0.3)^2 150 = 13.5 \text{ W}$

250Ω resistor: $P = i^2 R = (0.3)^2 250 = 22.5 \text{ W}$

$$\Sigma P = 0 \quad \checkmark$$

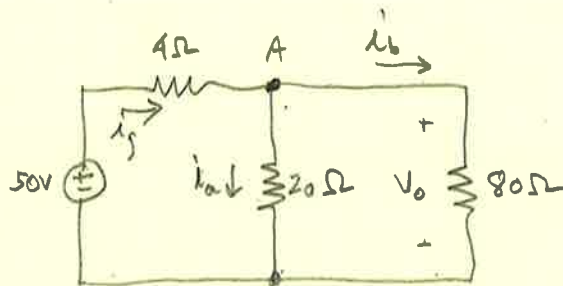FIND i_a , i_b , v_o + the power of each element.



applying KCL @ node A:

$$i_g = i_a + i_b$$

Since v_o is common to the $20\Omega + 80\Omega$ resistors,

$$i_a 20 = i_b 80 \Rightarrow i_a = 4 i_b$$

writing a KVL around the outer loop:

$$\sum V_{loop} = 0$$

$$-50 + i_g(4) + i_b(80) = 0$$

$$\text{but } i_g = i_a + i_b \text{ and } i_a = 4 i_b \text{ so}$$

$$-50 + 4(4 i_b + i_b) + i_b(80) = 0$$

$$i_b = \frac{50}{100} = \underline{\underline{0.5 A}}$$

$$i_a = 4 i_b = \underline{\underline{2.0 A}}$$

$$i_g = i_a + i_b = \underline{\underline{2.5 A}}$$

$$v_o = i_b(80) = \underline{\underline{40.0 V}}$$

$$P_{4\Omega} = i v = i^2 R = \frac{v^2}{R} = 2.5^2(4) = \underline{\underline{25 W}} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \text{dissipated}$$

$$P_{20\Omega} = i_a v_o = \underline{\underline{80 W}}$$


$$P_{80\Omega} = i_b v_o = \underline{\underline{20 W}}$$

$$P_{50V} = -i_g(50) = \underline{\underline{-125 W}} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{generated}$$

$$\sum \text{power} = \underline{\underline{0}}$$

$$i_0 = 1A$$

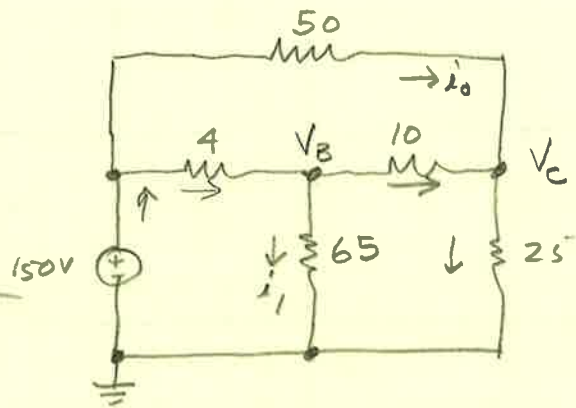- a) Find i_1
 b) Find Power for all R 's
 3) verify $P_{dev} = P_{abs}$



$$a) \quad V_C = 150 - 50(1) = 100V$$

$$i_{25} = V_C / 25 = 4A$$

$$i_{10} = i_{25} - i_0 = 3A$$

$$V_B = V_C + i_{10}(10) = 100 + 30 = 130V$$

$$i_1 = \frac{150 - V_B}{4} = 5A$$

$$i_{65} = \frac{V_B}{65} = \boxed{2A = i_1}$$

$$b) \quad P_{50} = i^2 R = (1)^2 50 = 50W$$

$$P_4 = i^2 R = (5)^2 4 = 100W$$

$$P_{65} = i^2 R = (2)^2 65 = 260W$$

$$P_{10} = i^2 R = (3)^2 10 = 90W$$

$$P_{25} = i^2 R = (4)^2 25 = 400W$$

$$P_{absorbed} = 900W$$

$$c) \quad i_{150} = i_{50} + i_1 = 1 + 5 = 6A$$

$$P_{150} = (-6)(150) = 900W \text{ delivered}$$