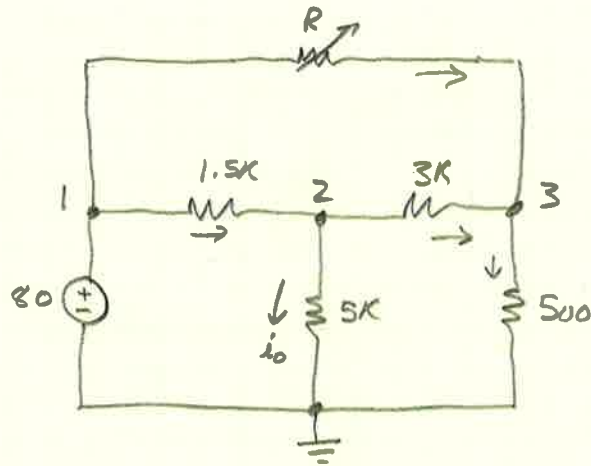


The Variable Resistor  $R$  is adjusted until  $i_o = 10 \text{ mA}$ . Find  $R$



1) assign Reference (at Bottom)

use Ohm's + Kirchoff's laws.

$$V_1 = 80 \text{ V}$$

$$V_2 = (10 \text{ mA})(5 \text{ k}) = 50 \text{ V}$$

$$i_{12} = \frac{80 - 50}{1.5 \text{ k}} = 20 \text{ mA}$$

$$i_{23} = i_{12} - i_o = 10 \text{ mA}$$

$$V_3 = V_2 - i_{23}(3 \text{ k}) = 50 - (10 \text{ mA})(3 \text{ k}) = 20 \text{ V}$$

$$i_{500} = \frac{20}{500} = 40 \text{ mA}$$


$$V_R = 80 - V_3 = 60 \text{ V}$$

$$\text{@ Node 3; } i_r = i_{500} - i_{3 \text{ k}} = 40 \text{ mA} - 10 \text{ mA} = 30 \text{ mA}$$

$$R = \frac{V}{I} = \frac{60}{30 \text{ mA}} = \boxed{2 \text{ k}\Omega}$$

$$i_0 = 1A$$

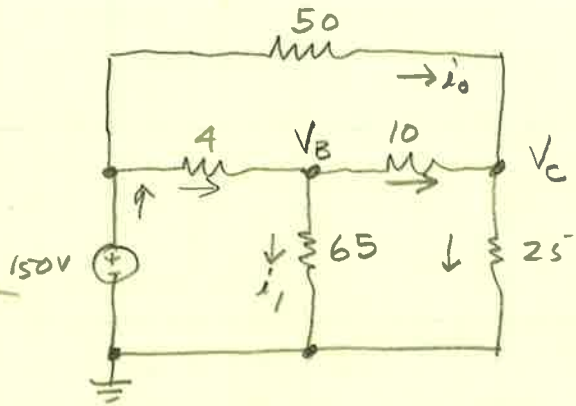- a) Find  $i_0$   
 b) Find Power for all  $R$ 's  
 3) verify  $P_{dev} = P_{abs}$



$$a) V_C = 150 - 50(1) = 100V$$

$$i_{25} = V_C / 25 = 4A$$

$$i_{10} = i_{25} - i_0 = 3A$$

$$V_B = V_C + i_{10}(10) = 100 + 30 = 130V$$

$$i_4 = \frac{150 - V_B}{4} = 5A$$

$$i_{65} = \frac{V_B}{65} = \boxed{2A = i_1}$$

$$b) P_{50} = i^2 R = (1)^2 50 = 50W$$

$$P_4 = i^2 R = (5)^2 4 = 100W$$

$$P_{65} = i^2 R = (2)^2 65 = 260W$$

$$P_{10} = i^2 R = (3)^2 10 = 90W$$

$$P_{25} = i^2 R = (4)^2 25 = 400W$$

$$P_{absorbed} = 900W$$

$$c) i_{150} = i_{50} + i_4 = 1 + 5 = 6A$$

$$P_{150} = (-6)(150) = 900W \text{ DELIVERED} \quad \checkmark$$