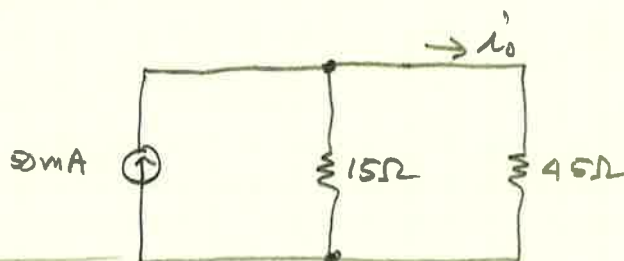


$$\% \text{ error} = \left(\frac{\text{measured value}}{\text{true value}} - 1 \right) \times 100$$

ammeter resistance = 0.1Ω

an ammeter is used
to measure i_o .
Find % error.



- Find true value of i_o
using current divider,

$$i_o = \frac{50 \text{ mA} (15)}{15 + 45} = 12.5 \text{ mA}$$

- Find measured value


$$i_o = \frac{50 \text{ mA} (15)}{15 + 45 + 0.1} = 12.4792 \text{ mA}$$

$$\% \text{ error} = \left(\frac{12.4792}{12.5} - 1 \right) \times 100 = \boxed{-0.166 \%}$$

The Bridge circuit is balanced ($i = 0$) when
 $R_1 = 500\Omega$, $R_2 = 1000\Omega$, $R_3 = 750\Omega$

$$V = 24V$$

$$24V$$

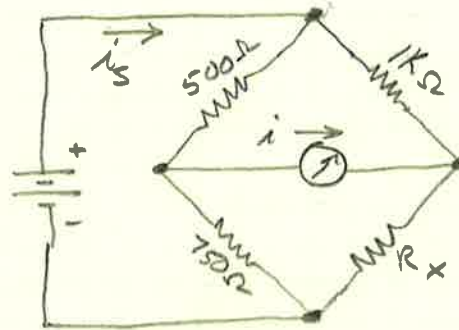

a) find R_x

$$\frac{500}{750} = \frac{1k}{R_x}$$


$$R_x = 1.5k\Omega$$

b) find i_s

First, find R_{eq}

$$R_{eq} = \frac{(1250)(2.5k)}{1250 + 2.5k} = 833\Omega$$
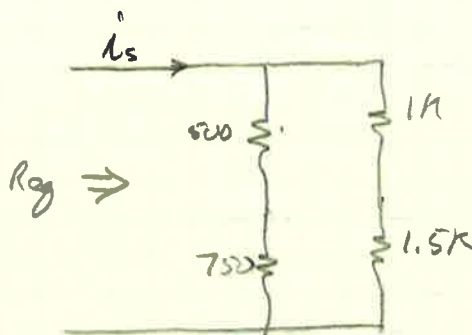
$$i_s = \frac{24}{833} = 28.8\text{ mA} = i_s$$




c) which resistor absorbs most power?
 d) " " " least " ?

using current divider,

$$i_1 = \frac{(28.8\text{ mA})(2.5k)}{1.25k + 2.5k} = 19.2\text{ mA}$$
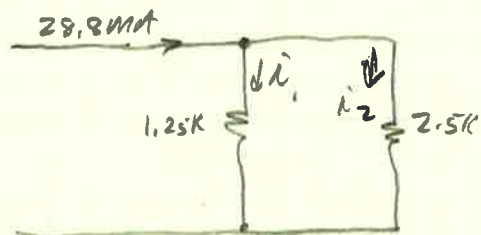
$$i_2 = \frac{(28.8\text{ mA})(1.25k)}{(1.25k + 2.5k)} = 9.6\text{ mA}$$



$$P_{500} = i^2 R = 184\text{ mW}$$

$$P_{750} = i^2 R = 276\text{ mW} \leftarrow \text{MOST}$$


$$P_{1k} = i^2 R = 92.2\text{ mW} \leftarrow \text{Least}$$

$$P_{1.5k} = i^2 R = 230\text{ mW}$$

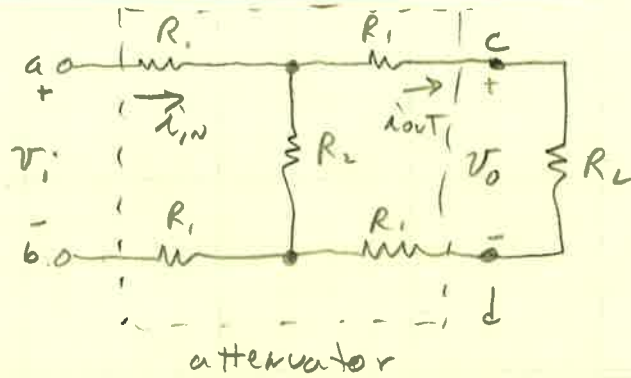a) Show that if $R_{ab} = R_L$ then

$$R_L^2 = 4R_1(R_1 + R_2) \text{ and}$$

$$\frac{V_0}{V_i} = \frac{R_2}{2R_1 + R_2 + R_L}$$



$$R_{ab} = 2R_1 + R_2 \parallel (R_1 + R_2)$$

$$= 2R_1 + \frac{R_2(R_1 + R_2)}{2R_1 + R_2 + R_L}$$

But $R_{ab} = R_L$ so $R_L = 2R_1 + \frac{R_2(2R_1 + R_2)}{2R_1 + R_2 + R_L}$

$$R_L(2R_1 + R_2 + R_L) = 2R_1(2R_1 + R_2 + R_L) + R_2(2R_1 + R_2)$$

$$R_L^2 = 4R_1^2 + 2R_1R_2 + 2R_1R_L + 2R_1R_2 + R_2R_L - 2R_1R_L - R_2R_L$$

$$= 4R_1^2 + 4R_1R_2$$

$$R_L^2 = 4R_1(R_1 + R_2)$$

when $R_{ab} = R_L$, $i_{in} = \frac{V_i}{R_L}$

using a current divider, $i_{out} = \frac{i_{in}(R_2)}{R_2 + 2R_1 + R_L}$

$$V_0 = i_{out}R_L = \frac{V_i(R_2)(R_L)}{R_L(R_2 + 2R_1 + R_L)}$$

$$\text{or } \frac{V_0}{V_i} = \frac{R_2}{2R_1 + R_2 + R_L}$$

b) Select R_1 & R_2 so $R_{ab} = R_L = 300 \Omega$ and $\frac{V_0}{V_i} = 0.5$

$$0.5 = \frac{R_2}{2R_1 + R_2 + 300}$$

$$300^2 = 4R_1(R_1 + R_2)$$

Solving these 2 equations;

$$\begin{cases} R_1 = 50 \Omega \\ R_2 = 400 \Omega \end{cases}$$


a) FIND V_0

- assume reference
at bottom of circuit

using voltage divider,

$$V_0 = \frac{160(R_2)}{R_1 + R_2}$$

$$\boxed{V_0 = 66V}$$

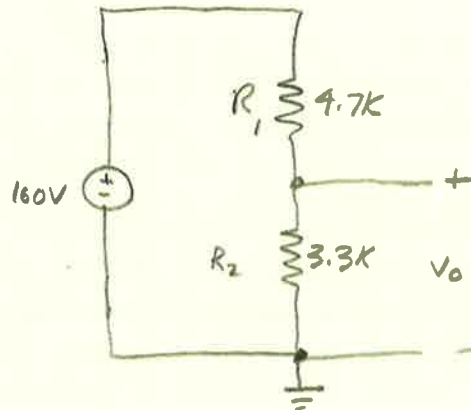

b) $P_{R_1} = \frac{V^2}{R} = \frac{(160-66)^2}{4.7K} = \boxed{1.88W}$

$$P_{R_2} = \frac{(66)^2}{3.3K} = \boxed{1.32W}$$

c) assume only .5W resistor available + V_0 is the same as part a. find the smallest value of R_1 + R_2

For R_2 , $P_{R_2} = \frac{V^2}{R_2} \Rightarrow 0.5 = \frac{(66)^2}{R_2} \Rightarrow \boxed{R_2 = 8.71K\Omega}$

For R_1 , $P_{R_1} = \frac{(160-66)^2}{R_1} \Rightarrow 0.5 = \frac{(94)^2}{R_1} \Rightarrow \boxed{R_1 = 17.67K\Omega}$


a) find v_x

For left branch:

$$V_{x+} = \frac{18(6k)}{6k+2k} = 13.5V$$

$$V_{x-} = \frac{18(3k)}{9k+3k} = 4.5V$$

$$v_x = V_{x+} - V_{x-} = \boxed{9.0V}$$

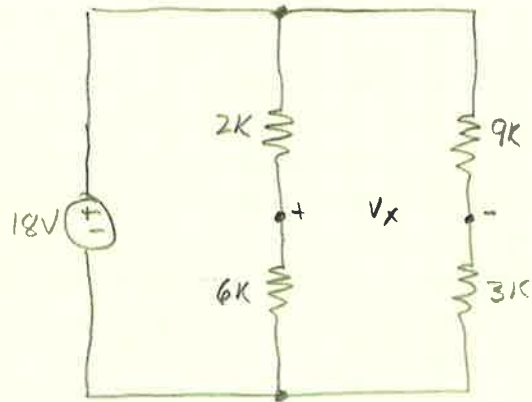


b) Replace the 18V source with a general source V_s .
Find v_x in terms of V_s .

$$V_{x+} = \frac{V_s(6k)}{6k+2k} = \frac{3}{4} V_s$$

$$V_{x-} = \frac{V_s(3k)}{9k+3k} = \frac{1}{4} V_s$$

$$v_x = V_{x+} - V_{x-} = \boxed{\frac{1}{2} V_s}$$

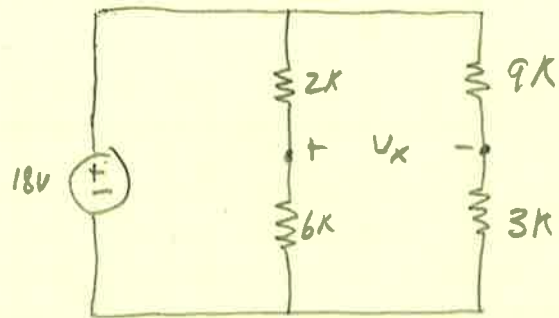- a) Find V_x
 b) Replace the 18V source with V_s . Find V_x as a function of V_s .



a) using a voltage divider,

$$V_{x+} = \frac{18(6k)}{2k+6k} = 13.5V$$

$$V_{x-} = \frac{18(3k)}{9k+3k} = 4.5V$$

$$V_x = V_{x+} - V_{x-} = 9V$$

b) $V_{x+} = \frac{V_s(6k)}{2k+6k} = 0.75V_s$

$$V_{x-} = \frac{V_s(3k)}{9k+3k} = 0.25V_s$$

$$V_x = V_{x+} - V_{x-} = 0.5V_s$$