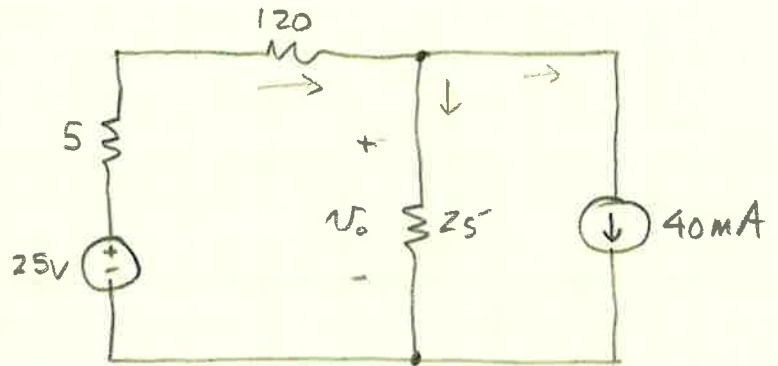


FIND V_0 using
the node-voltage
method.




NOTE: $\sum i_{in} = \sum i_{out}$

$$\frac{25 - V_0}{125} = \frac{V_0}{25} + 40 \text{ mA}$$

$$V_0 = 3.33 \text{ V}$$

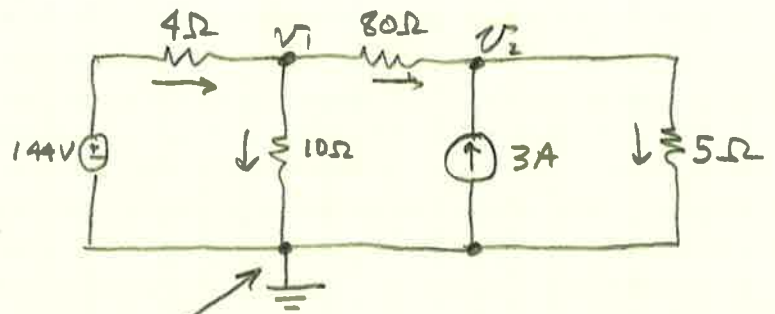use the node-voltage method to find v_1 + v_2



1. assign reference node
2. label currents
3. solve

@ node v_1 : $\sum i_{in} = \sum i_{out}$

$$\frac{144 - v_1}{4} = \frac{v_1 - v_2}{80} + \frac{v_1}{10} \quad (1)$$


@ node v_2 : $\sum i_{in} = \sum i_{out}$

$$\frac{v_1 - v_2}{80} + 3 = \frac{v_2}{5} \quad (2)$$

solving (1) + (2):

$v_1 = 100 \text{ V}$ $v_2 = 20 \text{ V}$
--

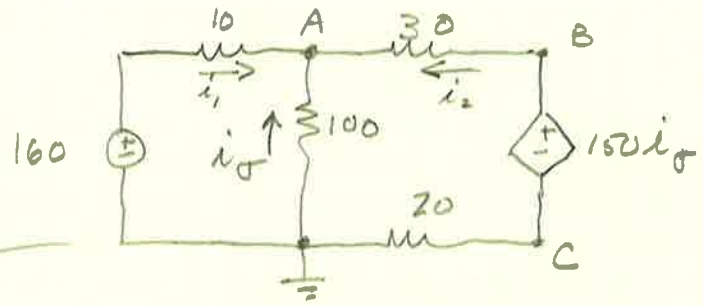use the node-voltage method + find P_{150i_σ} source.



$$V_C = -20i_2$$

$$V_B = -20i_2 + 150i_\sigma$$

node A: $i_1 + i_2 + i_\sigma = 0$

$$\frac{160 - V_A}{10} + \frac{(-20i_2 + 150i_\sigma) - V_A}{30} + \frac{(0 - V_A)}{100} = 0$$

$$i_\sigma = \frac{-V_A}{100}$$

$$i_2 = \frac{V_B - V_A}{30} = \frac{-20i_2 + 150i_\sigma - V_A}{30} \Rightarrow i_2 = 3i_\sigma - \frac{V_A}{50}$$

Substitution + solving:

$$i_\sigma = -1A$$

$$i_2 = -5A$$

$$V_A = 100V$$


So $i_\sigma + i_2$ are actually going the other way.

$$P_{150i_\sigma} = iV = i_2(150i_\sigma) = 5(150(-1)) = \boxed{-750W}$$

The dependent source is delivering Power to the circuit.

a) Find Power developed using node voltage method

b) Find power absorbed

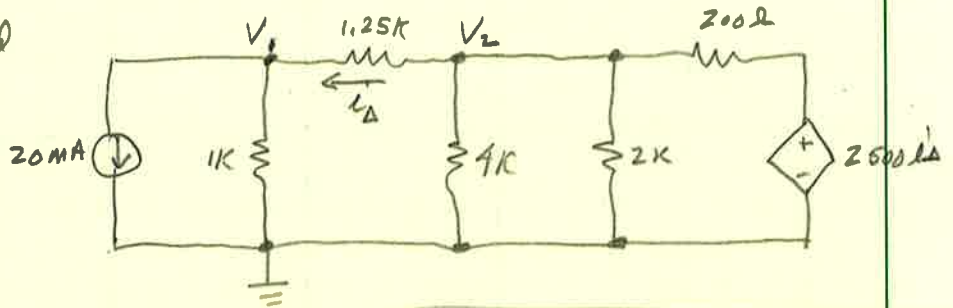

assign all currents positive down and to the left.

$$\text{node } V_1: \frac{V_2 - V_1}{1.25k} = \frac{V_1}{1k} + 20\text{mA}$$

$$\text{node } V_2: \frac{2500 i_D - V_2}{200} = \frac{V_2}{2k} + \frac{V_2}{4k} + \frac{V_2 - V_1}{1.25k}$$

$$i_D = \frac{V_2 - V_1}{1.25k}$$

$$\text{Solving: } \begin{aligned} V_1 &= 60\text{V} \\ V_2 &= 160\text{V} \\ i_D &= 80\text{mA} \end{aligned}$$

Find P_{dev} .

$$P_{20\text{mA}} = 60(0.02) = 1.2\text{W (absorbed)}$$

$$V_{0s} = 2500 i_D = 200$$

$$i_{ds} = \frac{200 - 160}{200} = 0.2\text{A} \uparrow$$

$$P_{dev} = (0.2)(200) = 40\text{W developed} \quad \text{or} \quad \boxed{-40\text{W}}$$