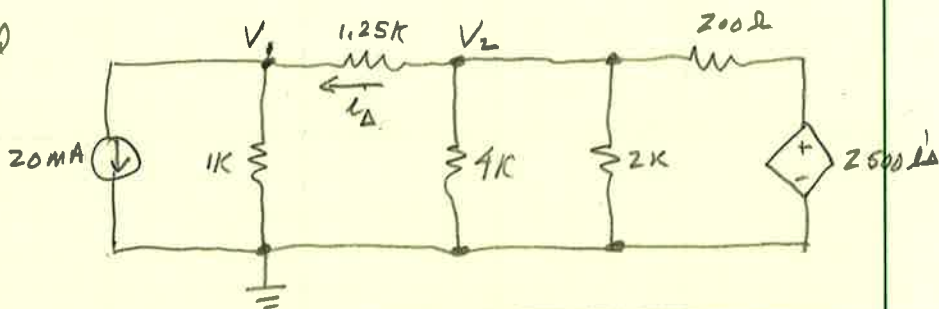


a) Find Power developed using node voltage method

b) Find power absorbed



assign all currents positive down and to the left.

node V_1 :
$$\frac{V_2 - V_1}{1.25k} = \frac{V_1}{1k} + 20mA$$

node V_2 :
$$\frac{2500 i_D - V_2}{200} = \frac{V_2}{2k} + \frac{V_2}{4k} + \frac{V_2 - V_1}{1.25k}$$

$$i_D = \frac{V_2 - V_1}{1.25k}$$

Solving :

$$\begin{aligned} V_1 &= 60V \\ V_2 &= 160V \\ i_D &= 80mA \end{aligned}$$

FIND P_{dev} .


$$P_{20mA} = 60(0.02) = 1.2W \text{ (absorbed)}$$

$$\begin{aligned} V_{0s} &= 2500 i_D = 200 \\ i_{ds} &= \frac{200 - 160}{200} = 0.2A \uparrow \end{aligned}$$

$$P_{dev} = (0.2)(200) = 40W \text{ developed}$$

$$\text{or } \boxed{-40W}$$

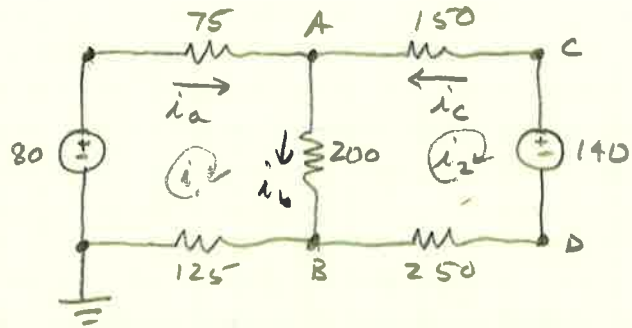a) use node-voltage method to find i_a, i_b, i_c



- 1) assign reference node
- 2) Super node problem

Node A : $i_a + i_c = i_b$

$$\frac{80 - V_A}{75} + \frac{V_C - V_A}{150} = \frac{V_A - V_B}{200} \quad (1)$$

Node V_B : $i_b = i_a + i_c$

$$\frac{V_A - V_B}{200} = \frac{V_B}{125} + \frac{V_B - V_D}{250} \quad (2)$$

Super node : $i_c = i_c$

$$\frac{V_B - V_D}{250} = \frac{V_C - V_A}{150} \quad (3)$$

Super node equation : $V_C = V_D + 140 \quad (4)$

Solving,	$V_A = 72.5V$
	$V_B = 12.5V$
	$V_C = 102.5V$
	$V_D = -37.5V$

b) Solve using mesh currents

mesh i_1 : $-80 + 75i_1 + 200(i_1 - i_2) + 125i_1 = 0$

$140 + 250(i_2) + 200(i_2 - i_1) + 150i_2 = 0$

$$400i_1 - 200i_2 = 80$$

$$-200i_1 + 600i_2 = -140$$

$i_1 = 0.1A$
$i_2 = -0.2A$

So, $V_A = 80 - 75i_1 = 72.5V$

$V_B = 0 + 125(i_1) = 12.5V$


$V_C = V_A + (-i_2)(150) = 102.5V$

$V_D = V_C - 140 = -37.5V$

also, $V_D = V_B + (i_2)(250) = -37.5V$

Find v_1 and v_2 using the mesh current method.

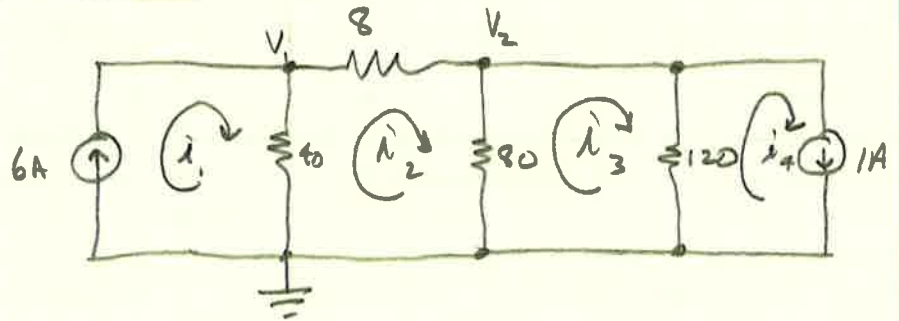- 1) Pick reference
- 2) assign mesh currents
- 3) solve



$$i_1 = 6A$$

$$\textcircled{1} \text{ mesh } i_2: 40(i_2 - i_1) + 8i_2 + 80(i_2 - i_3) = 0$$

$$\textcircled{2} \text{ mesh } i_3: 80(i_3 - i_2) + 120(i_3 - i_4) = 0$$

$$i_4 = 1A$$

$$\text{Solving } \textcircled{1} + \textcircled{2}: \begin{cases} i_2 = 3A \\ i_3 = 1.8A \end{cases}$$

$$v_1 = 40(i_1 - i_2) = 40(6 - 3) = \underline{\underline{120V}}$$

$$v_2 = v_1 - 8i_2 = \underline{\underline{96V}}$$

a) use mesh-current method to find P_{SA} .

mesh i_1 :

$$5 + 38(i_1 - i_3) + 30(i_1 + i_2) + 12i_1 = 0$$

mesh i_2 :

$$-67 + 6(i_2 + i_3) + 30(i_2 + i_1) + 40i_2 = 0$$

mesh i_3 :

$$i_3 = 5A$$

Solving:

$$\begin{aligned} i_1 &= 2.5A \\ i_2 &= -0.5A \\ i_3 &= 5A \end{aligned}$$

$$P_{SA} = VI = (V_{38} + V_6)5A = [38(i_1 - i_3) + 6(i_2 + i_3)]5 = (-122)(5) = -610W$$

5A source is delivering 610W

b) $P_{5V} = 5(2.5) = 12.5W$
 $P_{67V} = 0.5(67) = 33.5W$

Total power delivered = 610W

c) check that power delivered = power absorbed

$$P_{38} = (2.5)^2 38 = 237.5W$$


$$P_6 = (4.5)^2 6 = 121.5W$$


$$P_{30} = (2)^2 30 = 120W$$

$$P_{40} = (0.5)^2 40 = 10W$$

$$P_{12} = (2.5)^2 12 = 75W$$
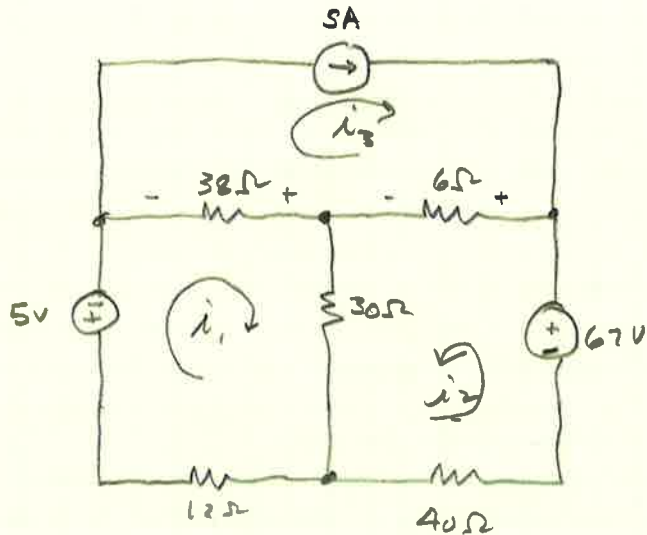
$$\begin{array}{r} +12.5W \\ +33.5W \\ \hline \boxed{610W} \end{array}$$



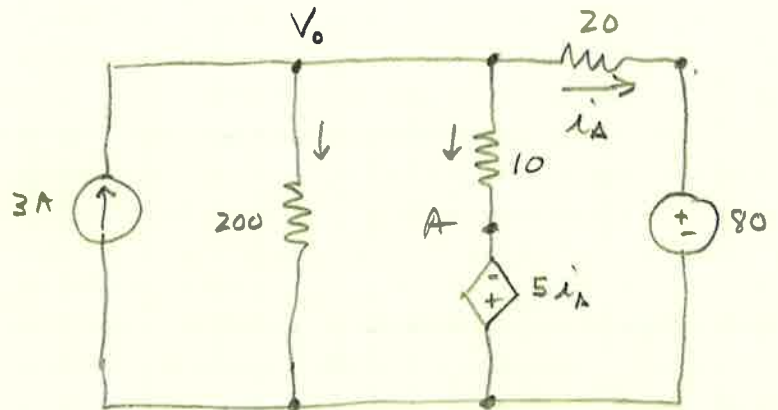

a) Find V_0

Choose the bottom node as a reference,
assign current direction.

node V_0 : $\sum i_{in} = \sum i_{out}$

$$3 = \frac{V_0 - 0}{200} + \frac{V_0 - (-5i_A)}{10} + \frac{V_0 - 80}{20} \quad (1)$$

dependent source: $i_A = \frac{V_0 - 80}{20}$

Solving, $\boxed{\begin{matrix} V_0 = 50V \\ i_A = -1.5A \end{matrix}}$

b) Find power absorbed by the dependent source

$$V_A = -5i_A = -5(-1.5) = 7.5V$$

$$i_{source} = \frac{V_A - 7.5}{10} = \frac{42.5}{10} = 4.25A$$

$$P_{source} = 7.5(4.25) = \boxed{31.9W = P_{source}}$$


c) Find power developed by the independent sources

$$P_{3A} = iV = -3(V_0) = -150W$$

$$P_{80V} = iV = i_A(80) = -(1.5)(80) = -120W$$

$$\boxed{\text{Total Power} = -270W \text{ delivered}}$$

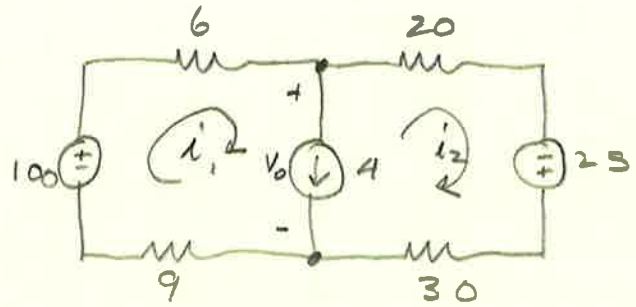use mesh currents
to find total power
dissipated



use outer loop:

$$-100 + 6i_1 + 20i_2 - 25 + 30i_2 + 9i_1 = 0$$

$$i_1 - i_2 = 4$$

$$15i_1 + 50i_2 = 125$$

$$i_1 - i_2 = 4$$

$$\Rightarrow \begin{cases} i_1 = 5A \\ i_2 = 1A \end{cases}$$


$$V_0 = 20i_2 - 25 + 30i_2 = 25V$$

$$\begin{aligned} P_{100V} &= -100i_1 = -500W && \text{generated} \\ P_{4A} &= 4(25) = 100W \\ P_{25V} &= -(1)(25) = -25W && \text{generated} \\ P_6 &= i_1^2 R = 150W \\ P_9 &= i_1^2 R = 225W \\ P_{20} &= i_2^2 R = 20W \\ P_{30} &= i_2^2 R = 30W \end{aligned}$$

$$\text{Power generated} = -25 - 500 = -525W$$

$$\text{Power absorbed} = 100 + 150 + 225 + 20 + 30 = 525W$$

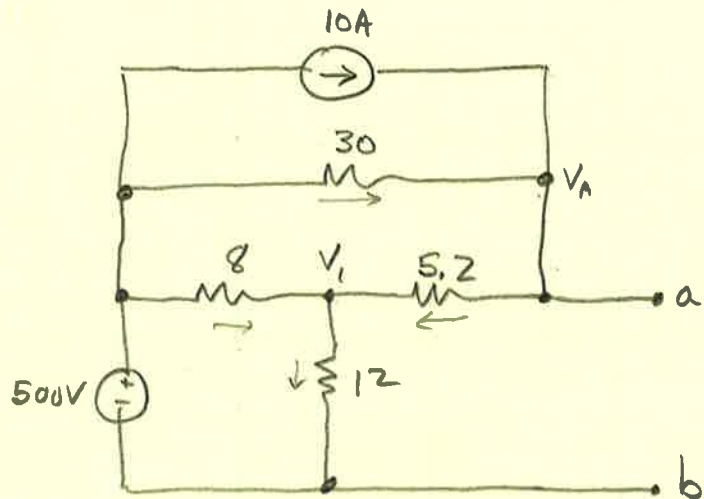
Find thevenin equivalent at terminals a-b.



Find R_{th} : $i \rightarrow$ open
 $v \rightarrow$ short

$$R_{th} = \left[(8 \parallel 12) + 5.2 \right] \parallel 30$$

$$= \boxed{7.5 \Omega}$$

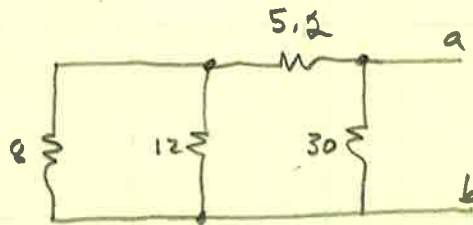

Find V_{th} :

node V_A : $\sum i_{in} = \sum i_{out}$

$$10 + \frac{500 - V_A}{30} = \frac{V_A - V_1}{5.2}$$


node V_1 : $\frac{500 - V_1}{8} + \frac{V_A - V_1}{5.2} = \frac{V_1}{12}$

$$\boxed{V_A = V_{th} = 425V}$$

$$V_1 = 360V$$

a) use node-voltage to find total power developed

b) find absorbed power.

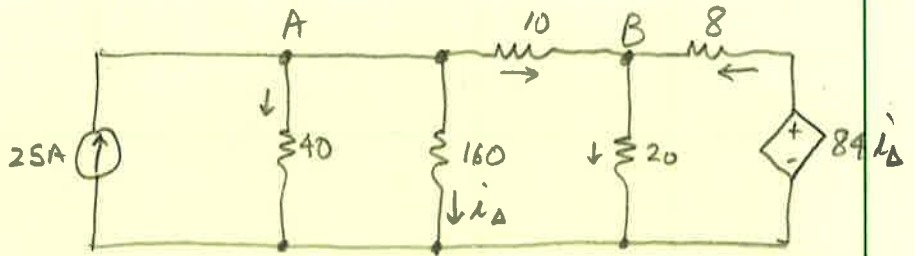

Node A: $\sum i_N = \sum i_{int}$

$$25 = \frac{V_A}{40} + \frac{V_A}{160} + \frac{V_A - V_B}{10} \Rightarrow 21V_A - 16V_B = 4000$$

Node B: $\frac{V_A - V_B}{10} + \frac{84i_D - V_B}{8} = \frac{V_B}{20} \Rightarrow 4V_A - 11V_B + 420i_D = 0$

Dependent Source: $i_D = \frac{V_A}{160} \Rightarrow V_A = 160i_D$

Solving:

$$\begin{aligned} V_A &= 352V \\ V_B &= 212V \\ i_D &= 2.2A \end{aligned}$$

$$\begin{aligned} V_{84i_D} &= 184.8V \\ i_{84i_D} &= -3.4A \end{aligned}$$

$$\begin{aligned} P_{25A} &= 25(352) = -8800W \text{ (generating)} \\ P_{84i_D} &= (184.8)(3.4) = 628.32W \text{ (absorbing)} \end{aligned}$$

$$P_{developed} = 8800W$$

$$P_{40\Omega} = \frac{352^2}{40} = 3097.6W$$

$$P_{160\Omega} = \frac{352^2}{160} = 774.4W$$

$$P_{10\Omega} = \frac{(352 - 212)^2}{10} = 1960W$$

$$P_{20\Omega} = \frac{(212)^2}{20} = 2247.2W$$

$$P_{8\Omega} = \frac{(184.8 - 212)^2}{8} = 92.48W$$


$$P_{abs} = 8800W = P_{gen}$$

a) Find V_o at node V_o :

$$\sum i_{in} = \sum i_{out}$$

$$\textcircled{1} \quad 3 = \frac{V_o - 0}{200} + \frac{V_o - (-5i_\Delta)}{10} + \frac{V_o - 80}{20}$$

$$\textcircled{2} \quad i_\Delta = \frac{V_o - 80}{20}$$

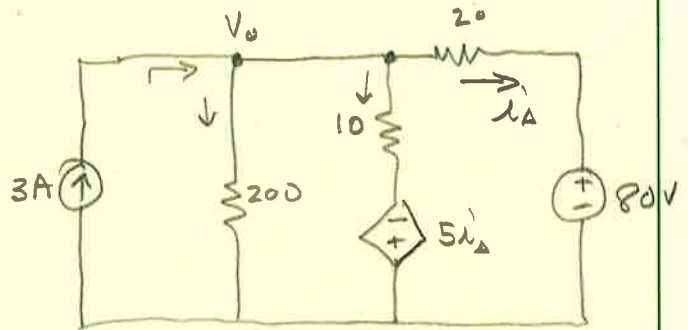Solving $\textcircled{1} + \textcircled{2}$,

$$V_o = 50V$$

$$i_\Delta = -1.5A$$

b) Find the power of the independent source

$$i_{5\Omega} = \frac{V_o + 5i_\Delta}{10} = 4.25A$$


$$V_{5\Omega} = 5i_\Delta = -7.5V$$

$$P = 31.875W \text{ dissipating}$$

c) Find power of independent sources

$$P_{3A} = (3)(V_o) = 150W \text{ generating}$$

$$P_{80V} = (80)(-1.5) = 120W \text{ generating}$$

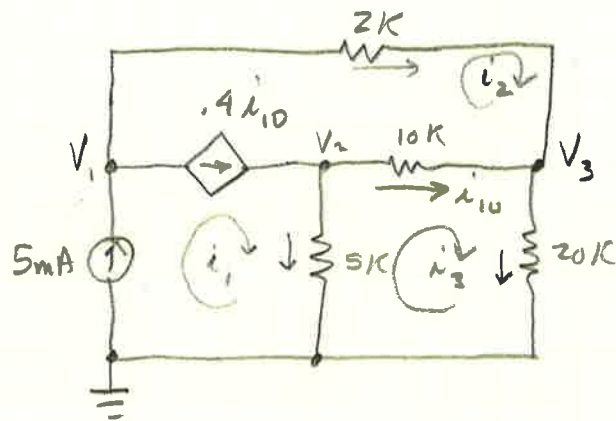Find i_{10} NODE ANALYSIS

$$\text{Node } V_1: 5\text{mA} = 0.4i_{10} + \frac{V_1 - V_3}{2\text{K}}$$

$$\text{Node } V_2: 0.4i_{10} = \frac{V_2}{5\text{K}} + \frac{V_2 - V_3}{10\text{K}}$$

$$\text{Node } V_3: \frac{V_1 - V_3}{2\text{K}} + \frac{V_2 - V_3}{10\text{K}} = \frac{V_3}{20\text{K}}$$

$$\text{Dependent eq: } i_{10} = \frac{V_2 - V_3}{10\text{K}}$$

$$\text{Solving: } \begin{aligned} V_1 &= 65.2\text{V} \\ V_2 &= 12\text{V} \\ V_3 &= 52\text{V} \end{aligned}$$

$$i_{10} = -4.0\text{mA}$$

MESH ANALYSIS

$$\text{Mesh } i_1: i_1 = 5\text{mA}$$

$$\text{Mesh } i_2: 0.4i_{10} = i_1 - i_2$$

$$\text{Mesh } i_3: 5\text{K}(i_3 - i_1) + 10\text{K}(i_3 - i_2) + 20\text{K}(i_3) = 0$$

$$i_{10} = i_3 - i_2$$

$$\text{Solving: } \begin{aligned} i_1 &= 5\text{mA} \\ i_2 &= 6.6\text{mA} \\ i_3 &= 2.6\text{mA} \end{aligned}$$

$$i_{10} = -4.0\text{mA}$$