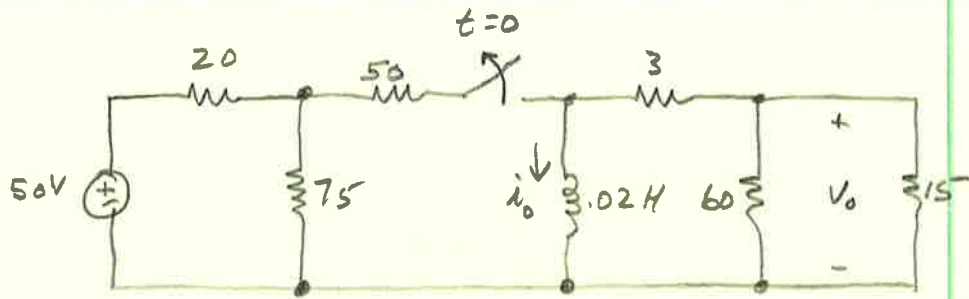


The switch has been closed for a long time. it is opened @ $t = 0$ sec.




a) find $i_o(t)$ for $t \geq 0$

First for $i_o(0)$, just before the switch opens. Replace the inductor with a wire. then:

No current flow to the right half of the circuit

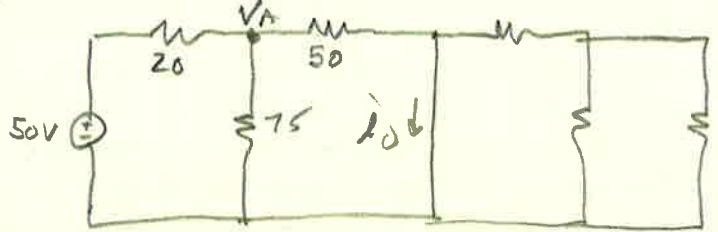
$$V_A = \frac{50(50 \parallel 75)}{60 \parallel 75 + 20} = 30V$$



$$i_o(0) = \frac{V_A}{50} = 0.6A$$

after the switch opens,
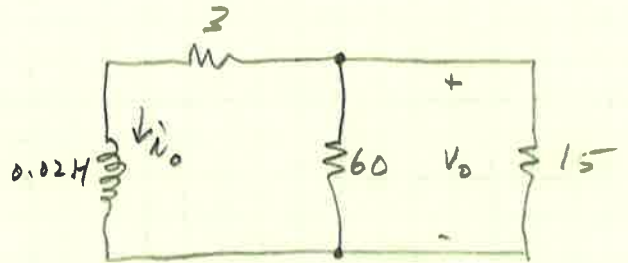
$$\tau = \frac{L}{R_{eq}} = \frac{0.02}{3 + 60 \parallel 15} = 1.333 \text{ ms}$$




$$i_L = I_0 e^{-\frac{t}{\tau}} = 0.6 e^{-750t} \text{ A for } t \geq 0 \text{ sec}$$

b) find $v_o(t)$ for $t \geq 0^+$

$$V_o = -i_o(60 \parallel 15) = -7.20 e^{-750t} \text{ V}$$

$$v = 160e^{-10t} \text{ V} \quad t \geq 0^+$$
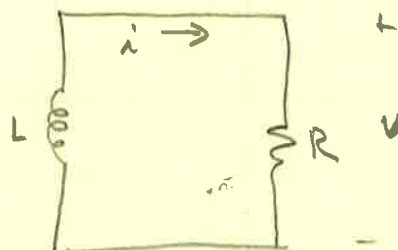
$$i = 6.4e^{-10t} \text{ A} \quad t \geq 0$$



A) FIND R

$$R = \frac{V}{I} = \frac{160}{6.4} = \boxed{25 \Omega}$$

b) FIND τ :

$$\tau = \frac{1}{10} = \boxed{100 \text{ ms}}$$

c) FIND L:

$$\tau = \frac{L}{R} ; L = \tau R = \boxed{2.5 \text{ H}}$$

d) FIND initial energy stored in inductor:



$$w(0) = \frac{1}{2} L I^2 = \frac{1}{2} (2.5) (6.4)^2 = \boxed{51.2 \text{ J}}$$

e) time to dissipate 60% of $w(0)$

$$w(t) = 51.2(0.4) = 20.48 \text{ J}$$

$$20.48 = \frac{1}{2} L I^2 \Rightarrow I = 4.0477 \text{ A}$$


$$4.0477 = 6.4e^{-10t} \Rightarrow \boxed{t = 45.8 \text{ ms}}$$

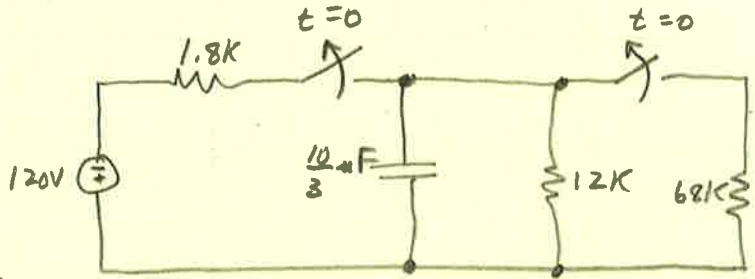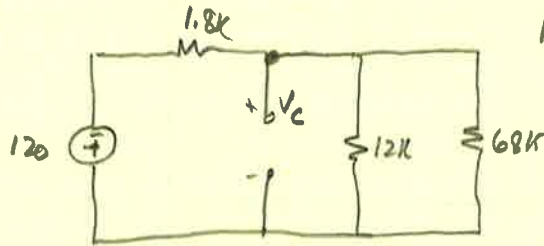For $t < 0$:

$$V_c(0^-) = \frac{-120(12||68)}{(12||68)+1.8} = -102V$$

for $t > 0$:

$$V_c(t) = -102e^{-25t}$$

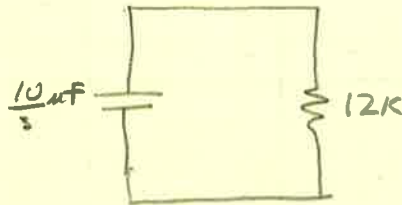

$$\text{Power} = \frac{V^2}{R} = .867e^{-50t}$$

- a) Find How many μJoules have been dissipated in R 12 ms after the switch opens.

$$W = \int_0^{.012} .867e^{-50t} dt$$

$$= \frac{.867}{-50} \left(e^{-50t} \Big|_0^{.012} \right) = \frac{.867}{-50} (.5488 - 1)$$

$$W = 7.824 \mu\text{J}$$

- b) How long does it take to dissipate 75% of the initial stored energy?

$$W(t) = \frac{1}{2} CV^2 = \frac{1}{2} \left(\frac{10}{3} \times 10^{-6} \right) (-102)^2 = 17.34 \text{ mJ}$$

$$75\% (W(t)) = 13 \text{ mJ}$$


$$\int_0^{t_0} .867e^{-50t} dt = .013 \Rightarrow t = 27.73 \text{ ms}$$

Switch moves @ $t=0$
Find $i_o(t)$ for $t \geq 0^+$

Before $t=0$,


$$i_c = 0 \text{ so } V_c(0) = 15V$$

after,

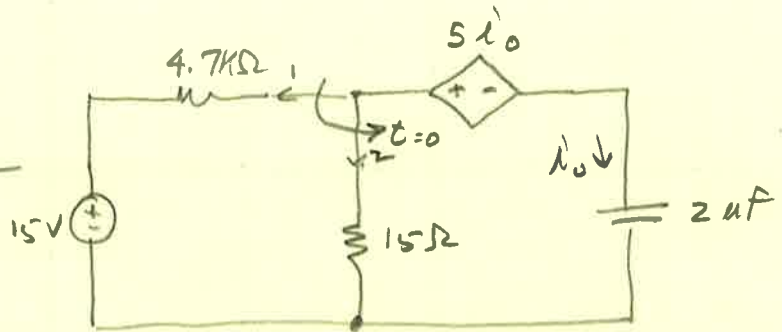

writing KVL,
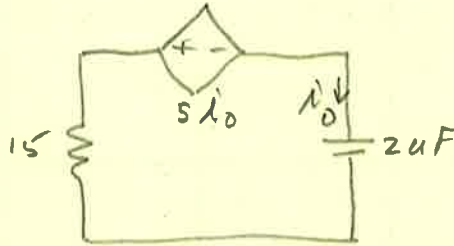
$$15i_o + 5i_o + \frac{1}{C} \int i_o dt = 0$$



$$20 \frac{di_o}{dt} + \frac{i_o}{C} = 0 \Rightarrow i_o = i_o(0) e^{-\frac{t}{20C}} = i_o(0) e^{-25,000t}$$

$$V_c = \frac{1}{C} \int i_c(t) dt = \frac{1}{C} \int i_o(t) e^{-25,000t} dt$$

$$V_c = \frac{i_o(0)}{-25,000C} e^{-25,000t}$$

$$V_c(0) = 15 = \frac{i_o(0)}{-25,000C} e^0 \Rightarrow i_o(0) = -0.75A$$

$$i_o(t) = -0.75 e^{-25,000t} \text{ A}$$

v_s is applied to the circuit shown.

$$v_c(0) = 0.0V$$

a) find v_o

$$v_c(t) = v_f(1 - e^{-\frac{t}{RC}}) + v_c(0)e^{-\frac{t}{RC}}$$

$$v_f = 50V$$

$$v_c(0) = 0$$

$$RC = (10 \times 10^{-9})(400 \times 10^3) = 0.004$$

$$v_c(t) = 50(1 - e^{-250t})V$$



$$v_o = v_s - v_c = 50e^{-250t} \quad 0 \leq t \leq 1ms$$

$$\text{@ } t = 1ms, v_c(1ms) = 50(1 - e^{-250(0.001)}) = 11.06V$$

$$v_c(\infty) = 0$$

$$v_c(t) = 11.06e^{-250(t-0.001)}$$

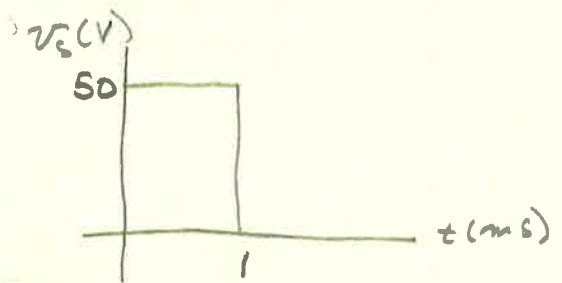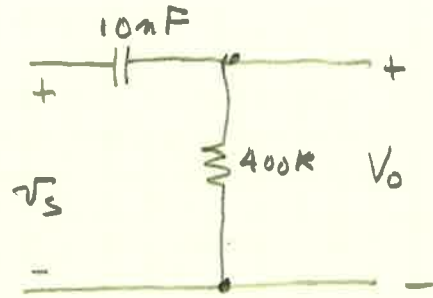
$$v_o(t) = v_s - v_c = -11.06e^{-250(t-0.001)} \quad t \geq 1ms$$




Switch closed at $t=0$

a) Find $i(0) + i(\infty)$

$i(0)$:

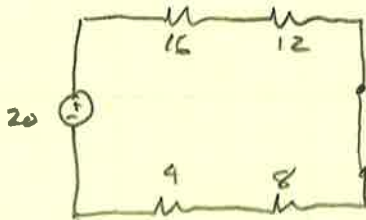

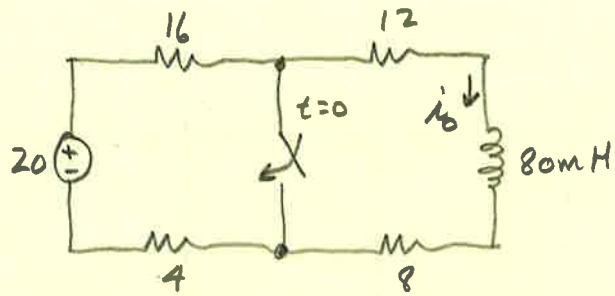
$$\downarrow i_0(0) = \frac{20}{40} = \underline{\underline{0.5A}}$$



$i(\infty) = \underline{\underline{0A}}$ (all energy is dissipated)

b) find $i(t)$ for $t \geq 0$

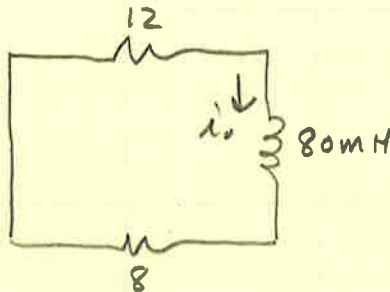


$$i_0(t) = I_0 e^{-\frac{t}{\tau}} = 0.5 e^{-\frac{R}{L}t} = \underline{\underline{0.5 e^{-250t} A}}$$

c) at what time is $i_0 = 100 \text{ mA}$?

$$100 \text{ mA} = 0.5 e^{-250t}$$


$$t = 6.94 \text{ ms}$$

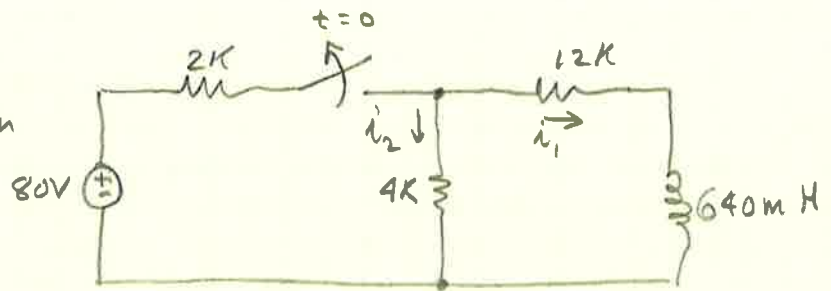The switch has been closed for a long time before opening @ $t=0$.



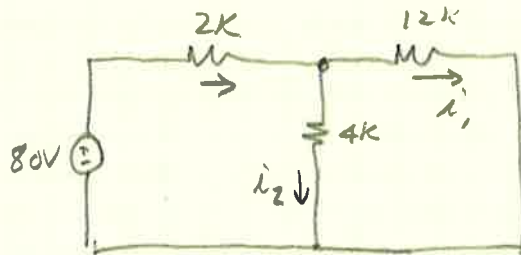a) find $i_1(0^-)$ and $i_2(0^-)$

$$i = \frac{80}{2k + 4k \parallel 12k} = 16 \text{ mA}$$




using a current divider

$$i_2(0^-) = \frac{i(12k)}{4k + 12k} = \frac{3}{4}i = 12 \text{ mA}$$

$$i_1(0^-) = \frac{i(4k)}{4k + 12k} = \frac{1}{4}i = 4 \text{ mA}$$

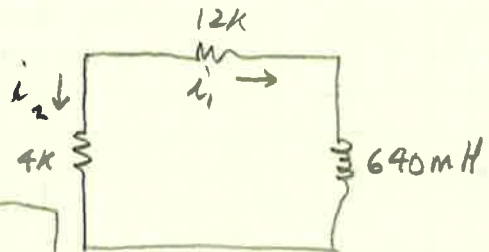b) find $i_1(0^+)$ and $i_2(0^+)$

Current cannot change instantaneously in an inductor.



So $i_1(0^-) = i_1(0^+) = 4 \text{ mA}$
 series we have a series circuit,
 $i_2(0^+) = -i_1(0^+) = -4 \text{ mA}$

c) find $i_1(t)$ for $t \geq 0$


$$i_1(t) = I_0 e^{-\frac{R}{L}t} = 4 e^{-\frac{16k}{.640}t} \text{ mA} = 4 e^{-25,000t} \text{ mA}$$

d) find $i_2(t)$ for $t \geq 0$

$$i_2(t) = -i_1(t) = -4 e^{-25,000t} \text{ mA}$$

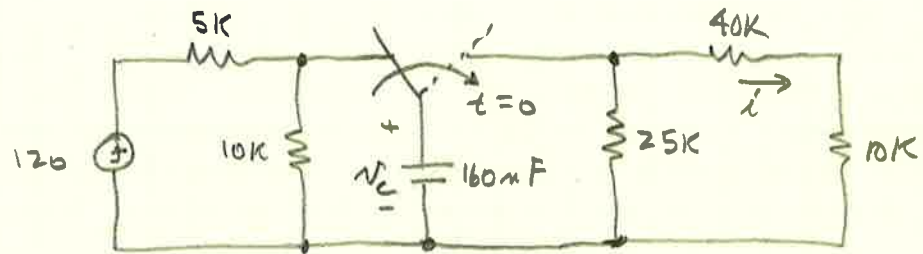e) explain why $i_2(0^-) \neq i_2(0^+)$

current in an inductor cannot change instantaneously, but current in a resistor can.




The switch has been in the left position for a long time. at $t=0$ it moves to the right position.

a) Find $v_c(t)$ for $t \geq 0$


$$v_c(t) = v_c(0) e^{-t/\tau} \text{ V}$$

The capacitor is an open circuit.
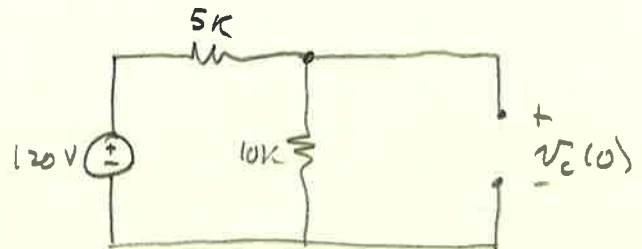
$$v_c(0) = \frac{120(10k)}{10k + 5k} = 80 \text{ V}$$



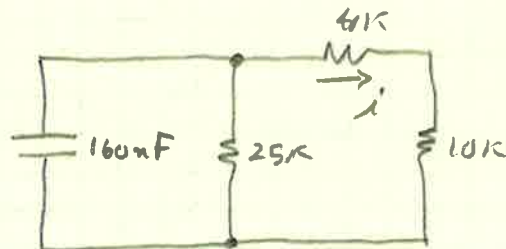for $t > 0$, the capacitor discharges through the circuit shown at the right.



$$R_{eq} = (40k + 10k) \parallel 25k = 16.667k\Omega$$

$$\tau = RC = (160 \times 10^{-9})(16.667k) = 2.667 \text{ ms}$$

$$v_c(t) = 80 e^{-375t} \text{ V}$$


b) find $i(t)$ for $t \geq 0$

$$\text{Since } v_c(t) = 80 e^{-375t},$$

$$i = \frac{v_c(t)}{40k + 10k} = 1.6 e^{-375t} \text{ mA} = i(t)$$

$$v = 72e^{-500t} \text{ V}, t \geq 0$$

$$i = 9e^{-500t} \text{ mA}, t \geq 0$$

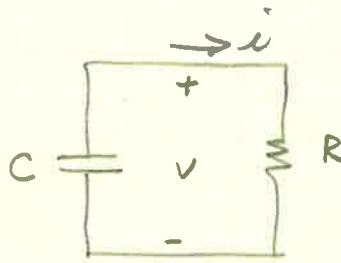

a) FIND R

$$R = \frac{v}{i} = \boxed{8 \text{ k}\Omega}$$

b) FIND C

$$\frac{1}{RC} = 500 \Rightarrow C = \frac{1}{500(8 \text{ k})} = \boxed{0.25 \mu\text{F}}$$

c) Find τ

$$\tau = \frac{1}{500} = \boxed{2 \text{ ms}}$$

d) initial energy in the capacitor

$$w = \frac{1}{2} c v^2 \Big|_{t=0} = \frac{1}{2} (.25 \times 10^{-6}) (72)^2 = \boxed{648 \mu\text{J}}$$

e) how many microseconds to dissipate 68% of the initial energy in the capacitor.

energy left is 32% of 648 μJ = 207.36 μJ

$$w = \frac{1}{2} c v^2 \text{ so } v = \sqrt{\frac{2w}{c}} = 40.7294 \text{ V}$$

$$40.7294 = 72e^{-500t} \Rightarrow \boxed{t = 1.139 \text{ ms}}$$