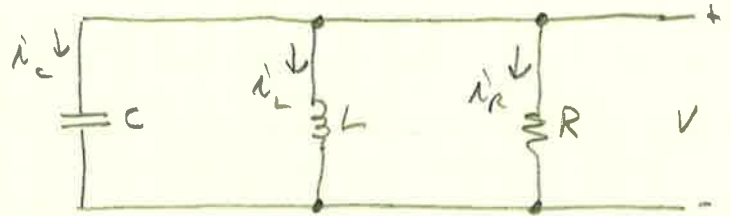


$$L = 10 \text{ mH}$$

for $t \geq 0$,

$$v(t) = 40e^{-1000t} - 90e^{-4000t} \text{ V}$$



a) Find ω_0 , α , C , and R

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1000$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -4000$$

adding, $-5000 = -2\alpha \Rightarrow \alpha = 2500 \text{ rad/s}$

$$-\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1000$$

$$-2500 + \sqrt{2500^2 - \omega_0^2} = -1000 \Rightarrow \omega_0 = 2000 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C = 25 \mu\text{F}$$

$$\alpha = \frac{1}{2RC} \Rightarrow R = 8 \Omega$$

b) Find $i_R(t)$, $i_L(t)$, and $i_C(t)$ for $t \geq 0^+$

$$i_R(t) = \frac{v(t)}{R} = 5e^{-1000t} - 11.25e^{-4000t} \text{ A} \leftarrow$$

$$i_C(t) = C \frac{dv_C}{dt} = (25 \times 10^{-6}) \left[-10000e^{-1000t} + 90(4000)e^{-4000t} \right]$$

$$= -e^{-1000t} + 9e^{-4000t} \text{ A} \leftarrow$$


$$i_L(t) = -(i_R + i_C) = -4e^{-1000t} + 2.25e^{-4000t} \text{ A} \leftarrow$$

For $t \geq 0$, Find $v(t)$ & $i_c(t)$

$$v_c(0) = i_c(0) = 0$$

$$i_c(\infty) = v(\infty) = 0$$

$$i_L(\infty) = 24 \text{ mA}$$

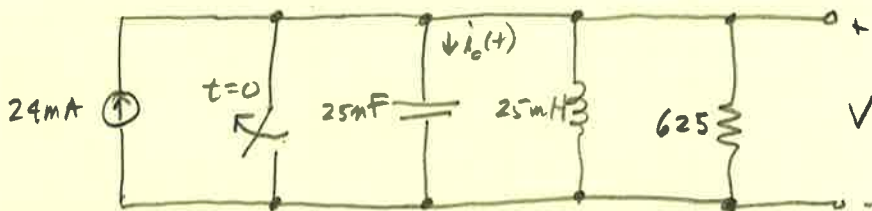

$$\alpha = \frac{1}{2RC} = \frac{1}{2(625)(25 \times 10^{-9})} = 32,000 \text{ rad/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{25 \times 10^{-3}(25 \times 10^{-9})}} = 40,000 \text{ rad/sec}$$

$$\omega_0 > \alpha \text{ So roots are underdamped } \omega_d = \sqrt{\omega_0^2 - \alpha^2} = 24,000 \text{ rad/s}$$

$$v_c(t) = v_{cf} + e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$= 0 + e^{-32,000t} (B_1 \cos 24,000t + B_2 \sin 24,000t)$$

$$v_c(0) = 0 = B_1$$

$$v_c(t) = e^{-32,000t} B_2 \sin 24,000t$$

$$i_c(0^+) = 24 \text{ mA} \text{ since } i_L \text{ can't change from } 0 \text{ @ } 0^- \text{ and } i_c \text{ change instantaneously}$$

$$i_c(0^+) = \left. \frac{dv_c}{dt} \right|_{t=0^+} = C \left[e^{-32,000t} B_2 (24,000) \cos 24,000t + B_2 \sin \dots \right]$$

$$24 \text{ mA} = 25 \times 10^{-9} (24,000) B_2 \Rightarrow B_2 = 40$$

$$v_c(t) = 40 e^{-32,000t} \sin 24,000t \text{ V}$$

$$i_c(t) = \frac{dv_c(t)}{dt} = C \left[40(24,000) e^{-32,000t} \cos 24,000t + \sin 24,000t (40)(-32,000) e^{-32,000t} \right]$$


$$i_c(t) = 24 e^{-32,000t} \cos 24,000t - 32 e^{-32,000t} \sin 24,000t \text{ mA}$$

$$i = B_1 e^{-200t} \cos 1500t + B_2 e^{-200t} \sin 1500t$$

$$C = 80 \text{ mF}$$

$$I_0 = 7.5 \text{ mA}$$

$$V_C(0) = -30 \text{ V}$$

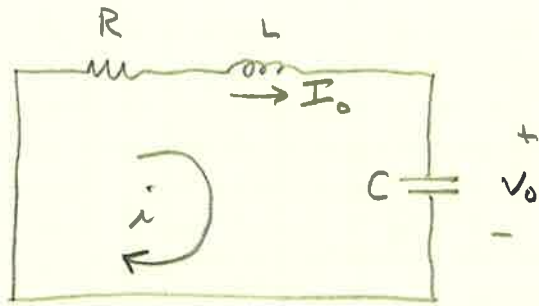

Find $R, L, B_1, \text{ and } B_2$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 1500 \quad \alpha = 2000$$

$$\omega_0^2 = \omega_d^2 + \alpha^2 \Rightarrow \omega_0 = 2500 \text{ rad/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega_0^2 C} = \boxed{2 \text{ H} = L}$$

$$\alpha = \frac{R}{2L} \Rightarrow R = 2L\alpha = 2(2)(2000) = \boxed{8000 \Omega = R}$$

$$i(0^-) = i(0^+) = 7.5 \text{ mA}$$

$$i(0^+) = \boxed{7.5 \text{ mA} = B_1}$$

$$i = 0.0075 e^{-200t} \cos 1500t + B_2 e^{-200t} \sin 1500t$$

$$\text{@ time } 0, \quad V_r + V_L + V_C = 0 \Rightarrow R I_0 + V_L - 30 = 0$$

$$-8000(0.0075) + 50 = V_L(0)$$

$$V_L(0) = -30 \text{ V}$$

$$V_L = L \frac{di}{dt}$$


$$-30 = V_L(0) = 2 \left[0.0075 e^{-200t} (-\sin 1500t)(1500) + \cos 1500t (-200)(0.0075) e^{-200t} + B_2 e^{-200t} \cos 1500t (1500) + \sin 1500t (-200) B_2 e^{-200t} \right] \Big|_{t=0}$$

$$-30 = 2 [-2000(0.0075) + B_2(1500)]$$

$$\boxed{B_2 = 0}$$

$$\boxed{i(t) = 0.0075 e^{-200t} \cos 1500t \text{ A}}$$

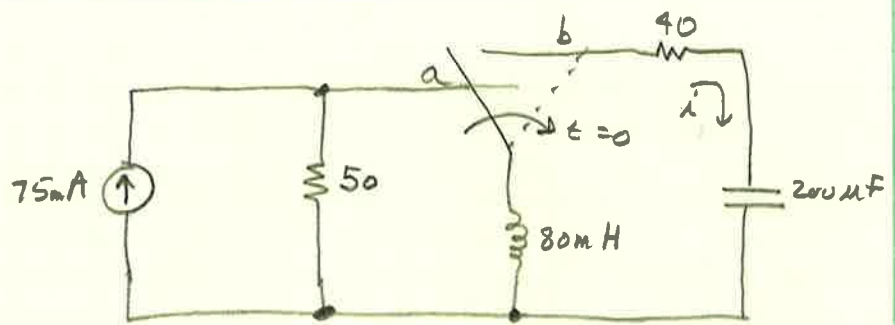
Switch has been at position a for a long time.
at $t=0$, switch moves to position b.
Find $i(t)$ for $t \geq 0$.



$$t < 0: i_L(0) = 75 \text{ mA}$$

$$v_C(0) = 0 \text{ V}$$


$$i(0) = -75 \text{ mA}$$

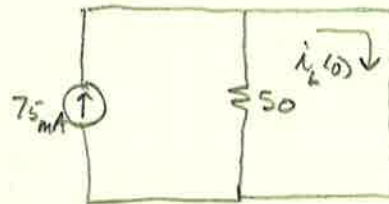

$t > 0$:

$$\alpha = \frac{R}{2L} = 250$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 250$$

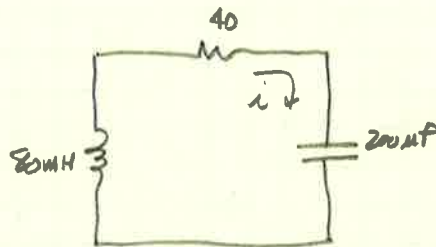

critically damped

$$i(t) = A_1 t e^{-250t} + A_2 e^{-250t}$$

$$\text{at } t=0, i = -75 \text{ mA} = A_2$$

$$i(t) = A_1 t e^{-250t} - 0.075 e^{-250t}$$

$$\text{KVL at } t=0: v_L + v_R + v_C = 0$$

$$L \frac{di_L}{dt} + (-0.075)(40) + 0 = 0$$

$$L \left[A_1 t (-250 e^{-250t}) + A_1 e^{-250t} - 0.075(-250) e^{-250t} \right]_{t=0} = 3$$

$$.08 [A_1 - 0.075(-250)] = 3$$


$$A_1 = 18.75$$

$$\therefore i(t) = 18.75 t e^{-250t} - 0.075 e^{-250t} \text{ A}$$

initial energy = 0

find $V_o(t)$ for $t \geq 0$
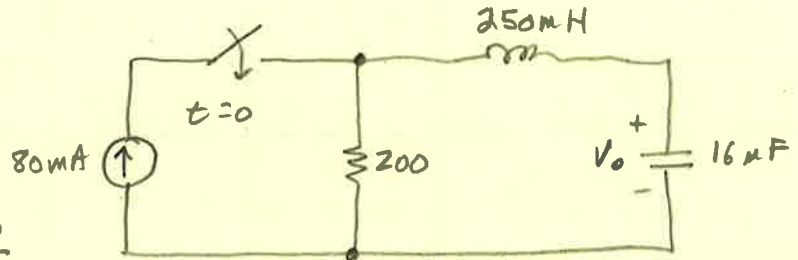
$$\alpha = \frac{R}{2L} = \frac{200}{2(.25)} = 400 \frac{\text{rad}}{\text{s}}$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{.25(16 \times 10^{-6})}} = 500 \frac{\text{rad}}{\text{s}}$$

$\omega_0 > \alpha$ so underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 300 \text{ rad/s}$$

$$v_o = V_f + B_1 e^{-400t} \cos 300t + B_2 e^{-400t} \sin 300t$$

$$v_o(\infty) = 200(.08) = 16\text{V}$$

$$v_o(0) = 16 + B_1 = 0 \Rightarrow B_1 = -16$$

$$\therefore v_o(t) = 16 - 16e^{-400t} \cos 300t + B_2 e^{-400t} \sin 300t$$

we know the current through the capacitor = 0 @ $t=0$

$$i_c = C \frac{dv_c}{dt} \Big|_{t=0} = 0 = C \left(-16e^{-400t} (300(-\sin 300t)) + \cos 300t (-16)(-400)e^{-400t} \right) + C \left(B_2 e^{-400t} \cos 300t (300) + \sin 300t (-400B_2 e^{-400t}) \right)$$

$$\text{evaluate @ } t=0 : 0 = (-16)(-400) + 300B_2$$

$$B_2 = -21.33$$

$$V_o(t) = 16 - 16e^{-400t} \cos 300t - 21.33e^{-400t} \sin 300t \text{ V}$$


$$R = 125 \Omega$$

$$L = 200 \text{ mH}$$

$$C = 5 \mu\text{F}$$

$$i_L(0) = -0.3 \text{ A}$$

$$V_C(0) = 25 \text{ V}$$

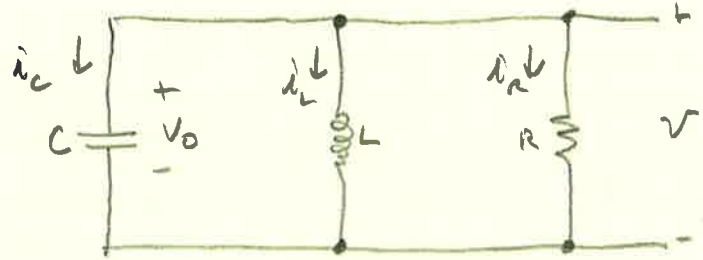

- a) Find the initial current in each element.

$$i_C = -300 \text{ mA}$$

$$i_R = \frac{V(0)}{R} = \frac{25}{125} = 200 \text{ mA} = i_R$$

$$i_C + i_L + i_R = 0 \Rightarrow i_L = -(i_C + i_R) = 100 \text{ mA} = i_L$$

- b) Find $v(t)$ for $t \geq 0$

$$\alpha = \frac{1}{2RC} = 800$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1000$$

$\omega_0 > \alpha$ so system is underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 600$$

$$v_C(t) = B_1 e^{-800t} \cos 600t + B_2 e^{-800t} \sin 600t$$

Finding B_1 and B_2 :

$$v_C(0) = 25 = B_1$$

$$\text{Node equation @ } t=0: i_C + i_L + i_R = 0$$

$$C \frac{dv}{dt} \Big|_{t=0} + (-300 \text{ mA}) + \frac{25}{125} = 0$$

$$(5 \times 10^{-6}) [-800 B_1 + B_2 \cdot 600] = 0.1$$

$$B_2 = 66.67$$

$$v = 25 e^{-800t} \cos 600t + 66.67 e^{-800t} \sin 600t \text{ V}$$

- c) Find $i_L(t)$ for $t \geq 0$

$$i_L = \frac{1}{L} \int_0^t v(t) dt = [-300 e^{-800t} \cos 600t - 191.7 e^{-800t} \sin 600t] \text{ mA}$$


the voltage response is

$$v(t) = D_1 e^{-80t} + D_2 e^{-80t} \quad t \geq 0$$

$$I_L(0) = -25 \text{ mA}$$

$$V_C(0) = 5 \text{ V}$$

$$R = 50 \Omega$$

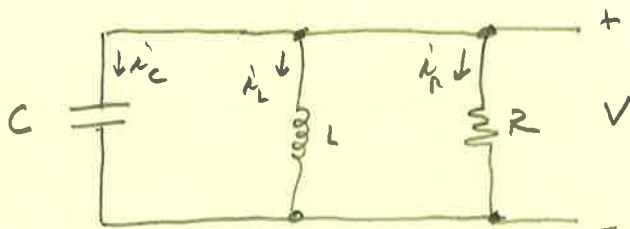

a) Find $C, L, D_1, + D_2$

Circuit is critically damped $\Rightarrow s_1 = s_2 = -\frac{1}{2RC} = -80$

$$C = \frac{1}{2(80)R} = \boxed{125 \mu\text{F}}$$

For critically damped, $\frac{1}{(2RC)^2} = \frac{1}{LC}$ or $L = 2^2 R^2 C = \boxed{1.25 \text{ H}}$

$$V(0) = \boxed{5 = D_2} \quad S_0$$

$$v(t) = D_1 e^{-80t} + 5 e^{-80t}$$

@ $t=0$, do node equation.

$$i_C(0) + i_L(0) + i_R(0) = 0$$

$$C \frac{dv_C(t)}{dt} + (-25 \text{ mA}) + \frac{V_C(t)}{R} = 0$$

$$125 \times 10^{-6} \left[D_1 (-80) e^{-80t} + e^{-80t} D_1 + 5(-80) e^{-80t} \right] \Big|_{t=0} - 25 \text{ mA} + \frac{5}{50} = 0$$

$$125 \times 10^{-6} [D_1 - 400] - 25 \text{ mA} + 0.1 = 0$$

$$\boxed{D_1 = -200}$$

b) find $i_C(t)$ for $t \geq 0^+$


$$i_C = C \frac{dv}{dt} = C \left[-200t (-80) e^{-80t} + e^{-80t} (-200) + 5(-80) e^{-80t} \right]$$

$$= C \left[16000t e^{-80t} - 600 e^{-80t} \right]$$

$$\boxed{i_C = (2t e^{-80t} - 0.75 e^{-80t}) \text{ A}}$$

Switch closes at $t=0$

Find $i_o(t)$ for $t \geq 0$

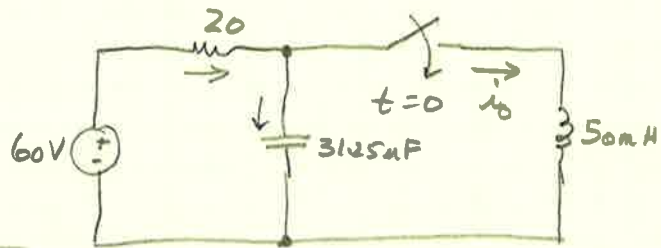


$$V_C(0) = 60 \text{ V}$$

$$i_L(0) = 0 \text{ A}$$

$$i_F(\infty) = \frac{60}{20} = 3 \text{ A}$$

$$\alpha = \frac{1}{2RC} = 800$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = 800$$

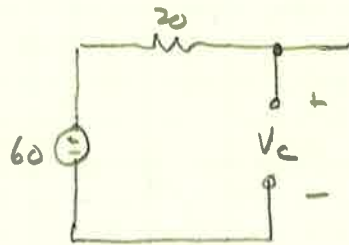

So critically damped.

$$i_o(t) = i_F + A_1 t e^{-800t} + A_2 e^{-800t}$$

$$i_o(0) = 0 = 3 + A_2 \Rightarrow A_2 = -3$$

$$\therefore i_o(t) = 3 + A_1 t e^{-800t} - 3 e^{-800t}$$

$$\left. \frac{di_o(t)}{dt} \right|_0 = A_1 t (-800 e^{-800t}) + A_1 e^{-800t} - 3(-800) e^{-800t} = \frac{V_L}{L} \Big|_{t=0}$$


$$A_1 + 2400 = \frac{60}{0.05} \Rightarrow A_1 = -1200$$

$$i_o(t) = 3 - (1200t + 3) e^{-800t} \text{ A}$$

R adjusted for critical damping.

$$V_C(0) = 15V$$

$$i_L(0) = 6mA$$

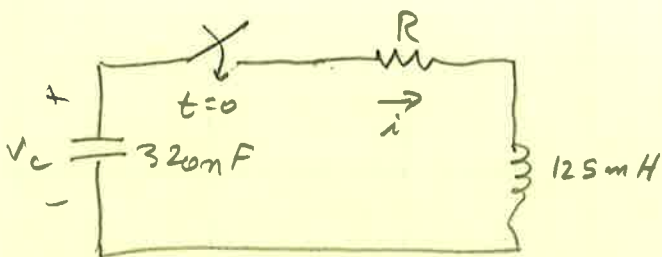

a) FIND R

$$\alpha = \omega_0 \Rightarrow \frac{R}{2L} = \sqrt{\frac{1}{LC}} \Rightarrow R = \boxed{1250 \Omega}$$

b) find $i(0^+)$ + $\frac{di}{dt}$ at 0^+

$$i(0^+) = i(0^-) = \boxed{6mA}$$

$$\text{@ } t=0^+ : V_C + V_R + V_L = 0$$

$$-15 + i(0)(1250) + V_L = 0 \Rightarrow V_L(0^+) = 7.5V$$

$$L \frac{di_L}{dt} = V_L = 7.5 \Rightarrow \left. \frac{di_L}{dt} \right|_{t=0^+} = \frac{V_L}{L} = \boxed{\frac{60A}{S}}$$

c) FIND $V_C(t)$ for $t \geq 0$

$$\text{critically damped so } V_C(t) = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$\text{where } s_{1,2} = -\alpha = -\frac{R}{2L} = -5000$$

$$\text{@ } t=0 : V_C(t) = 15 = D_2 \Rightarrow V_C(t) = D_1 t e^{-5000t} + 15 e^{-5000t}$$

$$i_C = C \frac{dV_C}{dt} = C [D_1 t (-5000 e^{-5000t}) + e^{-5000t} (D_1) + 15(-5000) e^{-5000t}] \Big|_{t=0}$$

$$i_C(0) = -i_L(0) = -6mA = C [D_1 + 15(-5000)] \Rightarrow D_1 = 56,250 \frac{V}{s}$$

$$\boxed{V_C = 56,250 t e^{-5000t} + 15 e^{-5000t} \text{ V } \quad t \geq 0}$$