

$$v(t) = 80 \cos(10t + 20^\circ) \text{ V}$$

$$i(t) = 15 \cos(10t + 60^\circ) \text{ A}$$

Find the instantaneous and average Power

$$P_{\text{INST}} = v(t) i(t)$$

$$= \frac{V_m I_m}{2} \left\{ \cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i) \right\}$$

$$= \frac{80(15)}{2} \left(\cos(-40^\circ) + \cos(20t + 80^\circ) \right)$$


$$P_{\text{INST}} = 459.6 + 600 \cos(20t + 80^\circ) \text{ W}$$

$$P_{\text{AVG}} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{80(15)}{2} \cos(-40^\circ)$$

$$P_{\text{AVG}} = 459.6 \text{ W}$$

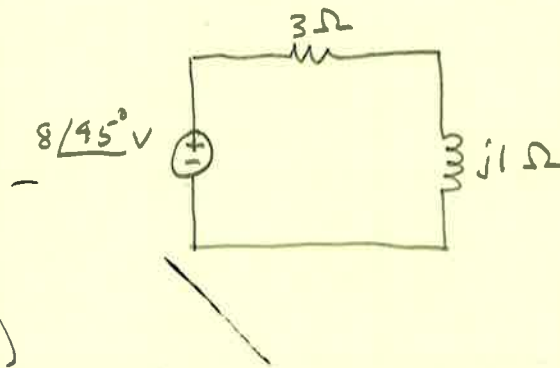Calculate the average power absorbed by the resistor and inductor + the power supplied by the source



$$P_{\text{AVG}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$i = \frac{8\angle 45^\circ}{3 + j1} = \frac{8\angle 45^\circ}{3.162\angle 18.4^\circ} = 2.53\angle 26.6^\circ \text{ A}$$

$$V_R = iR = 7.59\angle 26.6^\circ$$

$$V_L = iZ_L = 2.53\angle 116.6^\circ$$

$$P_{\text{AVG}_R} = \frac{1}{2} (7.59)(2.53) \cos(26.6^\circ - 26.6^\circ) = \underline{\underline{9.6 \text{ W}}}$$

$$P_{\text{AVG}_L} = \frac{1}{2} (2.53)(2.53) \cos(116.6^\circ - 26.6^\circ) = \underline{\underline{0 \text{ W}}}$$

$$P_{\text{SOURCE}} = \frac{1}{2} (8)(2.53) \cos(45^\circ - 26.6^\circ) = \underline{\underline{9.6 \text{ W}}}$$

1) Calculate the average and reactive powers if:

$$V = 100 \cos(\omega t + 15^\circ) \text{ V}$$

$$I = 4 \sin(\omega t - 15^\circ) \text{ A}$$

using the trig identity $\sin \omega t = \cos(\omega t - 90^\circ)$

$$I = 4 \cos(\omega t - 105^\circ) \text{ A}$$


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (100)(4) \cos(15 - (-105)) = \underline{\underline{-100 \text{ W}}}$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = \frac{1}{2} (100)(4) \sin(15 + 105) = \underline{\underline{173.21 \text{ VAR}}}$$

2) Is the circuit delivering or absorbing average + reactive power?

Since average power is negative - delivering.
 " Reactive " " positive - absorbing

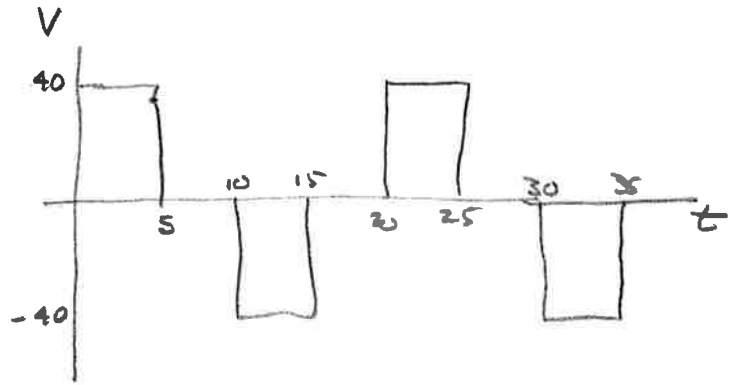a) Find the RMS value of the periodic waveform.



$$\begin{aligned}
 V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T V^2 dt} \\
 &= \left[\frac{1}{20} \left(\int_0^5 40^2 dt + \int_{10}^{15} (-40)^2 dt \right) \right]^{1/2} \\
 &= \left[\frac{1}{20} (1600(5) + 1600(15-10)) \right]^{1/2} \\
 &= 28.28 \text{ V}_{\text{RMS}}
 \end{aligned}$$

$$b) P_{\text{Avg}} = \frac{V^2}{R} = 20 \text{ W}$$