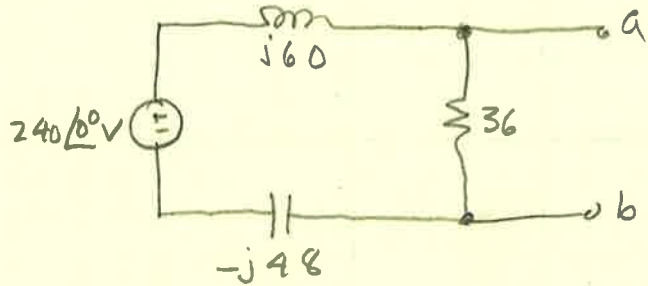


Use source transformation to find thevenin equiv. at ab.



$$Z = j60 - j48 = j12$$


$$I = \frac{V}{Z} = \frac{240 \angle 0^\circ}{12 \angle 90^\circ} = 20 \angle -90^\circ$$

$$Z \parallel 36 = \frac{(j12)(36)}{12j + 36}$$

$$= \frac{432 \angle 90^\circ}{37.95 \angle 18.43^\circ}$$

$$= 11.384 \angle 71.565^\circ$$


$$= Z_{th}$$

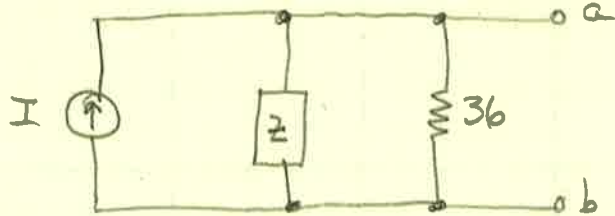

$$V_{th} = I_{th} Z_{th}$$

$$= 20 \angle -90^\circ (11.384 \angle 71.565^\circ)$$
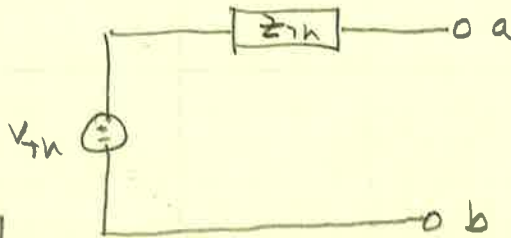
$$= 227.7 \angle -18.435^\circ \text{ V}$$



$$V_{th} = 227.7 \angle -18.435^\circ \text{ V}$$

$$= 216 - 72j \text{ V}$$

$$Z_{th} = 11.384 \angle 71.565^\circ \Omega$$

$$= 3.6 + 10.8j \Omega$$

$$i = 125 \cos(800t + 36.87^\circ) \text{ mA}$$

a) FIND F

$$800 = \omega = 2\pi f \Rightarrow f = \frac{800}{2\pi} = \boxed{127.32 \text{ Hz}}$$

b) FIND T in milliseconds

$$T = \frac{1}{f} = \frac{1}{127.32} = \boxed{7.854 \text{ ms}}$$

c) FIND I_m

$$I_m = \boxed{125 \text{ mA}}$$

d) FIND $i(0)$

$$i(0) = 125 \cos(36.87^\circ) = \boxed{100 \text{ mA}}$$

e) FIND ϕ in degrees + radians

$$\boxed{\phi = 36.87^\circ} = \frac{36.87(2\pi)}{360^\circ} = \boxed{0.644 \text{ radians} = \phi}$$

f) Smallest positive value of t for which $i = 0$.

$$0 = 125 \cos(800t + 36.87^\circ)$$

$$800 \frac{\text{rad}}{\text{sec}} t = 53.13^\circ = 53.13 \left(\frac{2\pi \text{ rad}}{360^\circ} \right) = 0.9273 \text{ rad}$$

$$t = \frac{0.9273}{800} = \boxed{1.159 \text{ ms}}$$


g) Smallest positive value of t at which $\frac{di}{dt} = 0$

$$\frac{di}{dt} = 125(-800 \sin(800t + 36.87^\circ))$$

$$\frac{di}{dt} = 0 \text{ when } 800t + 36.87^\circ = 180^\circ$$

$$t = \frac{(180^\circ - 36.87^\circ) \left(\frac{2\pi}{360} \right)}{800} = \boxed{3.12 \text{ ms}}$$
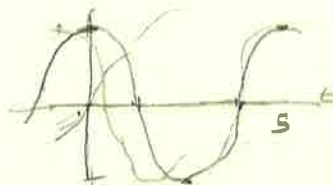
$$v(t) = 25 \cos(400\pi t + 60^\circ) \text{ V}$$



a) what is the maximum amplitude of v ?

$$V_{\max} = 25 \text{ V}$$

b) Find freq. in Hz

$$\omega = 2\pi f = 400\pi \Rightarrow f = \frac{400\pi}{2\pi} = 200 \text{ Hz}$$

c) Find freq in rad/sec $\Rightarrow \omega = 400\pi = 1257 \text{ rad/sec}$

d) Find phase angle in radians

$$\theta = 60^\circ = 60 \left(\frac{\pi}{180} \right) = \frac{\pi}{3} = 1.047 \text{ rad}$$

e) find θ in degrees

$$\theta = 60^\circ$$

f) find period

$$P = \frac{1}{f} = \frac{1}{200} = 5 \text{ ms}$$

g) what is the first time after $t=0$ that $v=0$ V?

for $\cos v=0$ after $\frac{1}{4}$ period

$$\text{But } 60^\circ = \frac{1}{6} \text{ period so crosses 0 after } \left(\frac{1}{4} - \frac{1}{6} \right) 5 \text{ ms} = \frac{1}{12} (5 \text{ ms}) = 416.7 \text{ ms}$$

h) v is shifted $\frac{5}{6}$ ms to the right. what is the new $v(t)$?

$$\frac{5}{6} \text{ ms is } \frac{1}{6} \text{ of a period} = 60^\circ \text{ so } v = 25 \cos 400\pi t \text{ V}$$

i) what is the minimum number of ms that the function must be shifted to the left for $v(t) = 25 \sin 400\pi t$ V?


$$\text{must be shifted } \frac{3}{4}T - \frac{1}{6}T = \frac{7}{12}T = 2.917 \text{ ms}$$

$$V_s = 75 \cos(4000t - 60^\circ)$$

$$R = 400 \Omega$$

$$L = 75 \text{ mH}$$

$$i_L(0) = 0 \text{ A}$$

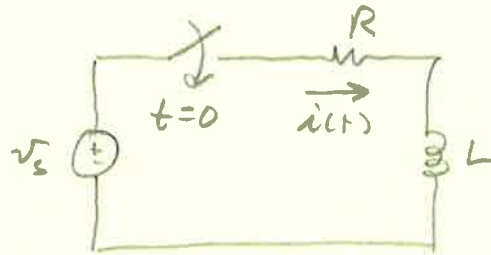

a) Find $i(t)$ for $t > 0$.

From equation 9.9:

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-t/\tau} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$\phi = -60^\circ, \quad \theta = \tan^{-1} \frac{\omega L}{R} = \tan^{-1} \frac{(4000)(0.075)}{400} = 36.87^\circ$$

$$i(t) = \frac{-75}{\sqrt{400^2 + 4000^2 (0.075)^2}} \cos(-60^\circ - 36.87^\circ) e^{-5333t} + \frac{75}{\sqrt{400^2 + 4000^2 (0.075)^2}} \cos(4000t - 60^\circ - 36.87^\circ)$$

$$i(t) = \underbrace{(+17.94 e^{-5333t})}_{\text{transient}} + \underbrace{150 \cos(4000t - 96.87^\circ)}_{\text{steady state}} \text{ mA}$$

b) What are the transient and steady state components?

c) Find i @ $t = 750 \mu\text{s}$

$$i(750 \mu\text{s}) = 39.45 \text{ mA}$$

d) What are the max amplitude, freq, + phase angle of the steady state current?

$$\begin{aligned} \text{Amp max} &= 150 \text{ mA} \\ f_{\text{max}} &= 4000 \text{ rad/sec} \\ \text{phase } \angle &= -96.87^\circ \end{aligned}$$


e) By how many degrees are the voltage + SS current out of phase?

→ The current lags the voltage by 36.87° .

$$f = 80,000 \text{ Hz}$$

$$v = 25 \sin(2\pi f \cdot t) \text{ mV}$$
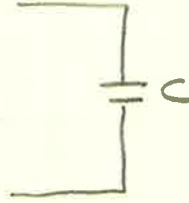
$$i = 628.32 \sin(2\pi f \cdot t + 90^\circ) \mu\text{A}$$



a) Find frequency in rad/sec

$$\omega = 2\pi f = 502,655 \text{ rad/sec}$$

b) Find phase of current.

$$v = 0.025 \angle 0$$

$$i = 628.32 \times 10^{-6} \angle 90^\circ$$

$$\theta_i = 90^\circ$$

c) Find Z_{cap}

$$Z_{cap} = \frac{v}{i} = \frac{1}{j\omega C} = \frac{0.025 \angle 0}{628.32 \times 10^{-6} \angle 90^\circ}$$

$$Z_{cap} = 39.79 \angle -90^\circ \Omega = -39.79 \Omega$$

$$Z_{cap} = -39.79 \Omega$$

d) Find C


$$Z_c = \frac{1}{j\omega C} = 39.79 \angle -90^\circ$$

$$C = \frac{1}{39.79 \angle -90^\circ (j)(\omega)} = 0.05 \mu\text{F}$$

$$C = 0.05 \mu\text{F}$$

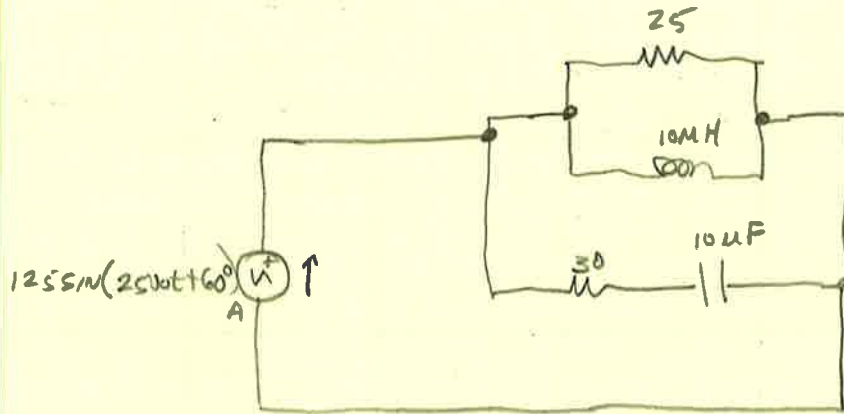e) Find Z_{cap}

$$Z_{cap} = 39.79 \angle -90^\circ = -j39.79$$




a) Draw Frequency-domain equivalent circuit

$$\omega = 2500$$

$$Z_L = j\omega L = 25j \Omega$$

$$Z_C = \frac{1}{j\omega C} = -40j \Omega$$
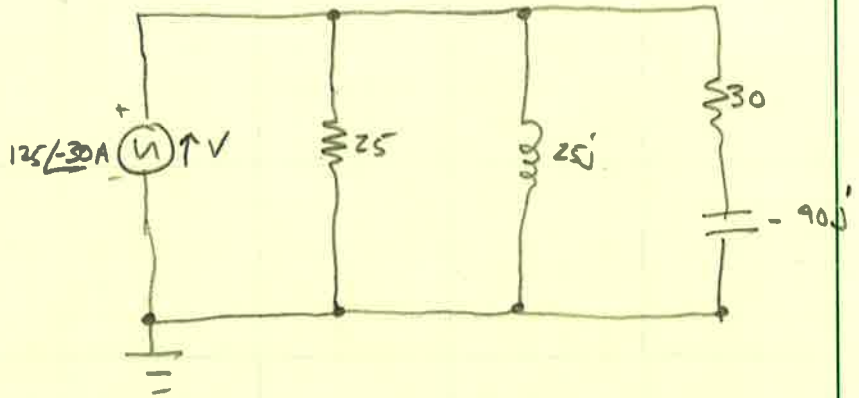
$$\text{Source: } 125 \sin \dots \\ = 125 \angle -30^\circ$$



b) Find V


$$Z_{eq} = 25 \parallel 25j \parallel (30 - 40j) = 17.46 \angle 24.78^\circ \Omega$$

$$V = I Z = 2182.6 \angle -5.22^\circ V$$

c) Find SS expression for $V(t)$

$$V(t) = 2182.6 \cos(2500t - 5.22^\circ) V$$


FIND $i_o(t)$.

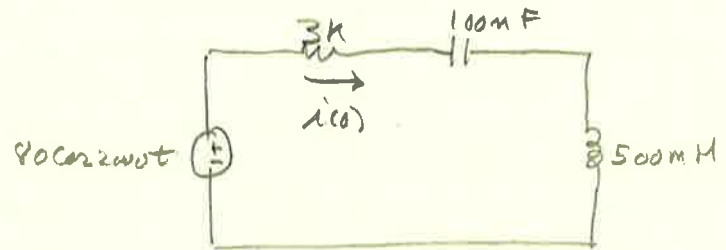

Convert to frequency domain using:

$$Z_L = j\omega L = j(2000)(0.5) = 1000j \Omega$$

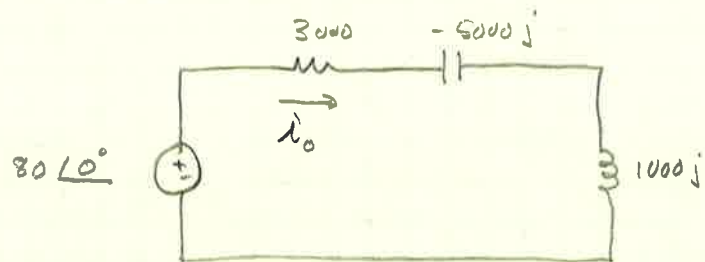
$$Z_C = \frac{1}{j\omega C} = -j \left(\frac{1}{2000(100 \times 10^{-6})} \right) = -5000j \Omega$$



$$\begin{aligned} \text{Loop equation: } 80 \angle 0^\circ &= i_o (3000 - 5000j + 1000j) \\ &= i_o (3000 - 4000j) \\ &= i_o (5000 \angle -53.13^\circ) \end{aligned}$$

$$\begin{aligned} i_o(t) &= \frac{80 \angle 0^\circ}{5000 \angle -53.13^\circ} = 16 \angle 53.13^\circ \text{ mA} \\ &= 16 \cos(2000t + 53.13^\circ) \text{ mA} \end{aligned}$$


use mesh-current method to find v_o .

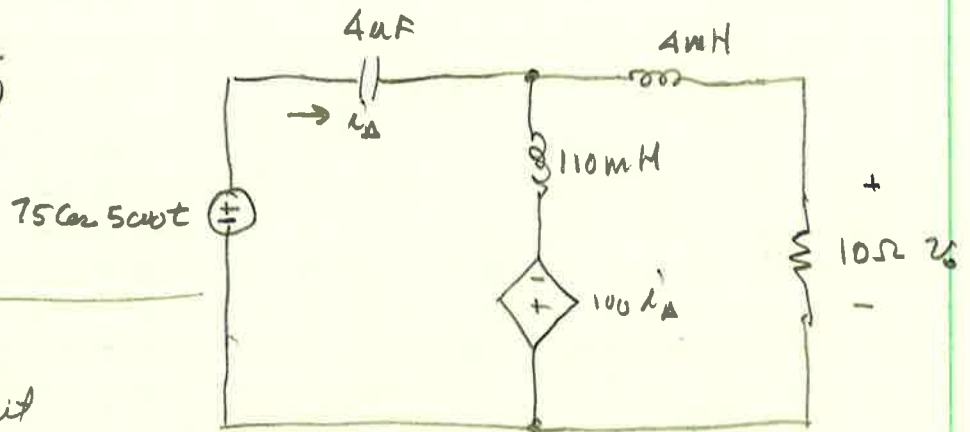

1) transform circuit

$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$

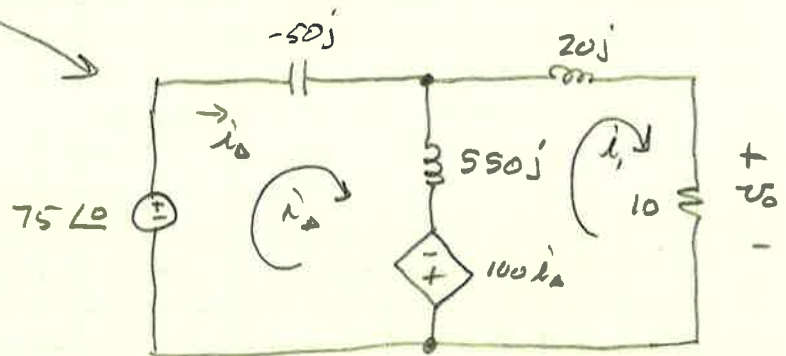

2) write mesh equations:

$$i_{\Delta}: -75 \angle 0 - 50j(i_{\Delta}) + 550j(i_{\Delta} - i_1) - 100 \angle 0 = 0$$

$$i_1: 20j(i_1) + 10(i_1) + 100 \angle 0 + 550j(i_1 - i_{\Delta}) = 0$$

$$i_{\Delta}: i_{\Delta}(400j) + i_1(-550j) = 75 \angle 0$$

$$i_1: i_{\Delta}(100 - 550j) + i_1(10 + 570j) = 0$$

$$\text{Solving: } i_{\Delta} = 3.25j \text{ A}$$

$$i_1 = 2.5j \text{ A}$$


$$v_o = 10(i_1) = 25j = 25 \angle 90^\circ = 25 \cos(5000t + 90^\circ) \text{ V}$$

10.64

HAGT 8th

Find the Thevenin equivalent seen by the $2-j\ \Omega$ impedance

then find I_1

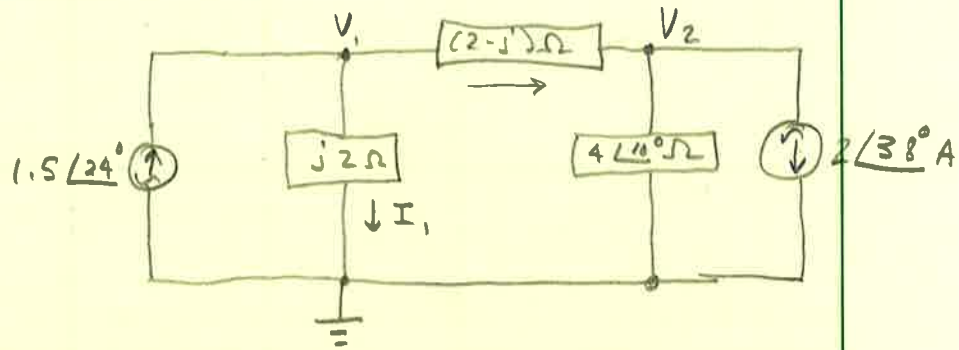


$$\begin{aligned} Z_{th} &= j2 + 4 \angle 10^\circ \\ &= 3.9392 + j 2.6946 \\ &= \boxed{4.773 \angle 34.3737^\circ \ \Omega} \end{aligned}$$

$$V_1 = j2(1.5 \angle 24^\circ) = (2 \angle 90^\circ)(1.5 \angle 24^\circ) = 3 \angle 114^\circ \text{ V}$$

$$V_2 = (4 \angle 10^\circ)(-2 \angle 38^\circ) = -8 \angle 48^\circ = 8 \angle -132^\circ \text{ V}$$

$$\begin{aligned} V_{th} = V_1 - V_2 &= 3 \angle 114^\circ - 8 \angle -132^\circ \\ &= -1.2202 + j 2.7406 - (-5.353 - j 5.9452) \end{aligned}$$
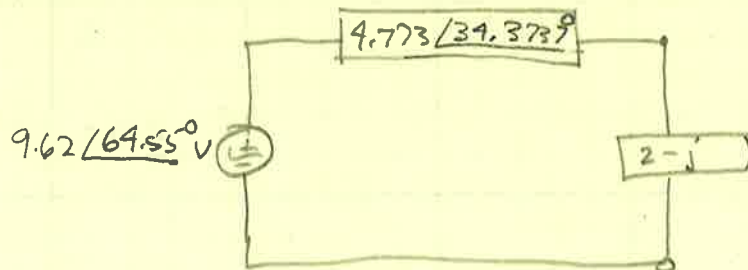
$$= 4.133 + j 8.6858 = \boxed{9.62 \angle 64.55^\circ \text{ V}}$$




$$I_{2-j} = \frac{V}{Z} = \frac{9.62 \angle 64.55^\circ}{4.773 \angle 34.3737^\circ} = 2.0153 \angle 30.18^\circ \text{ A}$$

$$\begin{aligned} I_1 &= 1.5 \angle 24^\circ - 2.0153 \angle 30.18^\circ \text{ A} \\ &= 1.3703 + j 0.6101j - (1.7421 + j 1.0131j) \\ &= -0.3718 - j 0.403j \text{ A} \end{aligned}$$

$$= \boxed{0.548 \angle -132.7^\circ \text{ A}}$$

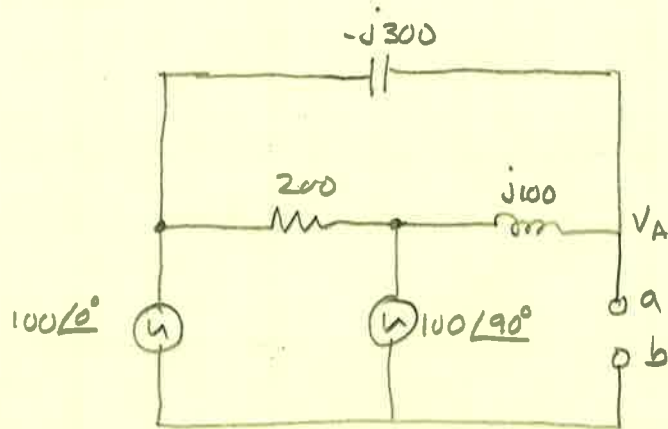
Find the Thevenin equivalent @ terminals ab.



Z_{th}

$$\begin{aligned} Z_{in} &= j100 \parallel -j300 \\ &= \frac{(j100)(-j300)}{j100 - j300} \\ &= 30000 / -200j \end{aligned}$$

$$Z_{in} = 150j \Omega$$

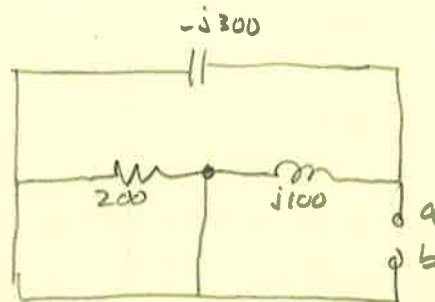

V_{th}

$$\text{NODE A: } \frac{100 \angle 0^\circ - V_A}{-j300} = \frac{V_A - 100 \angle 90^\circ}{j100}$$

$$V_A = 158.11 \angle 108.43^\circ \text{ V}$$