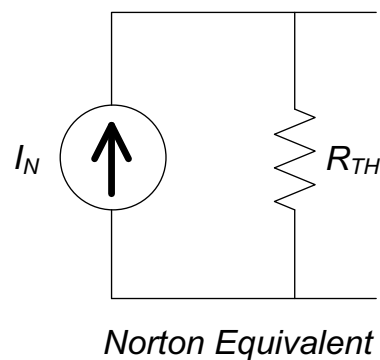
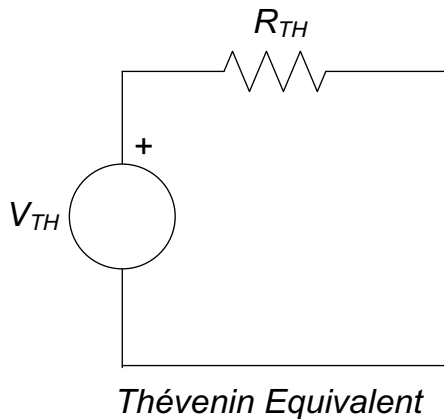


**Thévenin and Norton Equivalent Circuits**

Name \_\_\_\_\_

**Introduction**

Solving electrical networks is often made easier by using Thévenin and Norton equivalent circuits to model an entire network. The Thévenin and Norton equivalents as shown below are themselves equivalent to each other as long as  $V_{TH} = I_N R_{TH}$ . This experiment considers how to determine the parameters of the equivalent circuits for a T-configuration of resistors attached to a voltage source as shown in step 2 on the following page.

**Objectives**

- Verify Thévenin's theorem;
- Verify Norton's theorem;
- Verify the Maximum Power Transfer theorem.

**Equipment**

- Digilent Analog Discovery 2 Module;
- Handheld DMM;
- Breadboard;
- Assorted resistors;
- Assorted wires.

**References**

- Zybooks text book;
- Course web site;
- Resistor color-code chart.

**Note:** For any measured value using your multi-meter, record the value displayed. For calculations, round your results to four significant digits but carry more digits in intermediate calculations.


**Procedure**

- 1) Select three of your resistors with the values shown below. Measure and record their resistance values. Calculate percentage error using the following formula:

$$\text{Percentage Error} = |(Nominal\ value - Measured\ value)| / (Nominal\ value) * 100\%$$

Resistor	Nominal Value	Measured Value	Percentage Error
R <sub>1</sub>	100 Ω		
R <sub>2</sub>	560 Ω		
R <sub>3</sub>	330 Ω		

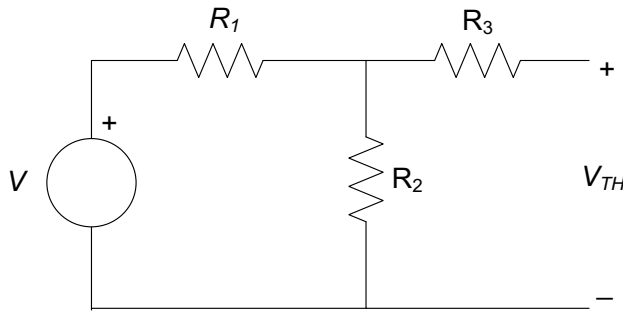- 2) Using the resistor values you measured in step 1, calculate the Thévenin resistance ( $R_{TH}$ ) in the circuit below and record it in step 3. This is the resistance seen looking into the circuit from the right, i.e. into the + and – terminals. Remember to replace the voltage source with a short circuit.



- 3) Wire up the T-network circuit shown above, except initially replace the voltage source with a short circuit and measure the Thévenin resistance ( $R_{TH}$ ) with your meter. This is the resistance seen looking into the circuit from the right, i.e. into the + and – terminals. Record the measured value and calculate the % Error.

$$R_{TH, Calculated} = \underline{\hspace{2cm}} \Omega \quad R_{TH, Measured} = \underline{\hspace{2cm}} \Omega \quad Error = \underline{\hspace{2cm}} \%$$



- 7) Using Excel or a similar graphing program, do a least squared error trendline fit to the **calculated** ( $I_R$ ,  $V_R$ ) data in the table above to determine the **calculated** Thévenin voltage,  $V_{TH}$ , and the **calculated** Norton current,  $I_N$ . Plot  $V_R$  (V) on the y-axis and  $I_R$  (mA) on the x-axis. The Thévenin voltage is the y-intercept, i.e. the open-circuit voltage, and the Norton current is the x-intercept, i.e. the short-circuit current. The slope of the line is the negative of the Thévenin (Norton) resistance divided by 1000. Label these points on the graph and record their values below, along with the calculated value of  $R_{TH}$ . Print out a copy of the graph.

$$V_{TH} = \underline{\hspace{2cm}} \text{ V} \qquad I_N = \underline{\hspace{2cm}} \text{ mA}$$

$$R_{TH} = \underline{\hspace{2cm}} \Omega \qquad r^2 = \underline{\hspace{2cm}}$$

- 8) Next, do a least squared error trendline fit to the **measured** ( $I_R$ ,  $V_R$ ) data in the table above to determine the Thévenin voltage,  $V_{TH}$ , and the Norton current,  $I_N$ . Label these points on the graph and record their values below, along with the calculated value of  $R_{TH}$ . Print out a copy of the graph.

$$V_{TH} = \underline{\hspace{2cm}} \text{ V} \qquad I_N = \underline{\hspace{2cm}} \text{ mA}$$

$$R_{TH} = \underline{\hspace{2cm}} \Omega \qquad r^2 = \underline{\hspace{2cm}}$$

- 9) Compile all measured and calculated values in the table below.

	$V_{TH}$	$I_N$	$R_{TH}$
Measured (step 4)			X
Calculated (step 5)			X
Trendline <sub>Calc</sub> (step 7)			
Trendline <sub>Meas</sub> (step 8)			

- 10) Using values of  $V_{TH}$  and  $R_{TH}$  from the trendline analysis, and the equation below, calculate the power dissipated in the resistor R for all values of R shown in the table. Compute  $P_R$  from both your calculated and measured data.

$$P = \left( \frac{V_{TH}}{R_{TH} + R} \right)^2 R$$

<b>R Ω</b>	<b>51  100</b>	<b>51</b>	<b>100</b>	<b>330  470</b>	<b>330</b>	<b>470</b>	<b>560</b>	<b>667</b>	<b>767</b>	<b>1000</b>
$P_{Calc}$ (mW)										
$P_{Meas}$ (mW)										

- 11) Using Excel, plot the calculated and measured power from step 10 above versus the load resistance R. Place power on the y-axis and resistance on the x-axis. Use different symbols for each and identify the curves as calculated and measured. Print out a copy of the graph.
- 12) From the Thévenin equivalent circuit (using the values of  $V_{TH}$  and  $R_{TH}$  from the **measured** trendline analysis in step 9) and the *Maximum Power Theorem*, calculate the maximum power dissipated by R and the value of R when this occurs. Compare this result with what you observe from the plot in step 11.

	<b><math>P_{MAX}</math></b>	<b>R</b>
$P_{MAX}$ Theorem		
Curve of calculated power (eyeball from graph)		
Curve of measured power (eyeball from graph)		

---

### To Turn In

Do your work on either the .pdf or .docx version of the lab and place in the **lab3** drop box by 11:59pm on Sunday, April 26.