

The book cover for ENGR 228: Circuit Analysis features an orange background with a circular diagram of electrical symbols. The diagram is divided into segments containing the following labels: V^2/R , $R \times I$, P/I , $R \times I^2$, $V \times I$, P , V , I , and R . At the bottom of the cover, it reads "Multiple instructors" and "SPRING 2020".

Chapter 3.2,3
Analysis Techniques
Super-Node and Super-Mesh
Methods

Engr228 - Circuit Analysis
Spring 2020

Dr Curtis Nelson

Section 3.2a and 3.3a Objective


- Learn to identify and apply the super-node and super-mesh analysis methods to analyze an electric circuit.

Circuit Analysis

- We need an organized method of applying KVL, KCL, and Ohm's law;
- *Nodal* analysis assigns *voltages* to each node, and then we apply *Kirchhoff's Current Law* to solve for the *node voltages*;
- *Mesh* analysis assigns *currents* to each mesh, and then we apply *Kirchhoff's Voltage Law* to solve for the *mesh currents*.


Mesh Analysis: Nodal Alternative

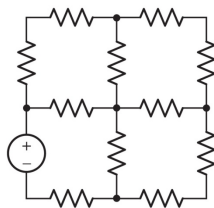- A mesh is a loop that does not contain any other loops within it;
- In mesh analysis, we assign mesh currents and solve using KVL;
- All terms in the equations are in units of *voltage*;
- Remember – voltage drops in the direction of current flow except for sources that are generating power;
- The circuit below has four meshes:




Node or Mesh: How to Choose?

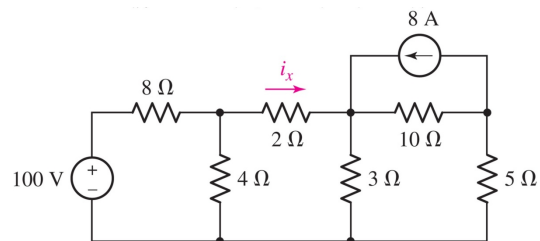- Use the one with fewer equations, or
- Use the method you like best, or
- Use both, and check your answers.




Voltage Sources and the Supernode

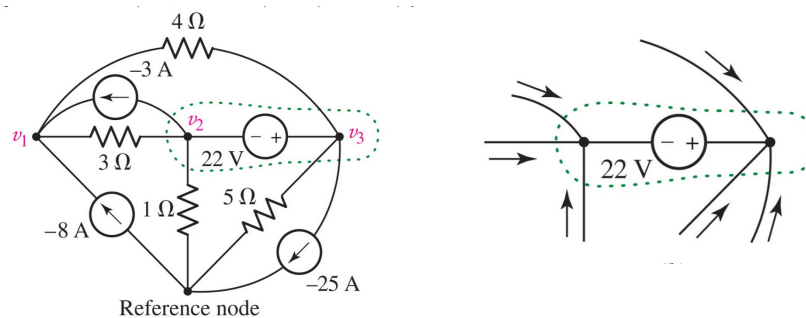If there is a DC voltage source between two non-reference nodes the current through the voltage source may not be known and an equation cannot be written for it. Therefore, we create a *supernode*.



The Supernode Analysis Technique

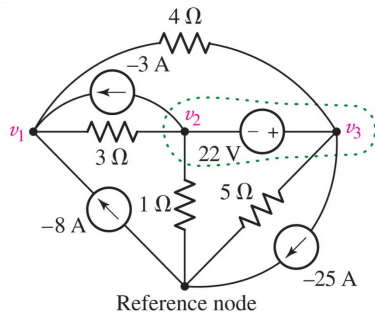

$$\begin{aligned}v_1 &= 1.0714V \\v_2 &= 10.5V \\v_3 &= 32.5V\end{aligned}$$

- Apply KCL at Node v_1 ;
- Apply KCL at the supernode;
- Add the equation for the voltage source inside the supernode.


$$\frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{3} = -3 - 8$$

$$\frac{v_1 - v_2}{3} + \frac{v_1 - v_3}{4} = -3 + \frac{v_2}{1} + \frac{v_3}{5} - 25$$

$$v_3 - v_2 = 22$$

Textbook Problem 4.36 (Nilsson 11th)

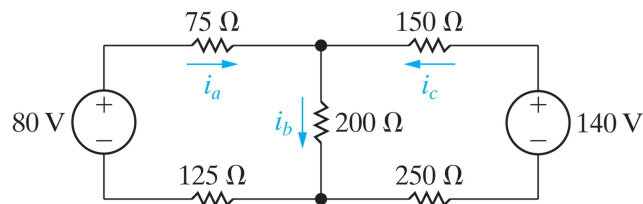Choose the reference point wisely and solve for the currents in the circuit below.




Answer:

$$\begin{aligned}i_a &= 0.1A \\i_b &= 0.3A \\i_c &= 0.2A\end{aligned}$$


Current Sources and the Supermesh

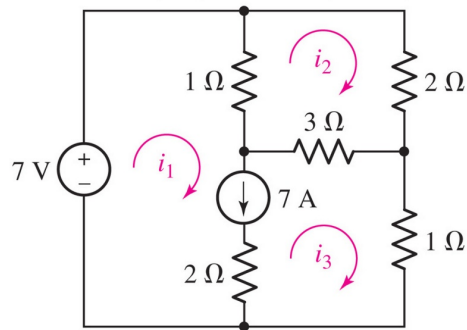If a current source is present in the network and shared between two meshes you must use a *supermesh* formed from the two meshes that have the shared current source.




Supermesh Example

Use mesh analysis to find V_x

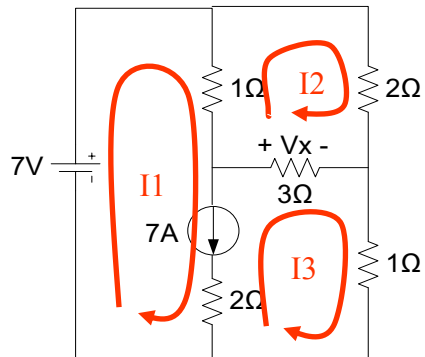


Supermesh Example - continued

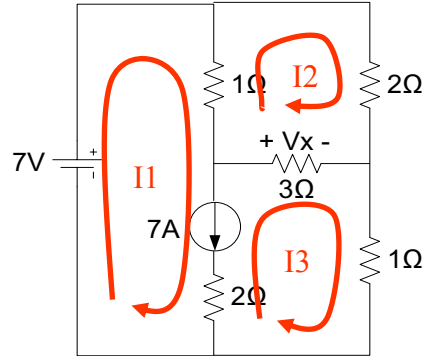

$$\begin{aligned} \text{Loop 2: } 1(I_2 - I_1) + 2I_2 + 3(I_2 - I_3) &= 0 \\ -I_1 + 6I_2 - 3I_3 &= 0 \quad \text{Equation I} \end{aligned}$$


Supermesh Example - continued

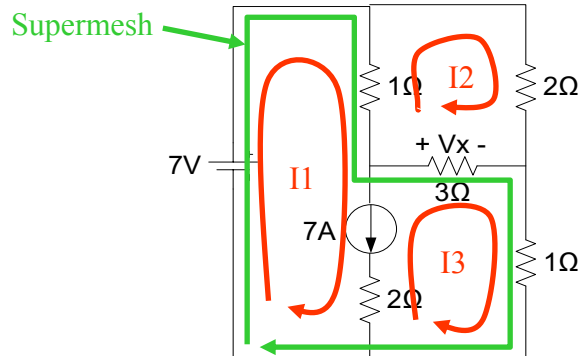

$$\begin{aligned} I_1 &= 9A & -7 + 1(I_1 - I_2) + 3(I_3 - I_2) + I_3 &= 0 \\ I_2 &= 2.5A & I_1 - 4I_2 + 4I_3 &= 7 \quad \text{Equation II} \\ I_3 &= 2A & I_1 - I_3 &= 7 \quad \text{Equation III} \\ V_x &= 3(I_3 - I_2) = -1.5V \end{aligned}$$

Supermesh Example – Zybooks Exercise 3.3.8

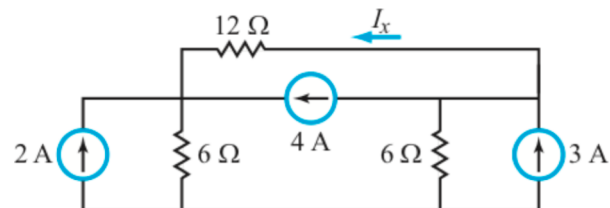(a) Use the supermesh concept to solve for I_x in the circuit below.



$$I_x = -1.75A$$

Section 3.2a and 3.3a Summary

- Learned to identify and apply the super-node and super-mesh analysis methods to analyze an electric circuit.