

Class 8 – April 15 – Sections 3.2-3

Super-Node and Super-Mesh Analysis

1. Announcements
 - a. Replace R4 in lab #2 with a 30k resistor.
 2. Homework due today
 - a. hw7
 3. New homework assigned
 - a. hw8 – Due 4/17
 4. Next class period
 - a. Chapter 3.8 – Thevenin and Norton Equivalent Circuits
-
-

Today's Class Activities

- Q & A
- Sections 3.2 and 3.3 – Super-node and super-mesh analysis
- Q & A