

Class 9 – April 17 – Sections 2.4, 3.8

Source Transformations, Thevenin and Norton Equivalent Circuits

1. Announcements
 - a. Lab #3 has been posted. Note change in deadline for submission.
 2. Homework due today: hw8
 3. New homework assigned: hw9 due 4/20
 4. Next class period: Chapter 3.8 – Thevenin and Norton Equivalent Circuits, Part II
-

Today's Class Activities

- Q & A
- Source Transformations, Thevenin and Norton Equivalent Circuits
- Q & A