


NAME KEY

SCORE _____/30

This is a closed book test except for your calculator and cheat sheet. Each page is worth 10 points. Partial credit may be given but only if you show your work.



- / The ideal input resistance of a multi-meter placed in the current-measuring mode is 0 Ω
- / When writing node equations, all terms are in units of Amps
- .5 How many **total** nodes are in the circuit below? 3
- .5 How many **total** branches are in the circuit below? 6

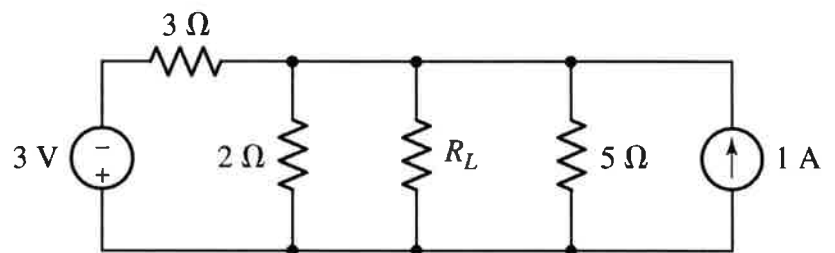- 7 What value of R_L will ensure it absorbs the maximum possible amount of power?



The value of R_L that absorbs the most power will be R_{Th} as seen by R_L .

To find R_{Th} , set all sources = 0

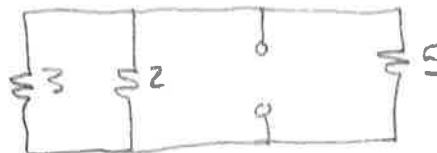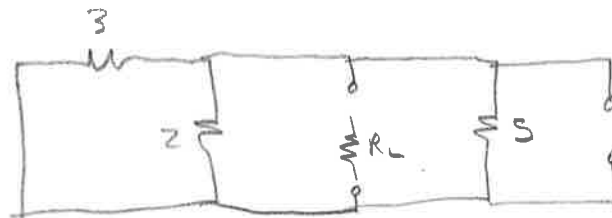


$$R_{Th} = 3 \parallel 2 \parallel 5$$

$$= 0.968 \Omega$$

$R_L \text{ for max power} = 0.968 \Omega$

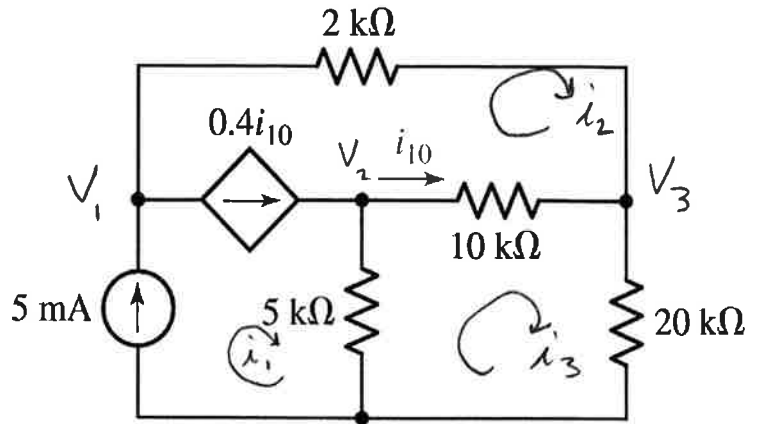Solve for the current labeled i_{10} in the circuit below. Use either mesh or loop analysis.



NODE ANALYSIS

Node V_1 : $5\text{ mA} = 0.4i_{10} + \frac{V_1 - V_3}{2\text{ k}\Omega}$

Node V_2 : $0.4i_{10} = \frac{V_2}{5\text{ k}\Omega} + \frac{V_2 - V_3}{10\text{ k}\Omega}$

Node V_3 : $\frac{V_1 - V_3}{2\text{ k}\Omega} + \frac{V_2 - V_3}{10\text{ k}\Omega} = \frac{V_3}{20\text{ k}\Omega}$

dependent eq: $i_{10} = \frac{V_2 - V_3}{10\text{ k}\Omega}$

Solving: $V_1 = 65.2\text{ V}$
 $V_2 = 12\text{ V}$
 $V_3 = 52\text{ V}$

$i_{10} = -4.0\text{ mA}$

MESH ANALYSIS

Mesh i_1 : $i_1 = 5\text{ mA}$

Mesh i_2 : $0.4i_{10} = i_1 - i_2$

Mesh i_3 : $5\text{ k}\Omega(i_3 - i_1) + 10\text{ k}\Omega(i_3 - i_2) + 20\text{ k}\Omega(i_3) = 0$

$i_{10} = i_3 - i_2$

Solving: $i_1 = 5\text{ mA}$
 $i_2 = 6.6\text{ mA}$
 $i_3 = 2.6\text{ mA}$

$i_{10} = -4.0\text{ mA}$

Solve this problem two ways:

Write the necessary **node** equations and solve for the power dissipated in the 4Ω resistor.

Write the necessary **mesh** equations and solve for the power dissipated in the 4Ω resistor.

Node

$$V_A = 10V$$


$$V_B = 15V$$

$$V_D = 3V$$

Node V_C :
$$\frac{V_A - V_C}{3} = 1 + \frac{V_C}{2} + \frac{V_C - V_D}{4}$$

$$V_C = 2.8462V$$
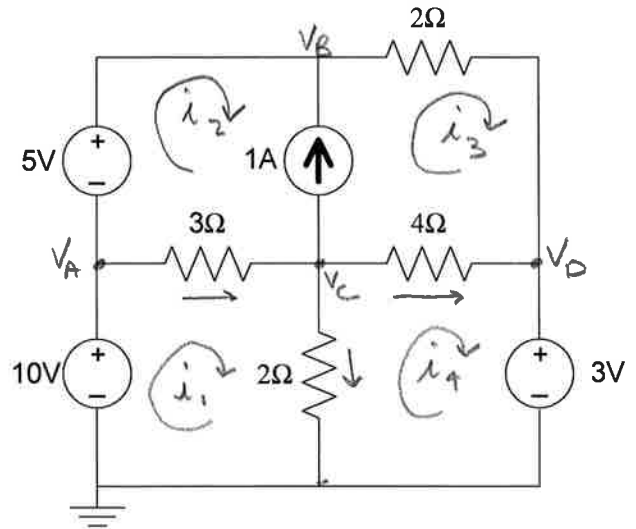
$$P_{4\Omega} = \frac{V^2}{R} = \frac{(V_C - V_D)^2}{4} = \boxed{5.917mW}$$



Mesh

This is a super mesh problem.

$$\text{Mesh } i_1: -10 + 3(i_1 - i_2) + 2(i_1 - i_4) = 0$$

$$i_2, i_3: -5 + 2i_3 + 4(i_3 - i_4) + 3(i_2 - i_1) = 0$$

$$1 = i_3 - i_2$$

$$i_4: 2(i_4 - i_1) + 4(i_4 - i_3) + 3 = 0$$

$$\begin{cases} 5i_1 - 3i_2 - 2i_4 = 10 \\ -3i_1 + 3i_2 + 6i_3 - 4i_4 = 5 \\ -i_2 + i_3 = 1 \\ -2i_1 - 4i_3 + 6i_4 = -3 \end{cases}$$

$$\text{Solving: } i_1 = 7.385A$$

$$i_2 = 5.00A$$

$$i_3 = 6.00A$$

$$i_4 = 5.962A$$


$$P_{4\Omega} = i^2 R = (i_4 - i_3)^2 \cdot 4 = \boxed{5.917mW}$$

NAME _____


SCORE KEY /30

This test is 60 minutes in length and is closed book except for your calculator and one side of a cheat sheet.

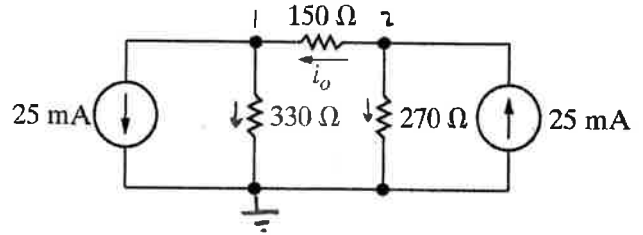6 pts Find i_0 using your method of choice.



1) Source transformations

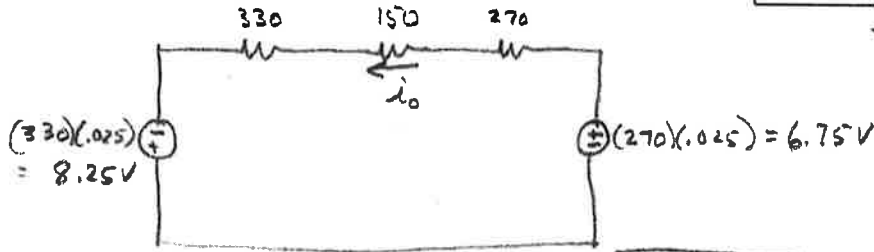

$$i_0 = \frac{V}{R} = \frac{8.25 + 6.75}{330 + 150 + 270} = \boxed{20 \text{ mA} = i_0}$$


2) mesh equations

$$i_1 = 25 \text{ mA}$$

$$i_2 = 25 \text{ mA}$$

$$\text{mesh } i_3: 150i_3 + 330(i_3 - i_1) + 270(i_3 - i_2) = 0$$

$$\boxed{i_3 = i_0 = 20 \text{ mA}}$$

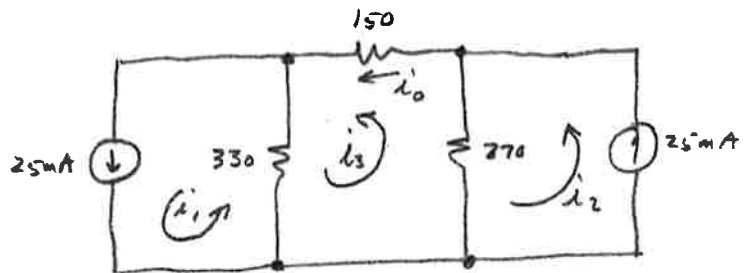


3) Node equations

$$\left. \begin{aligned} \text{Node 1: } \frac{V_2 - V_1}{150} &= 25 \text{ mA} + \frac{V_1}{330} \\ \text{Node 2: } 25 \text{ mA} &= \frac{V_2 - V_1}{150} + \frac{V_2}{270} \end{aligned} \right\} \begin{aligned} V_1 &= -1.65 \text{ V} \\ V_2 &= +1.35 \text{ V} \end{aligned}$$

$$i_0 = \frac{V_2 - V_1}{150} = \underline{\underline{20 \text{ mA}}}$$

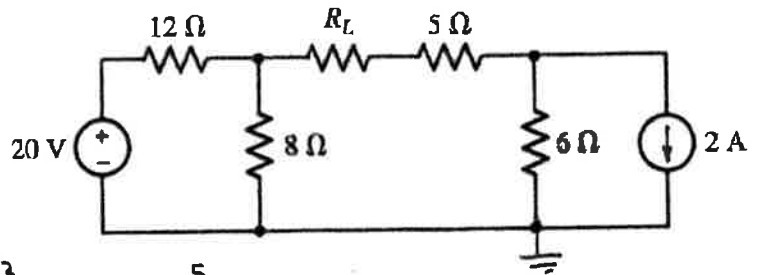
5 pts Find the Thévenin equivalent as seen by R_L



Find R_{Th}

$$R_{Th} = (12 \parallel 8) + 6 + 5$$

$$R_{Th} = 15.8 \Omega$$


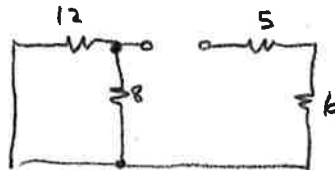


Find V_{Th}

$$V_+ = \frac{20(8)}{12+8} = 8V$$

$$V_- = -(2)(6) = -12V$$

$$V_{Th} = V_+ - (V_-) = 20V$$

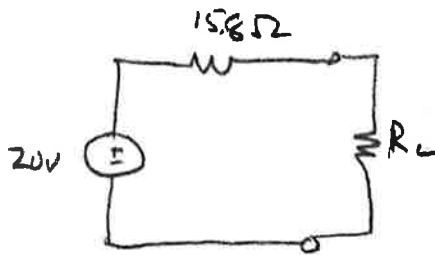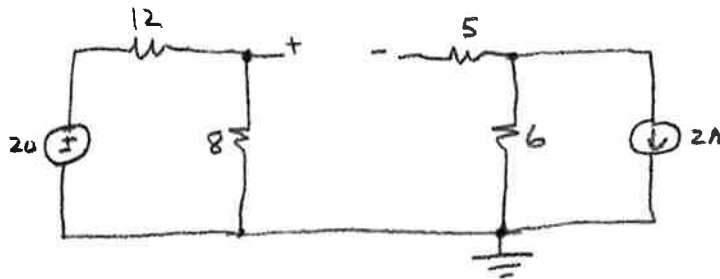

1 pt What value of R_L will dissipate the most power?

$$R_L = R_{Th} = 15.8 \Omega$$

2 pts Find the maximum power dissipated by R_L

$$P = \frac{V_{Th}^2}{4R_L} = \frac{(20)^2}{4(15.8)} = 6.329W$$