

NAME KEY

SCORE _____/30

This test is 60 minutes in length and is closed book except for your calculator and one side of a cheat sheet.

10 pts Phasor Analysis


7 pts Find the current through the 10Ω resistor.
Express your answer in polar form.

Current Divider

$$i_{10\Omega} = \frac{3 \angle 30^\circ (-j5)}{-j5 + j5 + 10}$$

$$= \frac{3 \angle 30^\circ (5 \angle -90^\circ)}{10}$$
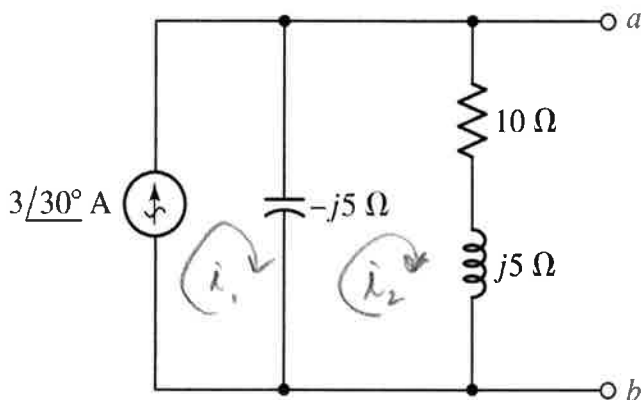
$$i_{10\Omega} = 1.5 \angle -60^\circ \text{ A}$$



mesh

$$i_1 = 3 \angle 30^\circ$$

$$\text{mesh } i_2: -j5(i_2 - i_1) + 10i_2 + j5i_2 = 0$$

$$i_2 = \frac{-15 \angle 30^\circ}{-j5 + j5 + 10} = 1.5 \angle -60^\circ \text{ A}$$

3 pts Find the voltage across the inductor. Express your answer in sinusoidal form.

$$V_{ind} = i_{ind} Z_{ind}$$

$$= (1.5 \angle -60^\circ) (5 \angle 90^\circ)$$

$$= 7.5 \angle 30^\circ \text{ V}$$

$$= 7.5 \cos(\omega t + 30^\circ) \text{ V}$$



10 pts First Order Circuits

- 4 pts The DC current source has been applied for a long time before the switch opens at $t = 0$ seconds. Find $I_L(0)$ i.e. the initial inductor current for $L = 100\text{mH}$.

using current divider;


$$i_L(0) = \frac{30\text{mA}(1\text{K})}{1\text{K} + 9\text{K}}$$

$$i_L(0) = 3\text{mA}$$

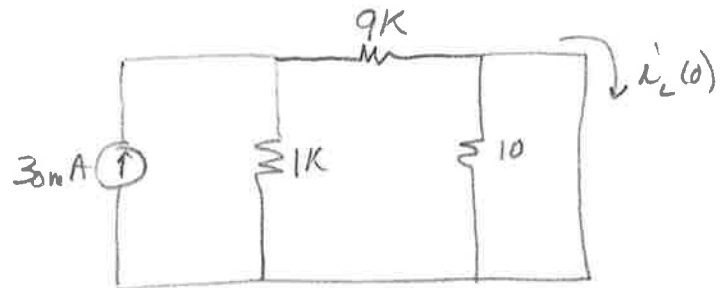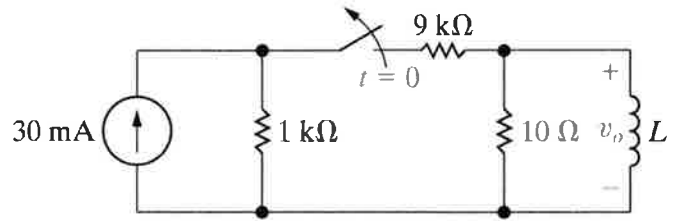

- 2 pts What is the time constant (τ) of this circuit for $t > 0$ seconds?
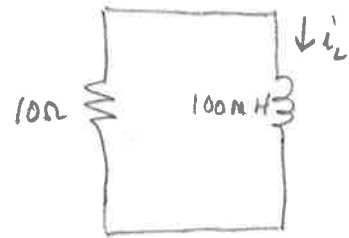
$$\tau = \frac{L}{R} = \frac{1}{10} = 10\text{ms}$$



- 2 pts What is I_L as time goes to infinity, i.e. $I_L(\infty)$?

$$i_L(\infty) = 0\text{ A}$$



- 2 pts Find $I_L(t)$ for $t \geq 0$ seconds

$$i_L(t) = i_L(0) e^{-\frac{t}{\tau}}$$

$$i_L(t) = 3 e^{-100t} \text{ mA} \quad t \geq 0$$

10 pts Second Order Circuits

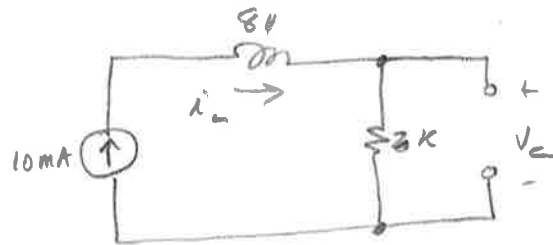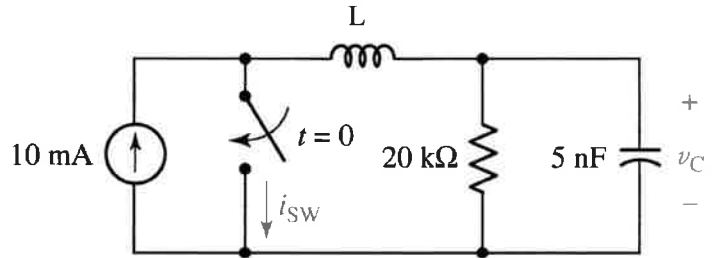The switch in the figure at the right has been open for a long time and closes at $t = 0$ seconds. Obtain an expression for the voltage labeled $v_C(t)$ for $t \geq 0$ seconds. Note that the correct answer has *transient terms only*. Take $L = 8.0$ Henries.



1) FIND I, C.'S

$$i_L(0) = 10 \text{ mA}$$

$$V_C(0) = (10 \text{ mA})(20 \text{ k}) = 200 \text{ V}$$

2) FIND α and ω_0

$$\alpha = \frac{1}{2RC} = 5000 \text{ rad/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 5000 \text{ rad/sec}$$

$\alpha = \omega_0$ so system is critically damped

$$V_C(t) = A_1 t e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5000$$

$$V_C(t) = (A_1 t + A_2) e^{-5000 t}$$

3) FIND A_1 and A_2

@ $t=0$, $V_C = 200 \text{ V} \Rightarrow 200 = A_2$ so $V_C(t) = (A_1 t + 200) e^{-5000 t}$

writing a KCL equation @ $t=0$:

$$i_L + i_R + i_C = 0$$

$$-10 \text{ mA} + \frac{200}{20 \text{ k}} + C \frac{dV_C}{dt} = 0$$

$$-10 \text{ mA} + 10 \text{ mA} + 5 \times 10^{-9} [A_1 t (-5000) e^{-5000 t} + e^{-5000 t} A_1 + 200(-5000) e^{-5000 t}] \Big|_{t=0} = 0$$

$$A_1 + 200(-5000) = 0 \Rightarrow A_1 = 1,000,000$$

$$\therefore V_C(t) = (1,000,000 t + 200) e^{-5000 t} \text{ V}$$