

Digital Logic

Homework #14

DUE: Friday, November 15

Objective

Learn state machine design using alternative architectures.

To Do

- 1) Using RET D flip-flops, design a state machine that counts either up or down (depending on an up/down input) through a 3-bit grey-code sequence:

000 → 001 → 011 → 010 → 110 → 111 → 101 → 100

- 2) Repeat your design using the alternative architectures listed below:
 - A direct addressed mux;
 - An indirect addressed mux.
- 3) In all cases, compute the number of IC's needed to implement the design.

Turn In

- **Staple this assignment sheet** to your solutions, which are to be done in accordance with the school of engineering homework guidelines posted on the course web page.