

# **Chapter 5**

## **Sequential Statements of VHDL**

**Dr. Curt Nelson**  
**Engr433 – Digital Design**

### **Outline**

VHDL process;  
Sequential signal assignment statement;  
Variable assignment statement;  
IF statement;  
CASE statement;  
Simple FOR loop statement.

## VHDL Process

- Contains a set of statements to be executed sequentially.
- The whole process is a concurrent statement.
- Can be interpreted as a circuit part enclosed in a black box.
- May or may not be able to be mapped to physical hardware.
- Two types of process
  - A process with a sensitivity list.
  - A process with a wait statement.

## A Process With a Sensitivity List

- Syntax

```
process(sensitivity_list)
  declarations;
begin
  sequential statement;
  sequential statement;
  ...
end process;
```

## VHDL Process Description

- A process is like a circuit part, which can be
  - active (known as *activated*);
  - inactive (known as *suspended*).
- A process is activated when a signal in the sensitivity list changes its value.
- Its statements will be executed sequentially until the end of the process.

## Example: 3-Input AND Circuit

```
signal a,b,c,y: std_logic;  
process(a,b,c)  
begin  
    y <= a and b and c;  
end process;
```

- The following code is lame

```
process(a)  
begin  
    y <= a and b and c;  
end process;
```
- For a combinational circuit, all inputs should be included in the sensitivity list.

## Process With a Wait Statement

- Process has no sensitivity list.
- Process continues execution until a wait statement is reached and then suspended.
- Forms of wait statement
  - **wait on** signals;
  - **wait until** boolean\_expression;
  - **wait for** time\_expression;

## Wait Statement Example

- 3-input AND circuit

```
process
begin
  y <= a and b and c;
  wait on a, b, c;
end process;
```
- A process can have multiple wait statements.
- A Process with a sensitivity list is preferred for synthesis.

## Sequential Signal Assignment Statement

- Syntax  
    `signal_name <= value_expression;`
- Syntax is identical to the simple concurrent signal assignment.
- Caution
  - Inside a process, a signal can be assigned multiple times, but only the last assignment takes effect.

## Sequential Signal Assignment Example

```
process(a,b,c,d)
begin
    y <= a or c;
    y <= a and b;
    y <= c and d;
end process;
```

- Same as  


```
process(a,b,c,d)
begin
    y <= c and d;
end process;
```
- What happens if the 3 statements are concurrent statements?
  - Wired AND function.

## Variable Assignment Statement

- Syntax  
variable\_name := value\_expression;
- Assignment takes effect immediately.
- No time dimension (i.e., no delay).
- Behaves like variables in C.
- Difficult to map to hardware, but depends on the context.
 
## Variable Assignment Interpretation

```
process(a,b,c)  
  variable tmp0, tmp1, tmp2: std_logic;  
begin  
  tmp0 := '0';  
  tmp1 := tmp0 or a;  
  tmp2 := tmp1 or b;  
  y <= tmp2;  
end process;
```



## What Happens if Signal is Used?

```
process(a,b,c,tmp)
begin          -- tmpentry := tmp
  tmp <= '0';   -- tmpexit := '0';
  tmp <= tmp or a; -- tmpexit := tmpentry or a;
  tmp <= tmp or b; -- tmpexit := tmpentry or b;
end process;   -- tmp <= tmpexit
```

- Same as

```
process(a,b,c,tmp)
begin
  tmp <= tmp or b;
end process;
```

## IF Statement Syntax

```
if boolean_expr_1 then
  sequential_statements;
elsif boolean_expr_2 then
  sequential_statements;
elsif boolean_expr_3 then
  sequential_statements;
...
else
  sequential_statements;
end if;
```

## IF Statement Example

```

architecture if_arch of mux4 is
begin
  process (a,b,c,d,s)
  begin
    if (s="00") then
      x <= a;
    elsif (s="01") then
      x <= b;
    elsif (s="10") then
      x <= c;
    else
      x <= d;
    end if;
  end process;
end if_arch;

```

input	output
s	x
0 0	a
0 1	b
1 0	c
1 1	d

## Binary Decoder Example

```

architecture if_arch of decoder4 is
begin
  process (s)
  begin
    if (s="00") then
      x <= "0001";
    elsif (s="01") then
      x <= "0010";
    elsif (s="10") then
      x <= "0100";
    else
      x <= "1000";
    end if;
  end process;
end if_arch;

```

input	output
s	x
0 0	0001
0 1	0010
1 0	0100
1 1	1000



## 4-to-2 Priority Encoder Example

```
architecture if_arch of prio_encoder42 is
begin
  process (r)
  begin
    if (r(3)='1') then
      code <= "11";
    elsif (r(2)='1') then
      code <= "10";
    elsif (r(1)='1') then
      code <= "01";
    else
      code <= "00";
    end if;
  end process;
  active <= r(3) or r(2) or r(1) or r(0);
end if_arch;
```

input	output	
r	code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

## Sequential Statement Example

```
sig <= value_expr_1 when boolean_expr_1 else
      value_expr_2 when boolean_expr_2 else
      value_expr_3 when boolean_expr_3 else
      . . .
      value_expr_n;
```

It can be written as

```
process (...)
  if boolean_expr_1 then
    sig <= value_expr_1;
  elsif boolean_expr_2 then
    sig <= value_expr_2;
  elsif boolean_expr_3 then
    sig <= value_expr_3;
  . . .
  else
    sig <= value_expr_n;
  end if;
end process
```

## Sequential Statement Example

Find the max of a, b, c

```
if (a > b) then
  if (a > c) then
    max <= a;  -- a>b and a>c
  else
    max <= c;  -- a>b and c>=a
  end if;
else
  if (b > c) then
    max <= b;  -- b>=a and b>c
  else
    max <= c;  -- b>=a and c>=b
  end if;
end if;
```

## Two Conditional Signal Assignment Codes

```
signal ac_max, bc_max: std_logic;
. . .
ac_max <= a when (a > c) else c;
bc_max <= b when (b > c) else c;
max <= ac_max when (a > b) else bc_max;

max <= a when ((a > b) and (a > c)) else
  c when (a > b) else
  b when (b > c) else
  c;
```

## Incomplete Branch and Signal Assignment

- According to VHDL definition
  - Only the “then” branch is required; “elsif” and “else” branches are optional.
  - Signals do not need to be assigned in all branches.
  - When a signal is unassigned due to omission, it keeps the “previous value” (implying “memory”).

## Incomplete Branch Example

```
process (a, b)
begin
    if (a=b) then
        eq <= '1';
    end if ;
end process ;
```

Implies:

```
process (a, b)
begin
    if (a=b) then
        eq <= '1';
    else
        eq <= eq;
    end if ;
end process
```

## Incomplete Branch Example Fix

```
process (a,b)
begin
    if (a=b) then
        eq <= '1';
    else
        eq <= '0';
    end if ;
end process
```

## Incomplete Signal Assignment

```
process (a,b)
begin
    if (a>b) then
        gt <= '1';
    elsif (a=b) then
        eq <= '1';
    else
        lt <= '1';
    end if;
end process;
```

## Incomplete Signal Assignment Fixes

```
process (a, b)
begin
  if (a>b) then
    gt <= '1';
    eq <= '0';
    lt <= '0';
  elsif (a=b) then
    gt <= '0';
    eq <= '1';
    lt <= '0';
  else
    gt <= '0';
    eq <= '0';
    lt <= '1';
  end if;
end process;
```


```
process (a, b)
begin
  gt <= '0';
  eq <= '0';
  lt <= '0';
  if (a>b) then
    gt <= '1';
  elsif (a=b) then
    eq <= '1';
  else
    lt <= '1';
  end if;
end process;
```

## Conceptual Implementation

- Same as the conditional signal assignment statement if the IF statement consists of
  - One output signal.
  - One sequential signal assignment in each branch.
- Multiple sequential statements can be constructed recursively.
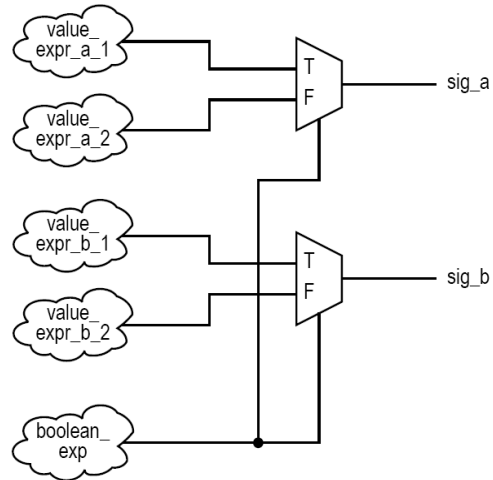
## Example


```
if boolean_expr then
  sig_a <= value_expr_a_1;
  sig_b <= value_expr_b_1
else
  sig_a <= value_expr_a_2;
  sig_b <= value_expr_b_2;
end if;
```



## Example Code

```
if boolean_expr_1 then
  if boolean_expr_2 then
    signal_a <= value_expr_1;
  else
    signal_a <= value_expr_2;
  end if;
else
  if boolean_expr_3 then
    signal_a <= value_expr_3;
  else
    signal_a <= value_expr_4;
  end if;
end if;
```

## Conceptual Implementation

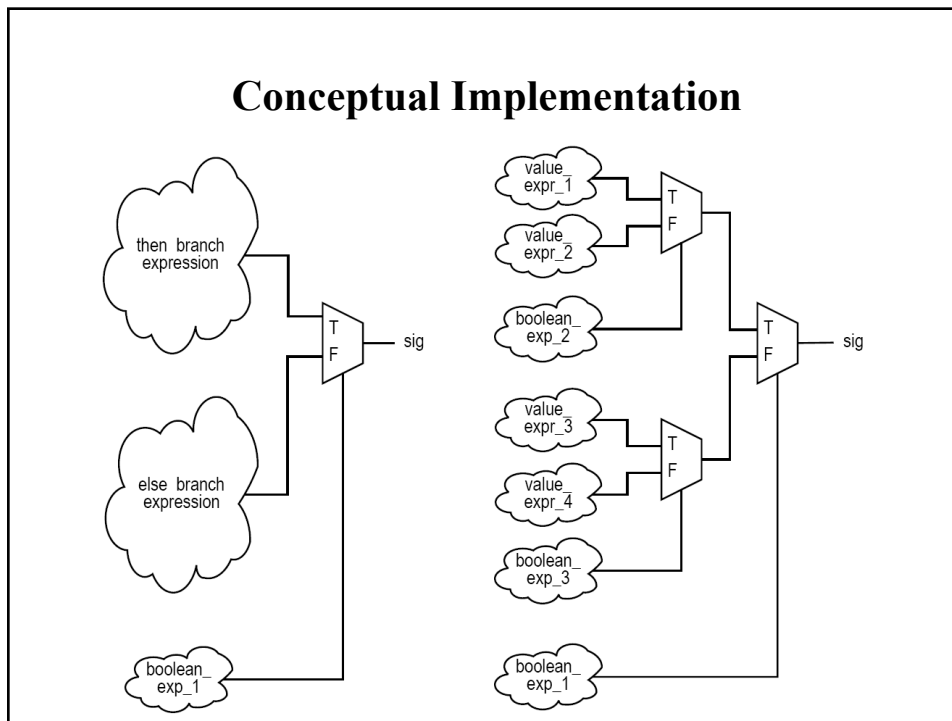

## Case Statement

- Syntax;
- Examples;
- Comparison to selected signal assignment statement;
- Incomplete signal assignment;
- Conceptual implementation.

## Case Statement Syntax

```
case case_expression is
  when choice_1 =>
    sequential statements;
  when choice_2 =>
    sequential statements;
  ...
  when choice_n =>
    sequential statements;
end case;
```

## Example: 4-to-1 Mux

```
architecture case_arch of mux4 is
begin
  process (a,b,c,d,s)
  begin
    case s is
      when "00" =>
        x <= a;
      when "01" =>
        x <= b;
      when "10" =>
        x <= c;
      when others =>
        x <= d;
    end case;
  end process;
end case_arch;
```

input	output
s	x
00	a
01	b
10	c
11	d



## Example: 2-to-2<sup>2</sup> Binary Decoder

```

architecture case_arch of decoder4 is
begin
  proc1:
  process (s)
  begin
    case s is
      when "00" =>
        x <= "0001";
      when "01" =>
        x <= "0010";
      when "10" =>
        x <= "0100";
      when others =>
        x <= "1000";
    end case;
  end process;
END case_arch;

```

input s	output x
0 0	0001
0 1	0010
1 0	0100
1 1	1000

## Example: 4-to-2 Priority Encoder

```

architecture case_arch of prio_encoder42 is
begin
  process (r)
  begin
    case r is
      when "1000"|"1001"|"1010"|"1011"|
           "1100"|"1101"|"1110"|"1111" =>
        code <= "11";
      when "0100"|"0101"|"0110"|"0111" =>
        code <= "10";
      when "0010"|"0011" =>
        code <= "01";
      when others =>
        code <= "00";
    end case;
  end process;
  active <= r(3) or r(2) or r(1) or r(0);
end case_arch;

```

input r	output code	output active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

## Comparison to Selected Signal Assignment

- Two statements are the same if there is only one output signal in case statement.
- Case statement is more flexible.
- Sequential statements can be used in choice branches.

## Example

```
with sel_exp select
  sig <= value_expr_1 when choice_1,
        value_expr_2 when choice_2,
        value_expr_3 when choice_3,
        . . .
        value_expr_n when choice_n;
```

It can be rewritten as:

```
case sel_exp is
  when choice_1 =>
    sig <= value_expr_1;
  when choice_2 =>
    sig <= value_expr_2;
  when choice_3 =>
    sig <= value_expr_3;
  . . .
  when choice_n =>
    sig <= value_expr_n;
end case;
```

## Incomplete Signal Assignment

- According to VHDL definition
  - Signals do not need to be assigned in all choice branch.
  - When a signal is unassigned, it keeps the “previous value” (implying “memory”).

## Incomplete Signal Assignment

```
process (a)
  case a is
    when "100"|"101"|"110"|"111" =>
      high <= '1';
    when "010"|"011" =>
      middle <= '1';
    when others =>
      low <= '1';
  end case;
end process;
```

## Incomplete Signal Assignment – Fix #1

```
process(a)
  case a is
    when "100"|"101"|"110"|"111" =>
      high <= '1';
      middle <= '0';
      low <= '0';
    when "010"|"011" =>
      high <= '0';
      middle <= '1';
      low <= '0';
    when others =>
      high <= '0';
      middle <= '0';
      low <= '1';
  end case;
end process;
```

## Incomplete Signal Assignment – Fix #2

```
process(a)
  high <= '0';
  middle <= '0';
  low <= '0';
  case a is
    when "100"|"101"|"110"|"111" =>
      high <= '1';
    when "010"|"011" =>
      middle <= '1';
    when others =>
      low <= '1';
  end case;
end process;
```


## Conceptual Implementation

- Same as selected signal assignment statement if the case statement consists of
  - One output signal.
  - One sequential signal assignment in each branch.
- Multiple sequential statements can be constructed recursively.

## Conceptual Implementation - Example

```
case case_exp is
  when c0 =>
    sig_a <= value_expr_a_0;
    sig_b <= value_expr_b_0;
  when c1 =>
    sig_a <= value_expr_a_1;
    sig_b <= value_expr_b_1;
  when others =>
    sig_a <= value_expr_a_n;
    sig_b <= value_expr_b_n;
end case;
```

## Conceptual Implementation - Example

 

## Simple For Loop Statement

- VHDL provides a variety of loop constructs.
- Only a restricted form of loop can be synthesized.
- Syntax of simple for loop  
**for** index **in** loop\_range **loop**  
    sequential statements;  
**end loop;**
- loop\_range must be static.
- Index assumes value of loop\_range from left to right.

## For Loop Example – Bit-wide XOR

```
library ieee;
use ieee.std_logic_1164.all;

entity wide_xor is
  port(
    a, b: in std_logic_vector(3 downto 0);
    y: out std_logic_vector(3 downto 0)
  );
end wide_xor;

architecture demo_arch of wide_xor is
  constant WIDTH: integer := 4;
begin
  process(a, b)
  begin
    for i in (WIDTH-1) downto 0 loop
      y(i) <= a(i) xor b(i);
    end loop;
  end process;
end demo_arch;
```

## For Loop Example – Reduced XOR

```
library ieee;
use ieee.std_logic_1164.all;

entity reduced_xor_demo is
  port(
    a: in std_logic_vector(3 downto 0);
    y: out std_logic
  );
end reduced_xor_demo;

architecture demo_arch of reduced_xor_demo is
  constant WIDTH: integer := 4;
  signal tmp: std_logic_vector(WIDTH-1 downto 0);
begin
  process(a, tmp)
  begin
    tmp(0) <= a(0); -- boundary bit
    for i in 1 to (WIDTH-1) loop
      tmp(i) <= a(i) xor tmp(i-1);
    end loop;
  end process;
  y <= tmp(WIDTH-1);
end demo_arch;
```

## Conceptual Implementation

- “Unroll” the loop.
- For loop should be treated as “shorthand” for repetitive statements.
- E.g., bit-wise xor

```
y(3)  <= a(3)  xor b(3);  
y(2)  <= a(2)  xor b(2);  
y(1)  <= a(1)  xor b(1);  
y(0)  <= a(0)  xor b(0);
```

## Reduced XOR Example

```
tmp(0) <= a(0);  
tmp(1) <= a(1) xor tmp(0);  
tmp(2) <= a(2) xor tmp(1);  
tmp(3) <= a(3) xor tmp(2);  
y <= tmp(3);
```



## Synthesis of Sequential Statements

- Concurrent statements
  - Modeled after hardware.
  - Have clear, direct mapping to physical structures.
- Sequential statements
  - Intended to describe “behavior”.
  - Flexible and versatile.
  - Can be difficult to be realized in hardware.
  - Can be easily abused.

## Conclusion

- **Think hardware!!**
- Designing hardware is not converting a C program to a VHDL program.