

Engr433: Digital Design

Review of Combinational Circuits

Dr. Curt Nelson

Combinational Review Topics

- Number Systems
 - Bases
 - Decimal
 - Binary
 - Hexadecimal
 - Conversions
 - Decimal \iff Binary
 - Decimal \iff Hexadecimal
 - Binary \iff Hexadecimal
- Basic gates
 - Inverters, And, Nand, Or, Nor, Xor, Xnor

Combinational Review Topics - Continued


- Boolean Algebra
 - Basic Laws
 - De'Morgans Theorems
- Truth Tables
 - Minterms, Sum of Products
 - Maxterms, Product of Sums
- Karnaugh Maps
 - Sum of Products - Minterms
 - Product of Sums - Maxterms
 - Minimization
 - Don't Cares
 - Entered Variable Mapping (EVM)

Combinational Review Topics - Continued


- Medium and Large Scale Integration (MSI and LSI)
 - Arithmetic: Adders / Subtractors
 - Data Format Converters: Encoders / Decoders
 - Data Selectors: Multiplexers/Demultiplexers
 - Other functions

Digital Abstraction

 - Why do we use abstraction in the digital arena?
 - To manage complexity.






(b) Graphic symbol

 

(c) Logic circuit

Digital Abstraction

   

Truth Tables

- All combinations of inputs on the left;
- Outputs on the right;
- 2-input **AND** and **OR** functions shown below.

x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND OR


Truth Table Proof of DeMorgan's Theorem

$$\overline{x \cdot y} = \bar{x} + \bar{y} \quad \text{DeMorgan's Theorem}$$


x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

}	}
LHS	RHS

 DeMorgan's Theorems in Terms of Logic Gates



 
$$(a) \overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$$




$$(b) \overline{\bar{x}_1 + \bar{x}_2} = x_1 x_2$$

- Function vs. Gate


SOP Implementation Using NAND Gates

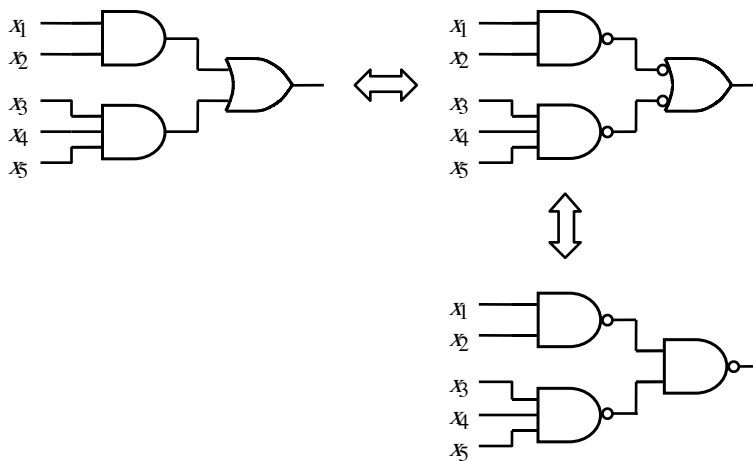

POS Implementation Using NOR Gates

 

Timing Diagram

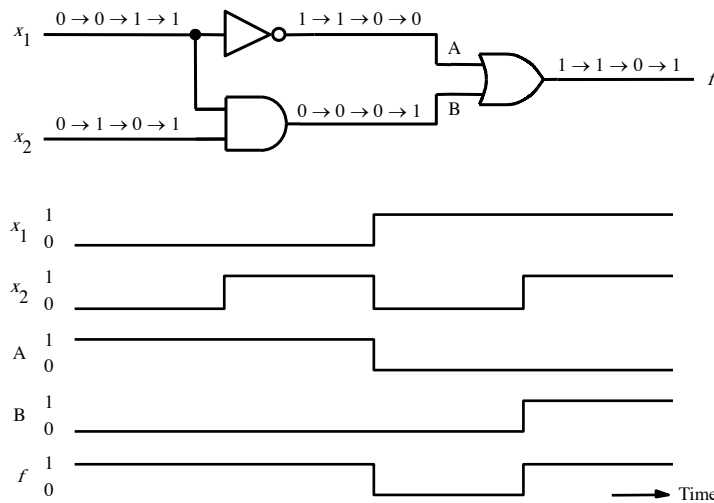

Logic Synthesis


- *Logic synthesis, or logic optimization, is the process of translating a truth table, schematic, or VHDL code into a network of logic gates.*

- Example:

- Minterm form;
- Maxterm form;
- Minimum form.


x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

SOP Implementation – NAND Gates

 

(a) Sum-of-products realization


POS Implementation – NOR Gates

 


(b) Product-of-sums realization

Minimal Implementation

4-Variable Karnaugh Map (Kmap)

 

4-Variable Kmap Example

 

Four-variable function $f = \sum m(2, 3, 5, 6, 7, 10, 11, 13, 14)$

4-Variable Function with Don't Cares

<i>cd</i> \ <i>ab</i>	00	01	11	10
00	0	1	d	0
01	0	1	d	0
11	0	0	d	0
10	1	1	d	1

$$f = \sum m(2, 4, 5, 6, 10) + d(12, 13, 14, 15)$$

Entered Variable (EV) Mapping

- Sometimes called Map Entered Variables (MEV's);
- Allows many variables to be presented using a reduced size K-map;
- Occurs quite frequently in digital systems, especially state machines;
- May require K-map **compression** and **expansion**;
- References (entered-variable mapping or map-entered variables):
 - Tinder, Engineering Digital Design, Second Edition (Library);
 - Other digital logic textbooks;
 - Web – YouTube, etc.

Entered Variable (EV) Mapping Example

a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$f = \sum m(2, 5, 6, 7)$$

$c \backslash ab$	00	01	11	10
0	0	1	1	0
1	0	0	1	1

$$\begin{aligned} f &= a'bc' + ab'c + abc' + abc \\ &= bc' + ac \end{aligned}$$


Entered Variable Truth Table Compression

a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

a	b	f
0	0	0
0	1	c'
1	0	c
1	1	1


Entered Variable Map Compression

 

$$f = a'bc' + ab'c + abc' + abc$$

$$= bc' + ac$$

Three Variable Compression Example

 

$$1 = c + c'$$

$$0 = cc'$$

Four Variable Compression Example

$cd \backslash ab$	00	01	11	10
00	1	1		
01		1	1	
11			1	1
10	1			1

The function $f = \sum m(0, 2, 4, 5, 10, 11, 13, 15)$


$c \backslash ab$	00	01	11	10
0	d'	1	d	0
1	d'	0	d	1

$b \backslash a$	0	1
0	$c'd'+cd' = d'$	$c'0+c1 = c$
1	$c'1+c0 = c'$	$c'd+cd=d$

Other Examples

- Expansion;
- Compression and expansion using don't cares.


MSI Circuits – Half Adder

 


(a) The four possible cases

x	y	Cary	Sum
		c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 

(c) Circuit

 

(d) Graphical symbol

MSI Circuits – Full Adder

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table


c_i	$x_i y_i$	00	01	11	10
0			1		1
1		1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

c_i	$x_i y_i$	00	01	11	10
0				1	
1		1	1	1	1


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 


(c) Circuit

N-bit Ripple Carry Adder

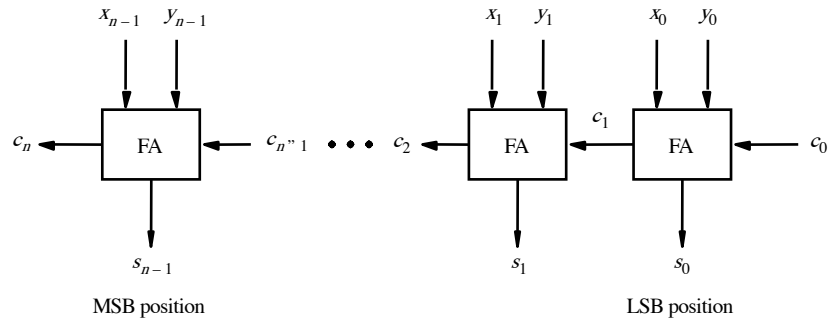


- Major issue – propagation delay.

Faster Adders – Carry Lookahead

 


Adder / Subtractor Circuit

 

Multiplexers

 - Devices that select one of many inputs to be routed to one output based on the binary value of select lines
 - Enable – used to enable or disable the complete function;
 - Select – used to select which one of the inputs gets routed to the output.




Synthesis of Logic Functions Using Mux's

- Mux's can be used to synthesize logic functions as follows:
 - Create truth table;
 - Compress as necessary;
 - Implement.
- In general, an N variable function can be implemented with one $N-1$ multiplexer and at most, one inverter.

Example: 3-Input Majority Function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


(a) Truth table

 

 (b) Circuit


De-Multiplexers

- A de-multiplexer is a circuit which places the value of a single data input onto one of a number of outputs.



An n -to- 2^n Decoder

 
- A decoder is a device that activates one output based on the binary value of the inputs;
- A decoder is a minterm generator;
- Enable – used to enable or disable the complete decoder function.




A 2-to-4 Decoder

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphic symbol

 

 
(c) Logic circuit

A 2^n -to- n Binary Encoder

- An encoder is a device that outputs a binary code representing which one of many inputs is active.
- Priority encoder – assigns priority to certain inputs
 - Used in embedded computer systems to service interrupts.



BCD to 7-segment Code Converter

 


(a) Code converter

(b) 7-segment display

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(c) Truth table

A Four-bit Magnitude Comparator

 

Arithmetic Logic Units (74HC381)

Operation	Inputs	Outputs
	s_2 s_1 s_0	F
Clear	0 0 0	0 0 0 0
$B=A$	0 0 1	$B=A$
$A=B$	0 1 0	$A=B$
ADD	0 1 1	$A+B$
XOR	1 0 0	$A \text{ XOR } B$
OR	1 0 1	$A \text{ OR } B$
AND	1 1 0	$A \text{ AND } B$
Preset	1 1 1	1 1 1 1