

Engr433 : Digital Design

Registers and Counters

Curtis Nelson


Overview

- In this presentation we cover:
 - Registers, which store multiple bits;
 - Shift registers, which shift the contents of registers;
 - Counters of various types.


Review - Sequential Circuits

- **Combinational** – outputs depends only on the inputs;
- **Sequential** – output depends on input and past behavior:
 - Requires use of storage elements;
 - Content of the storage elements is called *state*;
 - Circuit goes through a sequence of states as a result of changes in inputs.
- **Synchronous** – Controlled by a clock;
- **Asynchronous** – No central clock.


Latches and Flip-Flops

 

Multibit Registers and Latches

 


74x374 8-bit Register

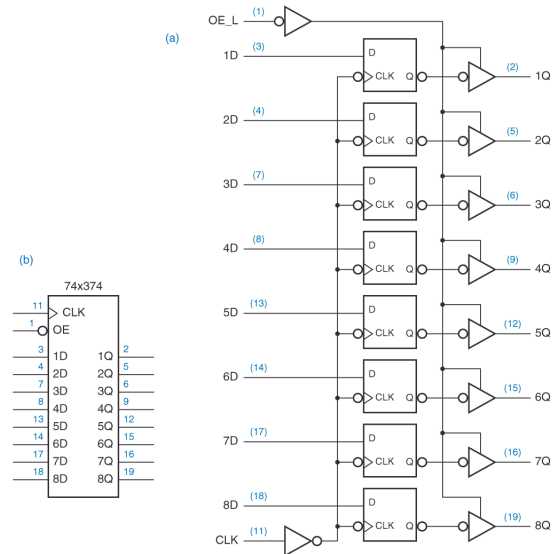


Shift Registers

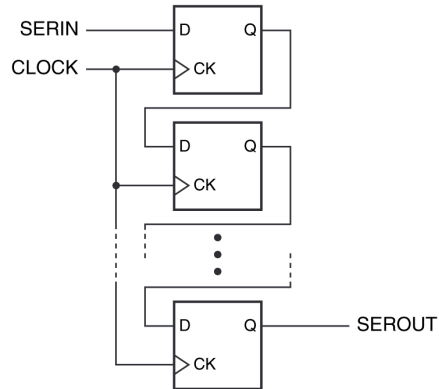- A *shift register* is an n-bit register with a provision for shifting stored data by one bit position at each tick of the clock.



 Shift Registers – Serial-in, Parallel-out



74x194 4-bit Universal Shift Register

| Function | Inputs | | Next state | | | |
|-------------|--------|----|------------|-----|-----|-----|
| | S1 | S0 | QA* | QB* | QC* | QD* |
| Hold | 0 | 0 | QA | QB | QC | QD |
| Shift right | 0 | 1 | RIN | QA | QB | QC |
| Shift left | 1 | 0 | QB | QC | QD | LIN |
| Load | 1 | 1 | A | B | C | D |

Table 8-24

Function table for the 74x194 4-bit universal shift register.

74x194 4-bit Universal Shift Register

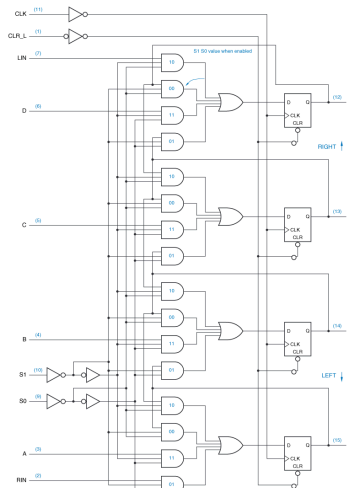


Figure 8-41

Logic diagram for the 74x194 4-bit universal shift register, including pin numbers for a standard 16-pin dual in-line package.

74x194 4-bit Universal Shift Register

 


Figure 8-42

Simplest design for a 4-bit, 4-state ring counter with a single circulating 1.

74x194 4-bit Universal Shift Register


 


Figure 8-43

Timing diagram for a 4-bit ring counter.

Counters

- *Counter* – generally used for any clocked sequential circuit whose state diagram contains a single cycle;
- *Modulus* – the number of states in the cycle;
- A counter with m states is called a *modulus- m* counter or a *divide-by- m* counter;
- *Ripple* counters (rare due to delays);
- *Synchronous* counters (common):
 - Connects all of its flip-flop clock inputs to the same common *CLK* signal so that all flip-flop outputs change at the same time.

 

Synchronous 4-bit Binary Counter – 74x163

 


Figure 8-27
Traditional logic symbol for the 74x163.

| Inputs | | | | Current State | | | | Next State | | | |
|--------|----|-----|-----|---------------|----|----|----|------------|-----|-----|-----|
| CLR | LD | ENT | ENP | QD | QC | QB | QA | QD* | QC* | QB* | QA* |
| 0 | x | x | x | x | x | x | x | 0 | 0 | 0 | 0 |
| 1 | 0 | x | x | x | x | x | x | D | C | B | A |
| 1 | 1 | 0 | x | x | x | x | x | QD | QC | QB | QA |
| 1 | 1 | x | 0 | x | x | x | x | QD | QC | QB | QA |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

Table 8-13
State table for a 74x163 4-bit binary counter.

Synchronous 4-bit Binary Counter – 74x163

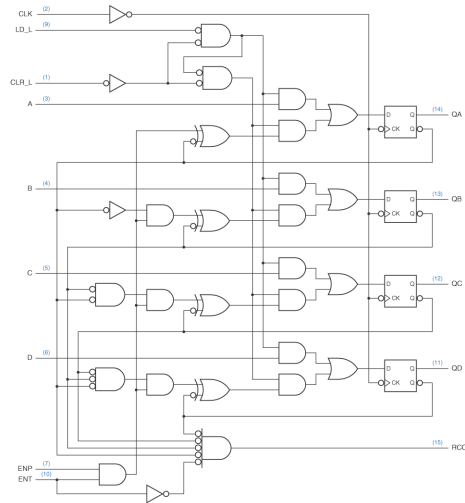


Figure 8-28

Logic diagram for the 74x163 synchronous 4-bit binary counter, including pin numbers for a standard 16-pin DIP package.

Synchronous 4-bit Binary Counter – 74x163

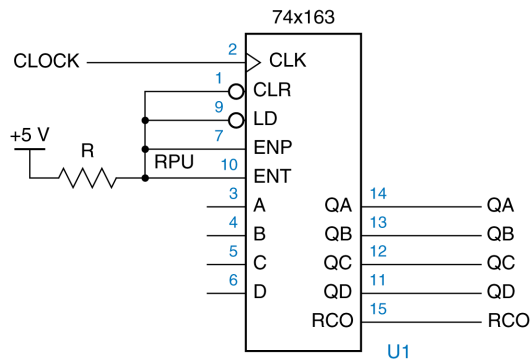


Figure 8-29

Connections for the 74x163 to operate in a free-running mode.

Synchronous 4-bit Binary Counter – 74x169



 


Figure 8-32
Logic symbol for the 74x169 up/down counter.

Ring Counter

 


(a) An n -bit ring counter

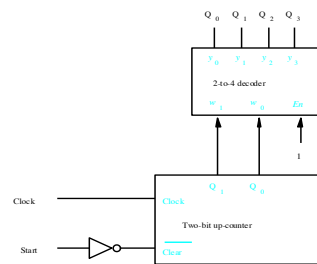


(b) A four-bit ring counter


Johnson Counter

 

Three-Bit Up-Counter

 


(a) Circuit

 


(b) Timing diagram

Three-bit Down-Counter

 


(a) Circuit

 


(b) Timing diagram

Four-bit Synchronous Up-Counter

 


(a) Circuit

 


(b) Timing diagram


Inclusion of Enable and Clear Capability

 

Modulo-6 Counter with Synchronous Reset

 


(a) Circuit

 


(b) Timing diagram

Modulo-6 Counter with Asynchronous Reset

 


(a) Circuit

 

(b) Timing diagram

A Two-digit BCD Counter

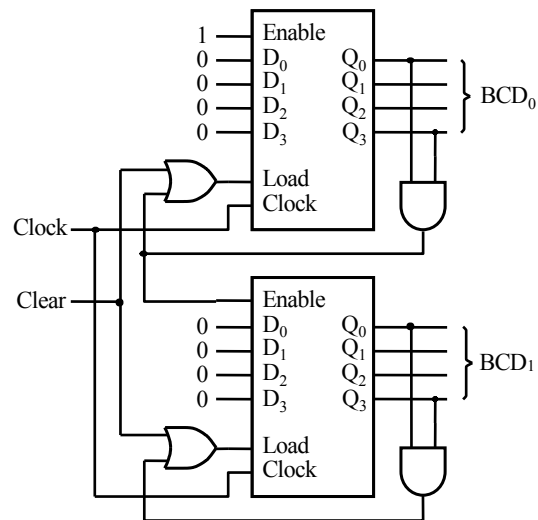

Summary

- In this presentation we covered:
 - Registers, which store multiple bits;
 - Shift registers, which shifts the contents of registers;
 - Counters of various types.