

VHDL Style Observations

Dr. Curt Nelson
Engr433 – Digital Design

Counter Design – Version 1

```
entity dec_counter is
  Port ( mclk : in  STD_LOGIC;
        en   : in  STD_LOGIC;
        ce_out : out STD_LOGIC);
end dec_counter;

architecture Behavioral of dec_counter is
  signal r_reg: unsigned(3 downto 0);
  signal r_next: unsigned(3 downto 0);
begin
  process(mclk,en,r_reg)
  begin
    if (mclk'event and mclk='1') then
      if (en = '1') then
        if (r_reg = "1001") then
          r_reg <= "0000";
          ce_out <= '1';
        else
          r_reg <= r_next;
          ce_out <= '0';
        end if;
      end if;
    end if;
  end process;
  r_next <= r_reg + 1;
end Behavioral;
```

Version 1 – FPGA Utilization

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	5	4,896	1%	
Number of 4 input LUTs	5	4,896	1%	
Number of occupied Slices	3	2,448	1%	
Number of Slices containing only related logic	3	3	100%	
Number of Slices containing unrelated logic	0	3	0%	
Total Number of 4 input LUTs	5	4,896	1%	
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	3.25			

Version Comparisons

Version 1

```
architecture Behavioral of dec_counter is
  signal r_reg: unsigned(3 downto 0);
  signal r_next: unsigned(3 downto 0);
begin
  process(mclk,en,r_reg)
  begin
    if (mclk'event and mclk='1') then
      if (en = '1') then
        if (r_reg = "1001") then
          r_reg <= "0000";
          ce_out <= '1';
        else
          r_reg <= r_next;
          ce_out <= '0';
        end if;
      end if;
    end if;
  end process;
  r_next <= r_reg + 1;
end Behavioral;
```

Version 2

```
architecture Behavioral of dec_counter_ver2 is
  signal r_reg: unsigned(3 downto 0);
  signal r_next: unsigned(3 downto 0);
begin
  process(mclk,en)
  begin
    if (mclk'event and mclk='1') then
      if (en = '1') then
        if (r_reg = "1001") then
          r_reg <= "0000";
        else
          r_reg <= r_next;
        end if;
      end if;
    end process;
    r_next <= r_reg + 1;
    ce_out <= '1' when r_reg = "1001" else '0';
  end Behavioral;
```

FPGA Utilization Comparisons


Version 1

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	5	4,896	1%	
Number of 4 input LUTs	5	4,896	1%	
Number of occupied Slices	3	2,448	1%	
Number of Slices containing only related logic	3	3	100%	
Number of Slices containing unrelated logic	0	3	0%	
Total Number of 4 input LUTs	5	4,896	1%	
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	3.25			


Version 2

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	4	4,896	1%	
Number of 4 input LUTs	5	4,896	1%	
Number of occupied Slices	3	2,448	1%	
Number of Slices containing only related logic	3	3	100%	
Number of Slices containing unrelated logic	0	3	0%	
Total Number of 4 input LUTs	5	4,896	1%	
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	3.57			


RTL View – Version 1

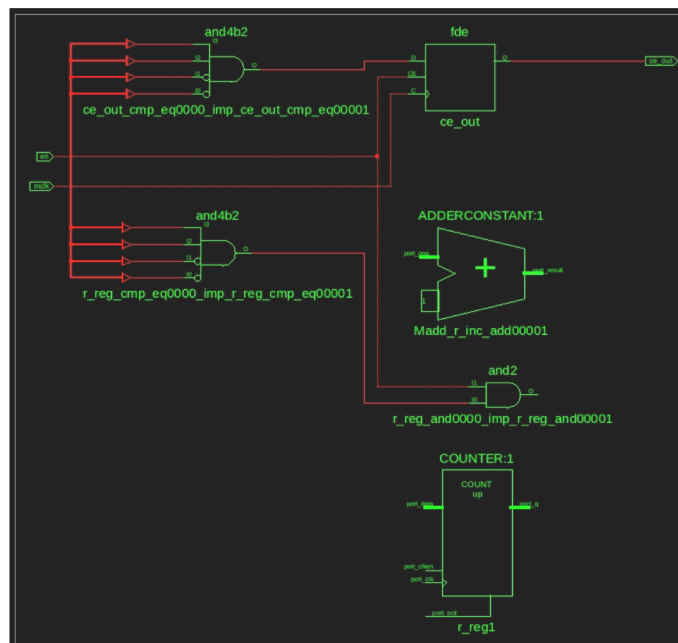


RTL View – Version 2

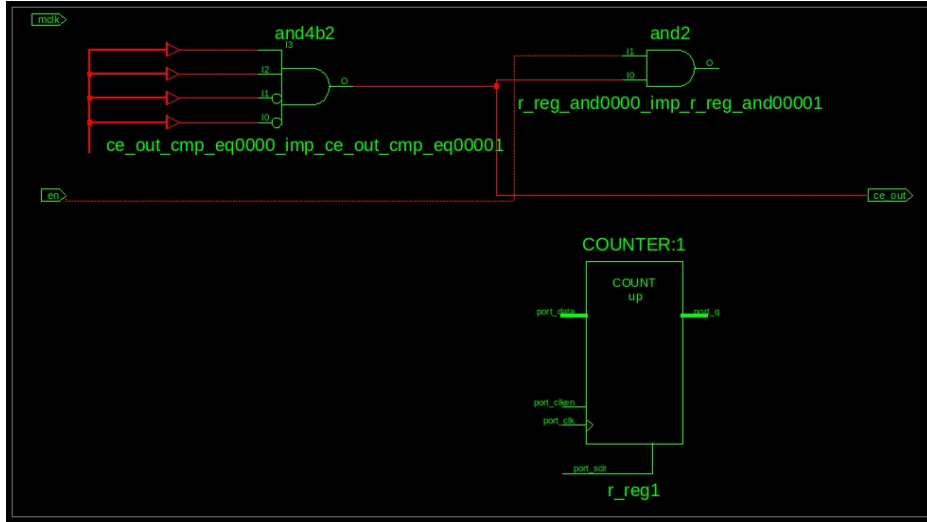


Tech View – Version 1

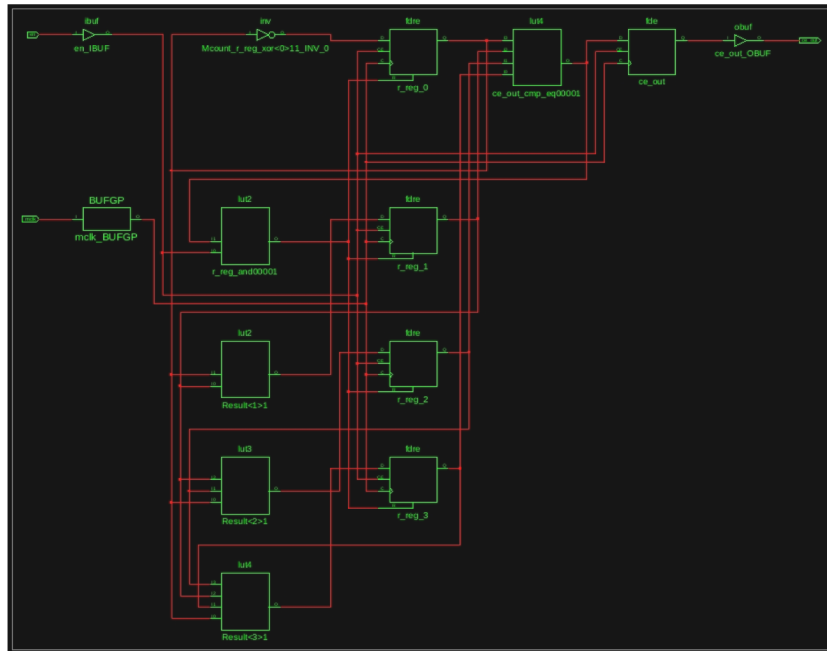


Tech View – Version 2

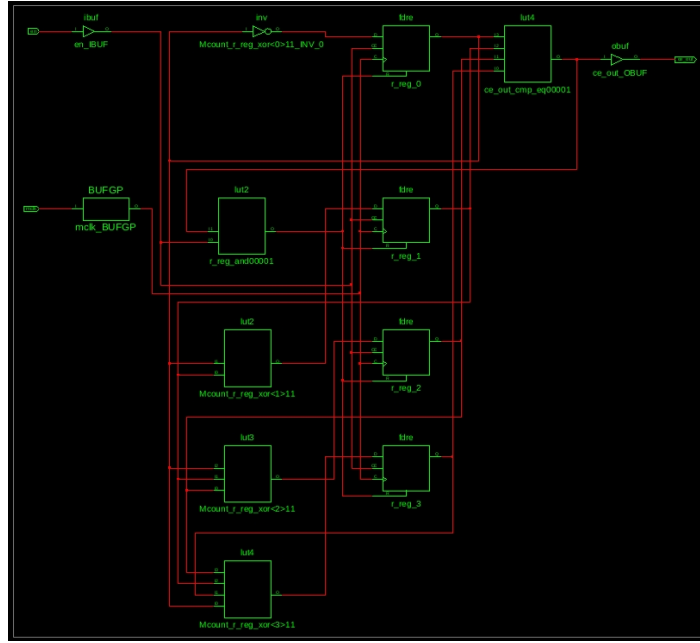

Timing – Version 1

 

Timing – Version 2

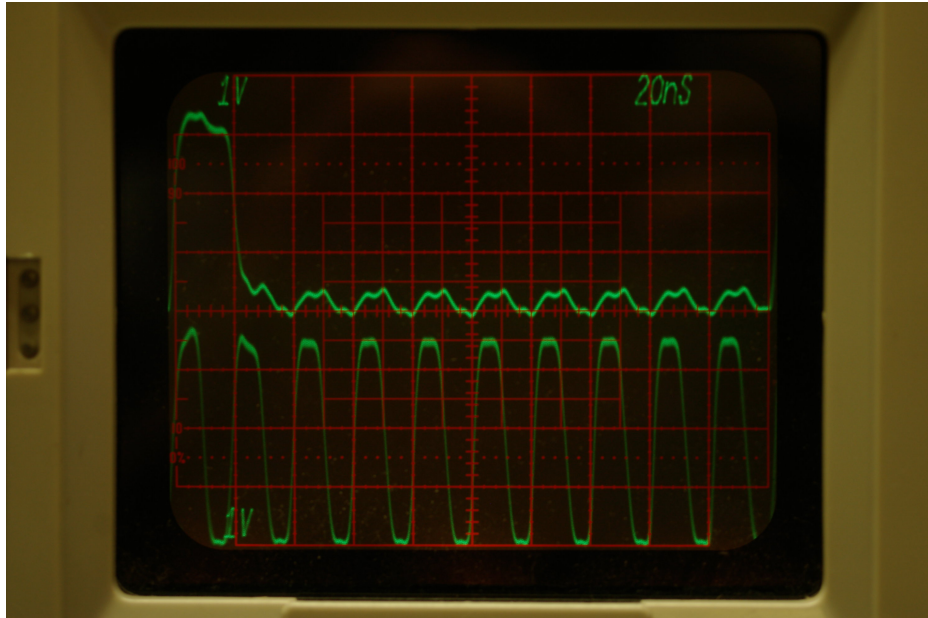

Behavioral Divide by 1,000,000 - Example 1

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity div_by_1000000_ver1 is
  Port ( mclk : in  STD_LOGIC;
        sclk_out : out  STD_LOGIC;
        mclk_out : out  STD_LOGIC);
end div_by_1000000_ver1;

architecture Behavioral of div_by_1000000_ver1 is
  -- divide by 1000000, so 20 bits needed
  signal r_reg: unsigned(19 downto 0);
  signal r_next: unsigned(19 downto 0);
begin
  process(mclk)
  begin
    if (mclk'event and mclk='1') then
      if (r_reg = 999999) then
        r_reg <= (others=>'0');
        sclk_out <= '1';
      else
        r_reg <= r_next;
        sclk_out <= '0';
      end if;
    end if;
  end process;
  r_next <= r_reg + 1;
  mclk_out <= mclk;
end Behavioral;

```

Behavioral Divide by 1,000,000 - Example 2

```

architecture Behavioral of div_by_1000000_ver2 is
-- divide by 1000000, so 20 bits needed
    signal r_reg: unsigned(19 downto 0);
    signal r_next: unsigned(19 downto 0);
begin
    process(mclk,r_reg)
    begin
        if (mclk'event and mclk='1') then
            if (r_reg = 999999) then
                r_reg <= (others=>'0');
            else
                r_reg <= r_next;
            end if;
        end if;
    end process;
    r_next <= r_reg + 1;
    sclk_out <= '1' when r_reg = 999999 else '0';
    mclk_out <= mclk;
end Behavioral;

```

FPGA Utilization Comparisons

Version 1

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	21	4,896	1%	
Number of 4 input LUTs	6	4,896	1%	
Number of occupied Slices	14	2,448	1%	
Number of Slices containing only related logic	14	14	100%	
Number of Slices containing unrelated logic	0	14	0%	
Total Number of 4 input LUTs	25	4,896	1%	
Number used as logic	6			
Number used as a route-thru	19			
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	2.21			

Version 2

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	20	4,896	1%	
Number of 4 input LUTs	6	4,896	1%	
Number of occupied Slices	13	2,448	1%	
Number of Slices containing only related logic	13	13	100%	
Number of Slices containing unrelated logic	0	13	0%	
Total Number of 4 input LUTs	25	4,896	1%	
Number used as logic	6			
Number used as a route-thru	19			
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	2.25			

Structural Divide by 1,000,000 Using Counters

```

entity div_by_1000000_struct is
  Port ( mclk : in  STD_LOGIC;
        mclk_out : out  STD_LOGIC;
        sclk_out : out  STD_LOGIC);
end div_by_1000000_struct;

architecture Behavioral of div_by_1000000_struct is

  component dec_counter
    Port ( mclk : in  STD_LOGIC;
          en : in  STD_LOGIC;
          ce_out : out  STD_LOGIC);
  end component;
  signal ce1, ce2, ce3, ce4, ce5: std_logic;
begin
  u1: dec_counter port map (mclk, '1', ce1);
  u2: dec_counter port map (mclk, ce1, ce2);
  u3: dec_counter port map (mclk, ce2, ce3);
  u4: dec_counter port map (mclk, ce3, ce4);
  u5: dec_counter port map (mclk, ce4, ce5);
  u6: dec_counter port map (mclk, ce5, sclk_out);
  mclk_out <= mclk;
end Behavioral;

```

FPGA Utilization Comparisons

Structural

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	24	4,896	1%	
Number of 4 input LUTs	29	4,896	1%	
Number of occupied Slices	17	2,448	1%	
Number of Slices containing only related logic	17	17	100%	
Number of Slices containing unrelated logic	0	17	0%	
Total Number of 4 input LUTs	29	4,896	1%	
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	3.97			

Behavioral – Ver 2

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	20	4,896	1%	
Number of 4 input LUTs	6	4,896	1%	
Number of occupied Slices	13	2,448	1%	
Number of Slices containing only related logic	13	13	100%	
Number of Slices containing unrelated logic	0	13	0%	
Total Number of 4 input LUTs	25	4,896	1%	
Number used as logic	6			
Number used as a route-thru	19			
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	2.25			

Testing r_next Instead of r_reg Comparison

```

architecture Behavioral of div_by_1000000_ver2 is
-- divide by 1000000, so 20 bits needed
    signal r_reg: unsigned(19 downto 0);
    signal r_next: unsigned(19 downto 0);
begin
    process(mclk,r_reg)
    begin
        if (mclk'event and mclk='1') then
            if (r_reg = 999999) then
                r_reg <= (others=>'0');
            else
                r_reg <= r_next;
            end if;
        end if;
    end process;
    r_next <= r_reg + 1;
    sclk_out <= '1' when r_reg = 999999 else '0';
    mclk_out <= mclk;
end Behavioral;

architecture Behavioral of div_by_1000000_ver4 is
-- divide by 1000000, so 20 bits needed
    signal r_reg: unsigned(19 downto 0);
    signal r_next: unsigned(19 downto 0);
begin
    process(mclk,r_next)
    begin
        if (mclk'event and mclk='1') then
            if (r_next = 1000000) then
                r_reg <= (others=>'0');
            else
                r_reg <= r_next;
            end if;
        end if;
    end process;
    r_next <= r_reg + 1;
    sclk_out <= '1' when r_next = 1000000 else '0';
    mclk_out <= mclk;
end Behavioral;
    
```



FPGA Utilization Comparisons


Version 2

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	20	4,896	1%	
Number of 4 input LUTs	6	4,896	1%	
Number of occupied Slices	13	2,448	1%	
Number of Slices containing only related logic	13	13	100%	
Number of Slices containing unrelated logic	0	13	0%	
Total Number of 4 input LUTs	25	4,896	1%	
Number used as logic	6			
Number used as a route-thru	19			
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	2.25			

Version 4

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	20	4,896	1%	
Number of 4 input LUTs	7	4,896	1%	
Number of occupied Slices	23	2,448	1%	
Number of Slices containing only related logic	23	23	100%	
Number of Slices containing unrelated logic	0	23	0%	
Total Number of 4 input LUTs	45	4,896	1%	
Number used as logic	7			
Number used as a route-thru	38			
Number of bonded IOBs	3	66	4%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	1.66			

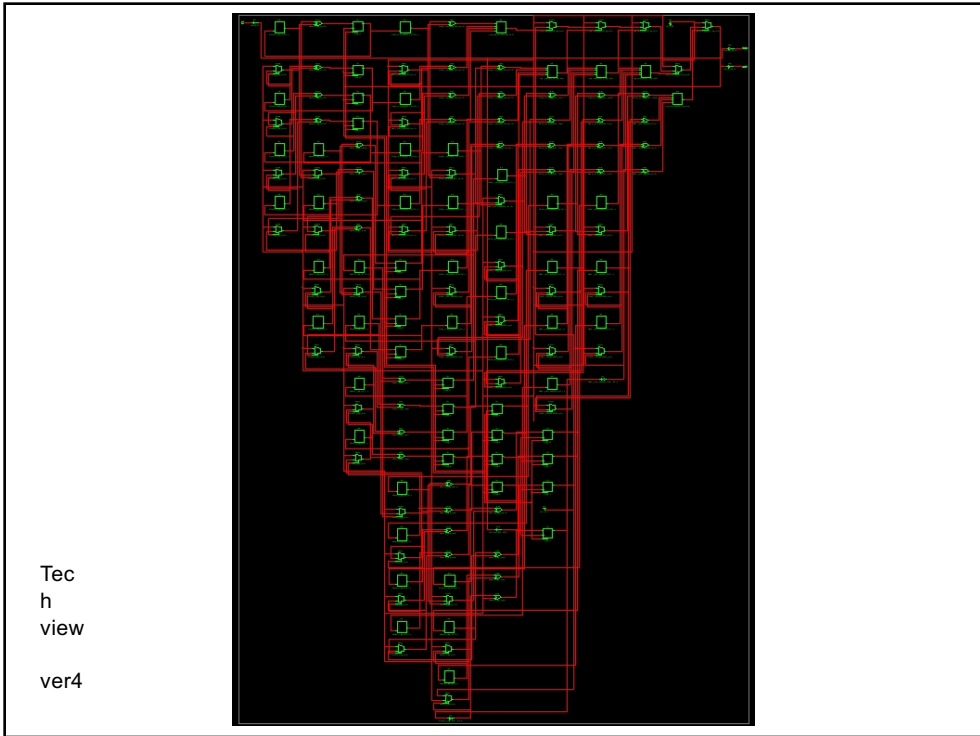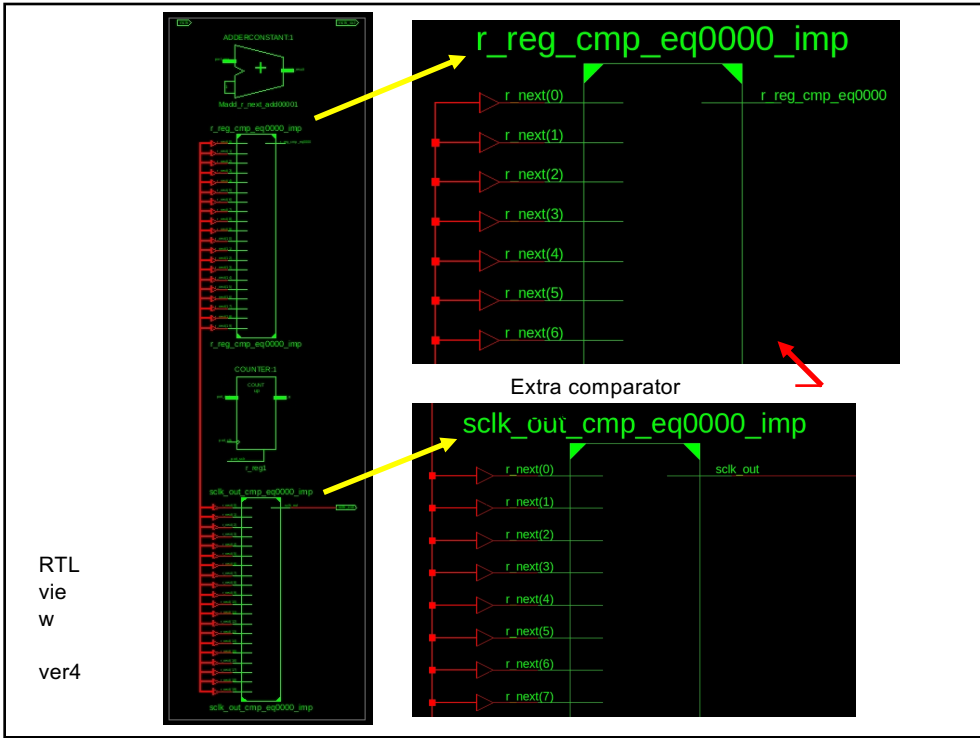

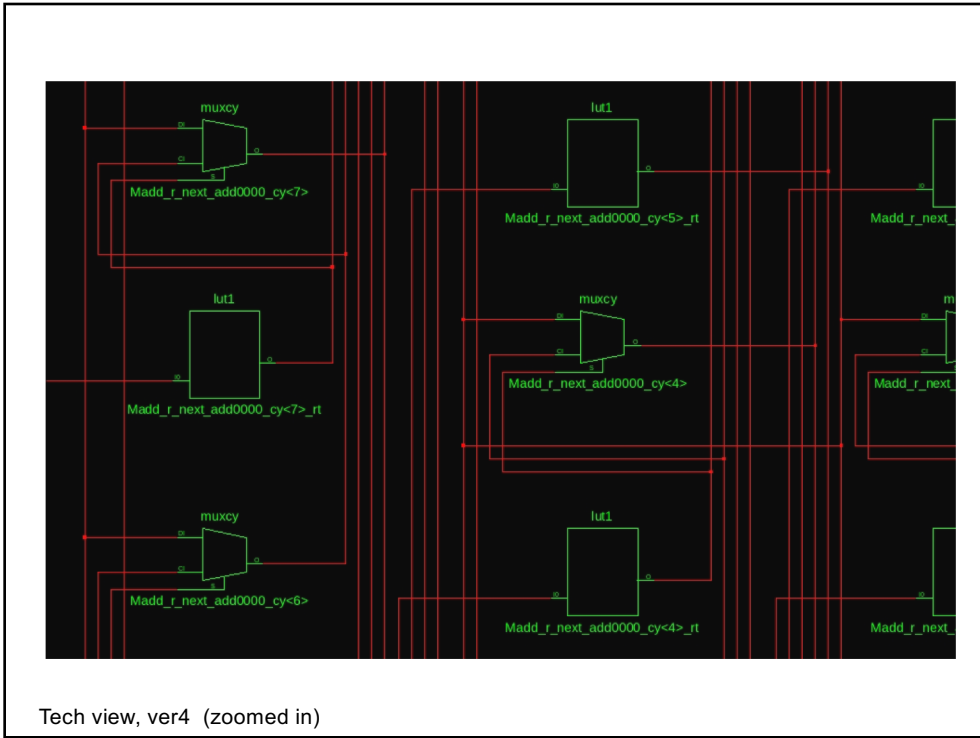

Tech view, ver4 (zoomed in)