

ENGR-384 - HW # 2  
Due Wednesday 1/20/21

Objectives

- Understand operation of a first order circuit
  - Apply the voltage divider relationship to solving a circuit problem
- 1) Do problem 1.4 in the textbook. This is based on the response of a first order system, i.e. instrument (see pages 28-32). Also, see my class notes posted on the class web page. Closely related is the idea of a first order filter. See the notes on filters posted on the class web page (the equations in this reference are in terms of frequency in hertz rather than in radians)
  - 2) Do problem 1.8 in the textbook.
  - 3) The circuit shown below is useful when there is a sensor that is basically a resistor (the resistor in the dashed circle) that changes value a small amount due to a change in its dimensions or the environment around it.

When the change in resistance is small, the change in voltage  $V_2$  will be small. To measure a change in  $V_2$  with respect to ground ( $V_2$  is the voltage across  $R_4$ ) requires a voltmeter with high precision (precision as defined in our text). However, assuming that the ratio  $R_1/R_2$  is nearly the same as  $R_3/R_4$  then a meter with low precision but high sensitivity can be used.

Write an expression for  $V_o$  in terms of  $V$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4 + \Delta R$ . (recall the voltage divider relationship).

