 


Classical State Machine Design




The Basic Memory Cell

Consider this circuit:



The Basic Memory Cell

Consider this circuit:

 

What is the output?


logic high?

logic low?


or something else?


Is this circuit drawn in the best way?


A better circuit diagram:

 

 Recall that it takes time for signals to propagate through a component



 


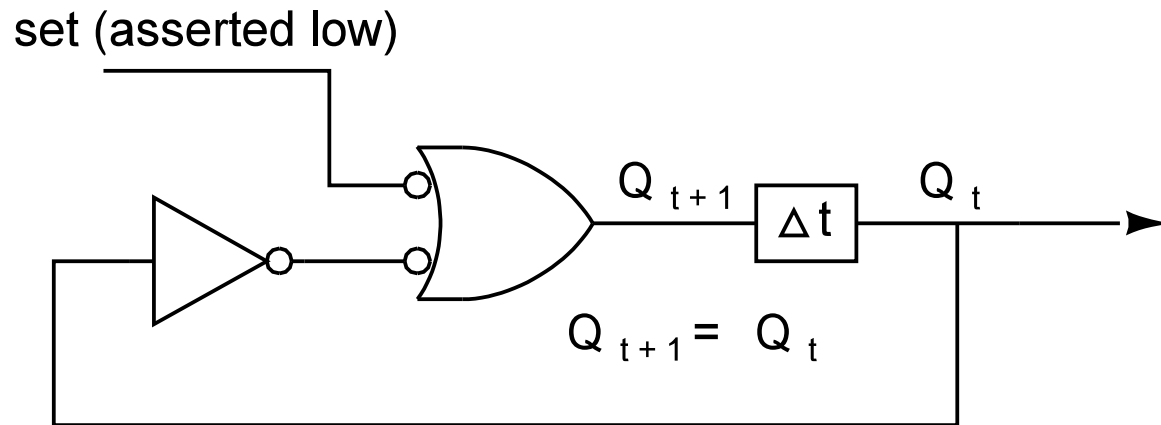

$Q_t =$ Present state

$Q_{t+1} =$ Next state

Set-dominant Basic Cell

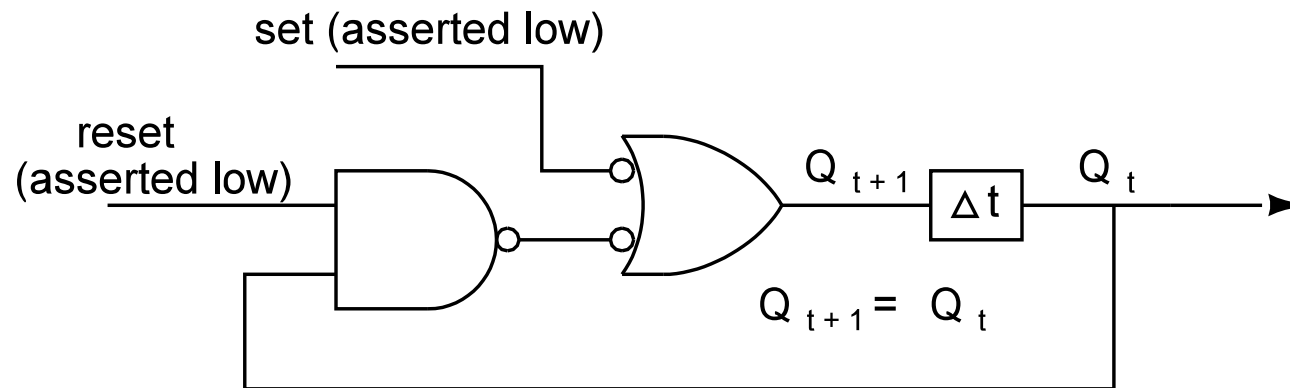


$Q_t =$ Present state

$Q_{t+1} =$ Next state

NAND-Centered (Set Dominant) Basic Cell

 - Inputs are active low (when they are *asserted*);
- Operation table indicates assertion, not voltage, levels.




S	R	Action	Q_{N+1}
0	0	hold	Q^N
0	1	reset	0
1	0	set	1
1	1	set	1

Operation Table

$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
$0 \rightarrow 0$	0	ϕ
$0 \rightarrow 1$	1	ϕ
$1 \rightarrow 0$	0	1
$1 \rightarrow 1$	1	ϕ
	ϕ	0

Excitation Table

 


State Diagram

S	R	Action	Q_{N+1}
0	0	hold	Q_N
0	1	reset	0
1	0	set	1
1	1	set	1

Operation Table

$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
$0 \rightarrow 0$	0	ϕ
$0 \rightarrow 1$	1	ϕ
$1 \rightarrow 0$	0	1
$1 \rightarrow 1$	1	ϕ
	ϕ	0

Excitation Table

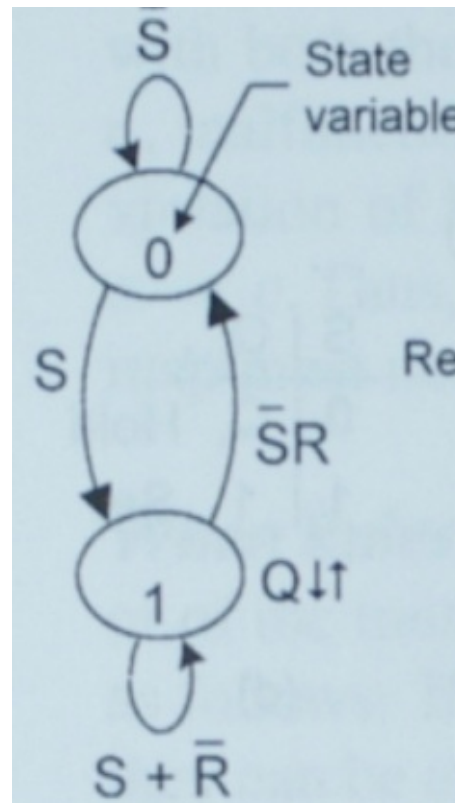


Combined Form of the Basic Cell

$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
0 \rightarrow 0	0	ϕ
0 \rightarrow 1	1	ϕ
1 \rightarrow 0	0	1
1 \rightarrow 1	1	ϕ
	ϕ	0

**Excitation Table
NAND-centered**


$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
0 \rightarrow 0	0	ϕ
	ϕ	1
0 \rightarrow 1	1	0
1 \rightarrow 0	ϕ	1
1 \rightarrow 1	ϕ	0

**Excitation Table
NOR-centered**

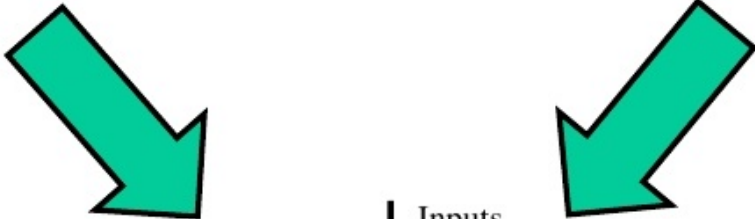


$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
0 \rightarrow 0	0	ϕ
0 \rightarrow 1	1	0
1 \rightarrow 0	0	1
1 \rightarrow 1	ϕ	0



**Excitation Table
Combined Form**

 


Basic Cell


Set dominant basic cell

 

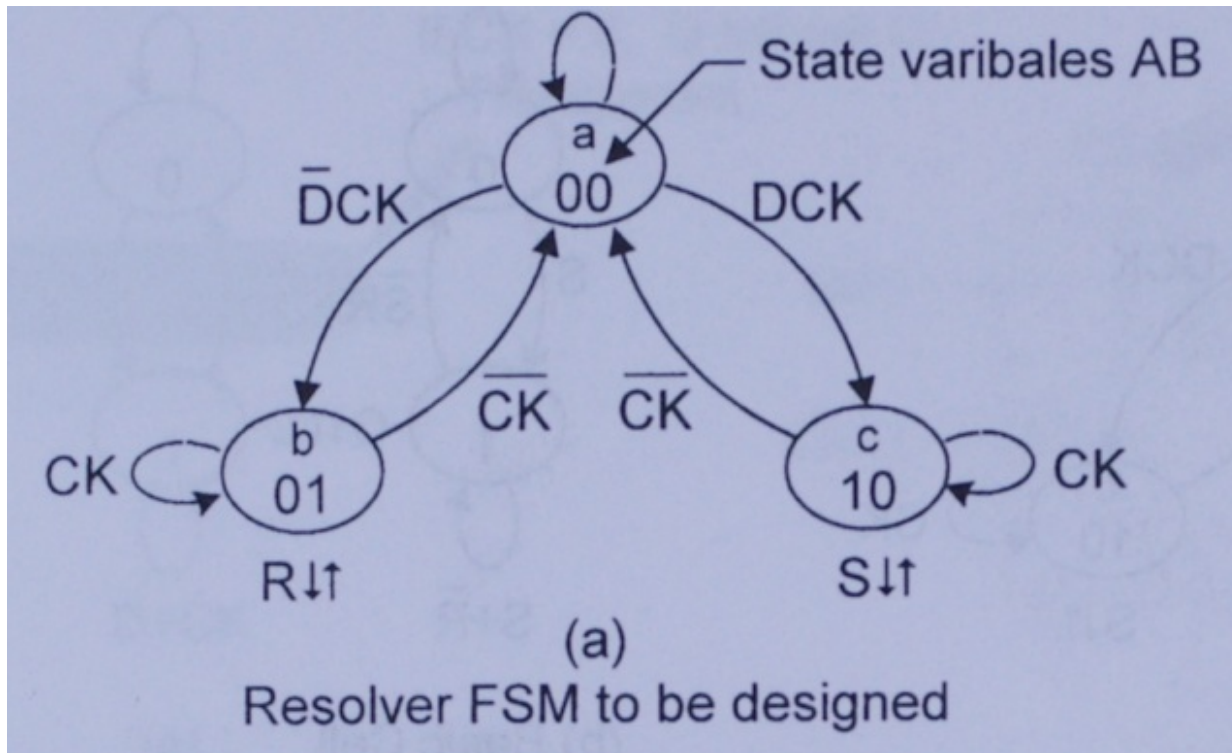 

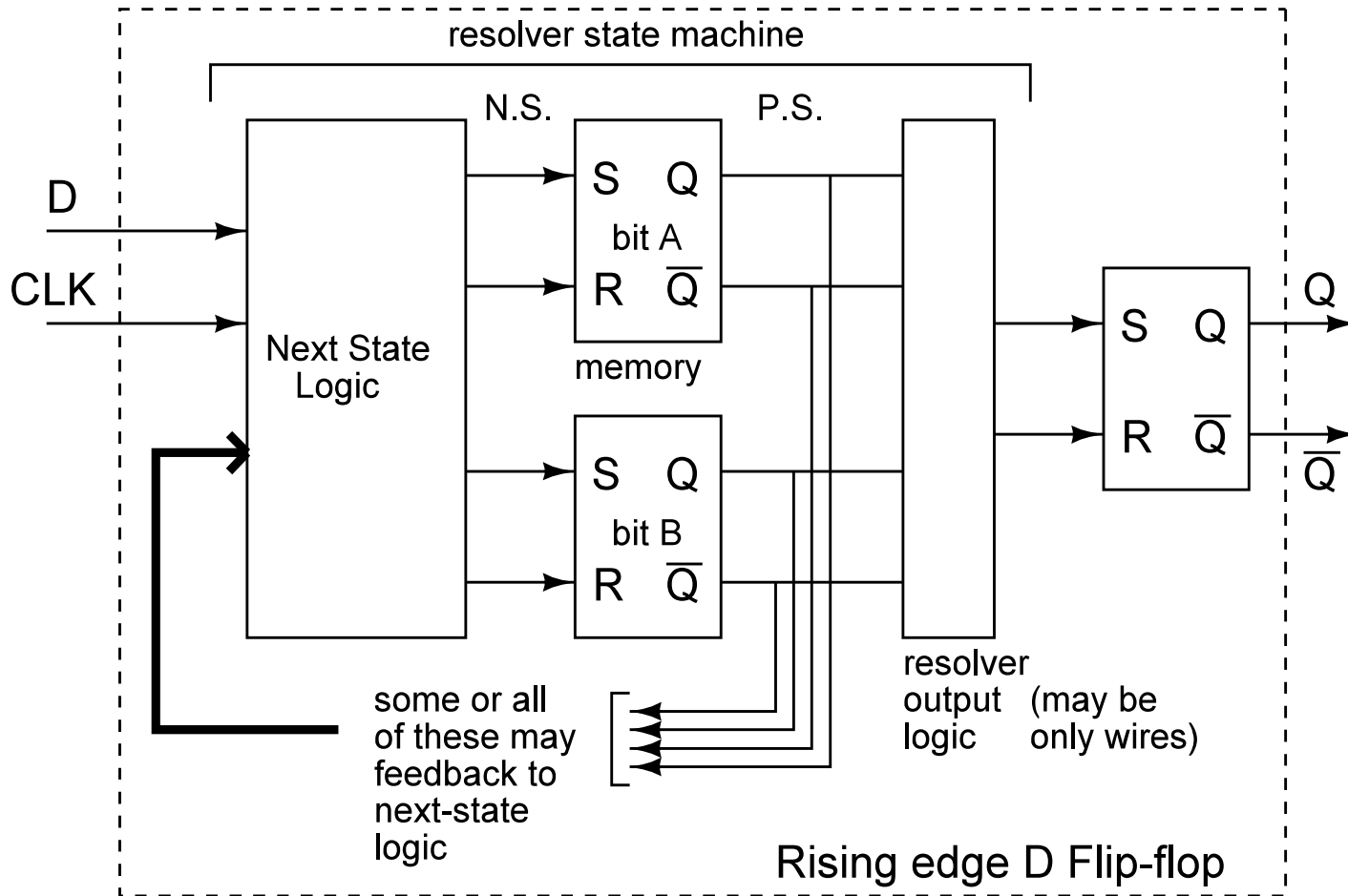
Note that the resolver state diagram has three states and thus two state bits are required. Each state bit will be implemented with a Set-Reset (SR) basic cell, sometimes called an SR-Latch.




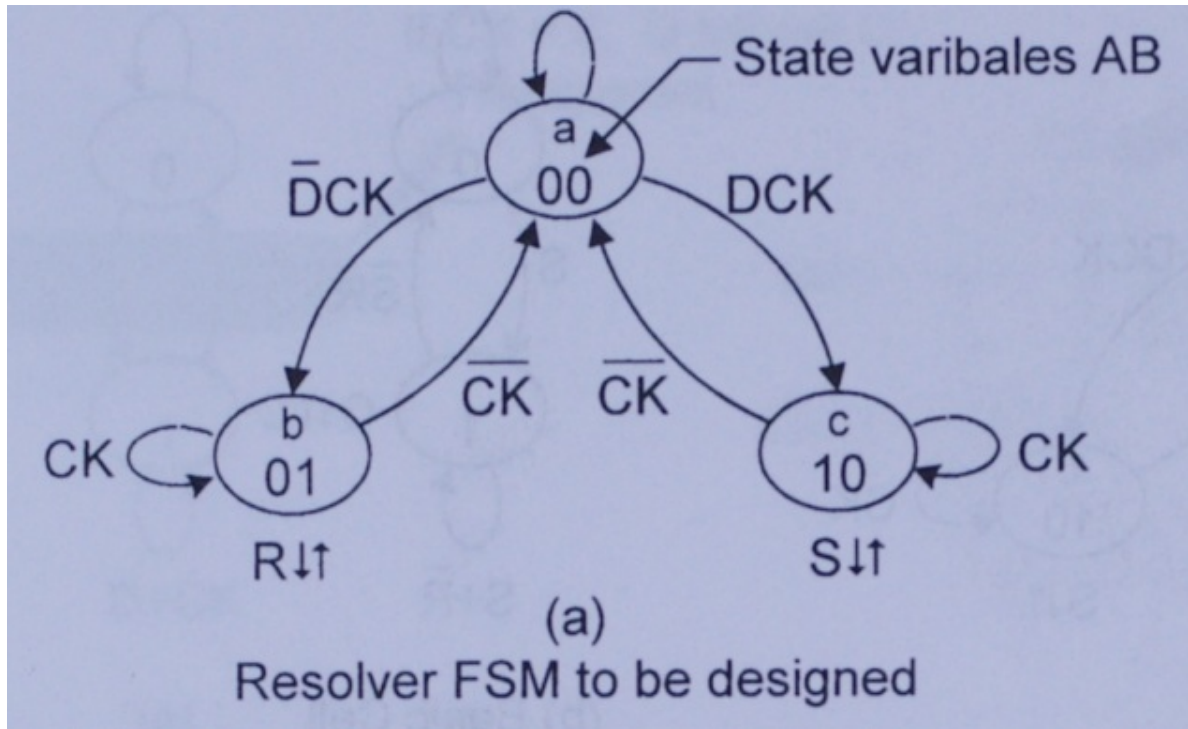

$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
$0 \rightarrow 0$	0	ϕ
$0 \rightarrow 1$	1	0
$1 \rightarrow 0$	0	1
$1 \rightarrow 1$	ϕ	0

 
EV-Kmap to document and reduce the needed Next State logic, bit A



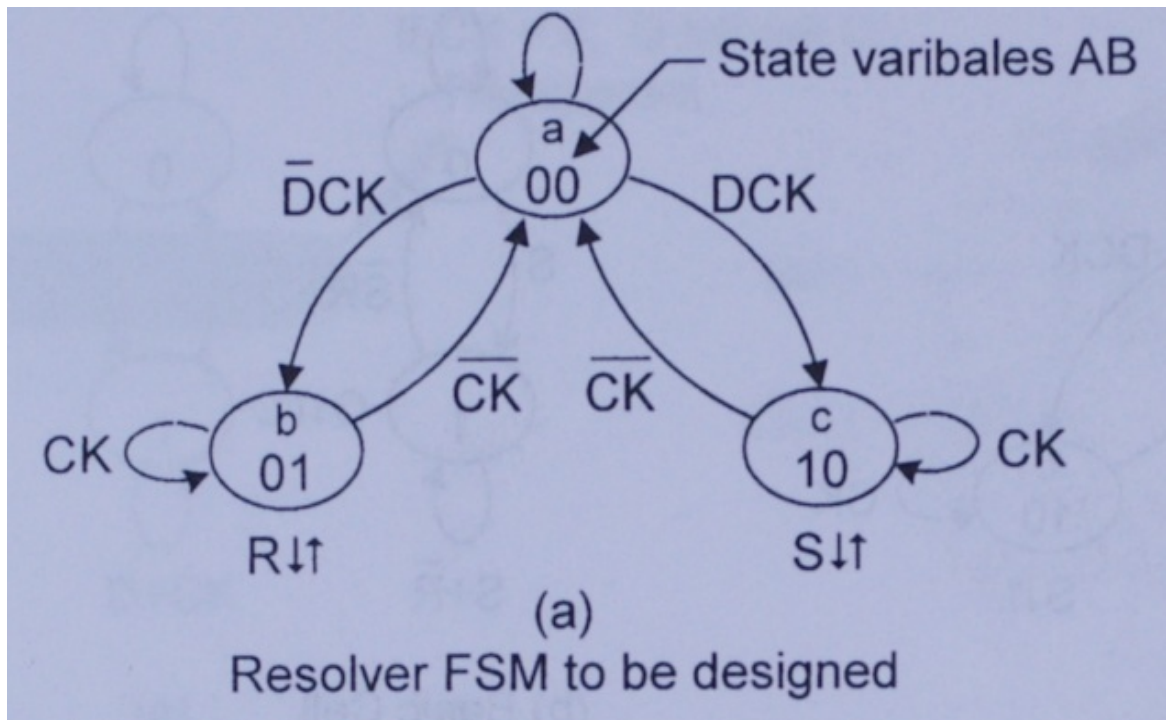

$Q_n \rightarrow Q_{n+1}$	Inputs	
	S	R
$0 \rightarrow 0$	0	ϕ
$0 \rightarrow 1$	1	0
$1 \rightarrow 0$	0	1
$1 \rightarrow 1$	ϕ	0

 EV-Kmap to document and reduce the needed Next State logic, bit B



blank page