

Garage door opener logic

Inputs:

| | |
|---------|----------------------------------|
| iOC | open or close door |
| iBLOCK | sense if door opening is blocked |
| iCLOSED | door is closed |
| iOPENED | door is opened |

Outputs:

| | |
|---------|------------------------------------|
| oOPEN | run door opener in open direction |
| oCLOSE | run door opener in close direction |
| (extra) | |
| oLIGHT | garage light, on for 60 seconds |

Draw state diagram, labeling states with state name and output levels, and transitions with input logic.

