

## PLC WIRING


Power input

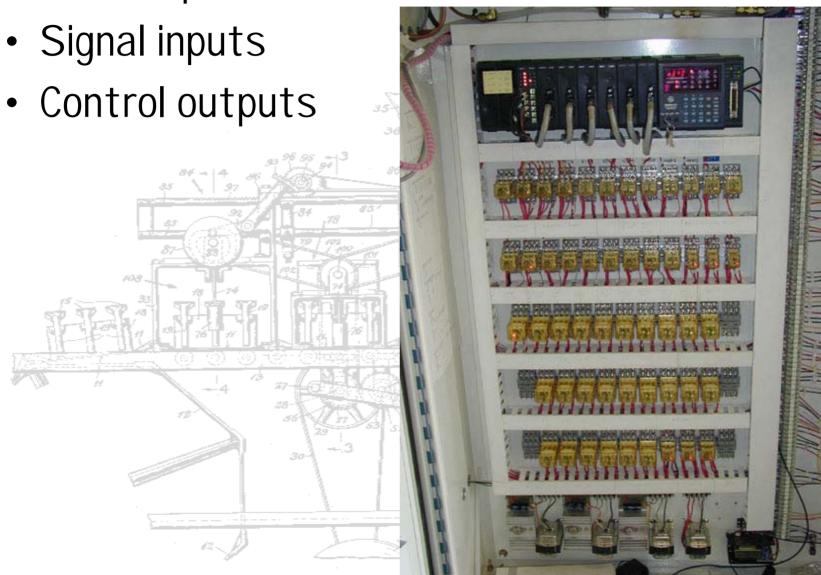


## POWER PLANT PLC

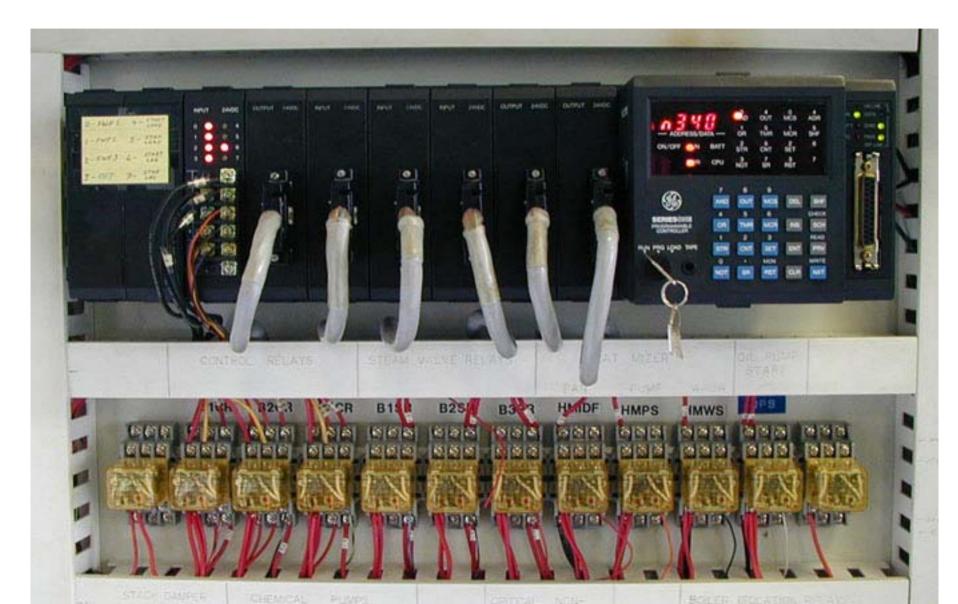


# POWER PLANT PLC

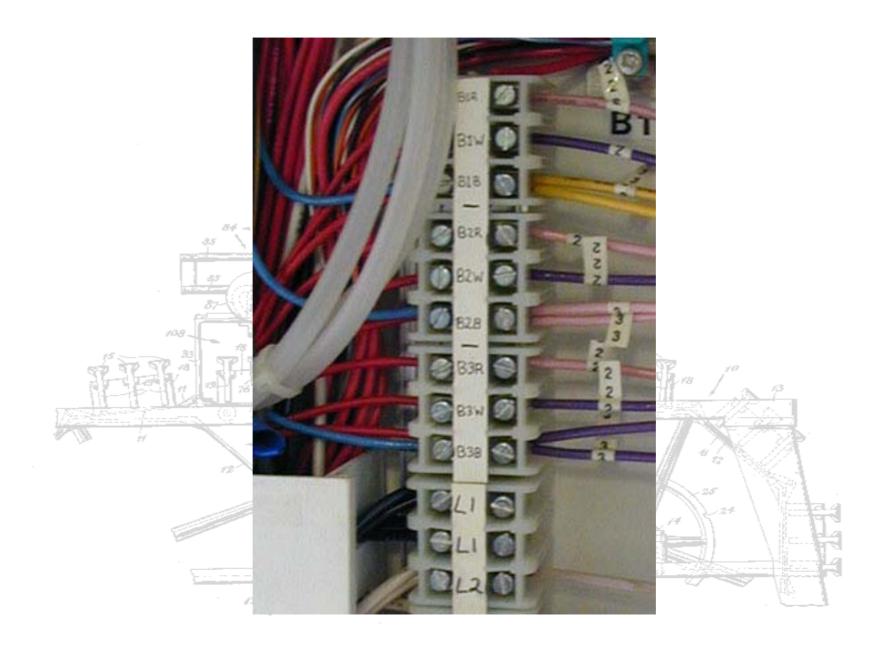


### POWER PLANT PLC

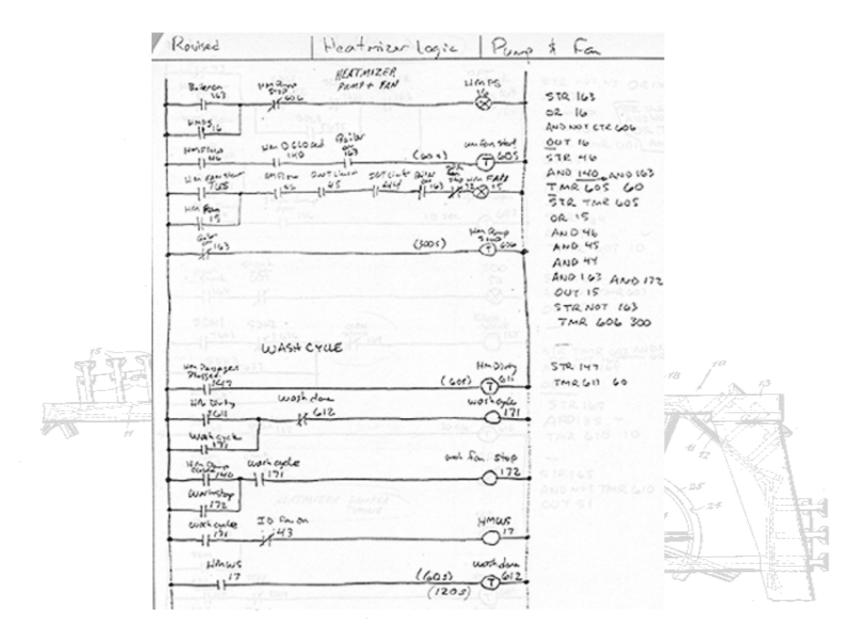


## PLC FRONT PANEL

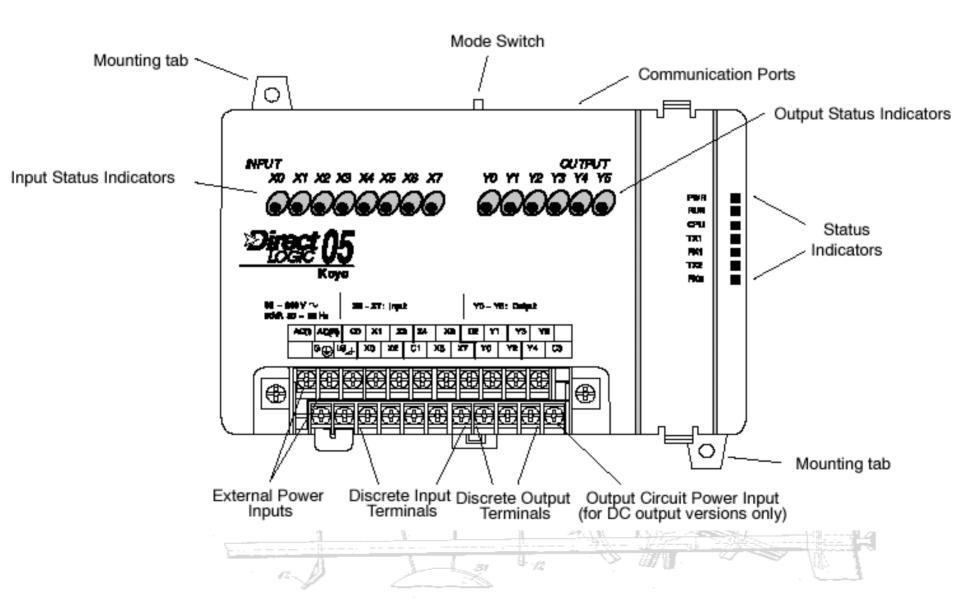


#### **POWER INPUT**

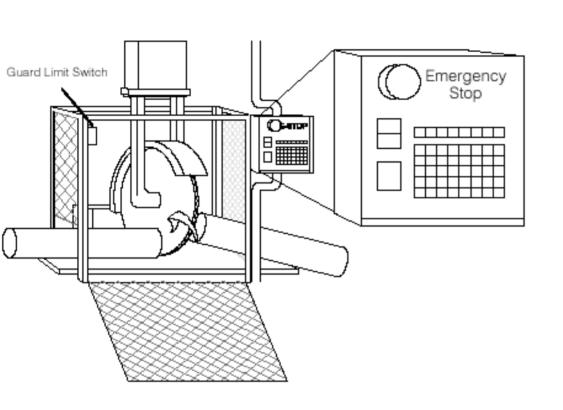

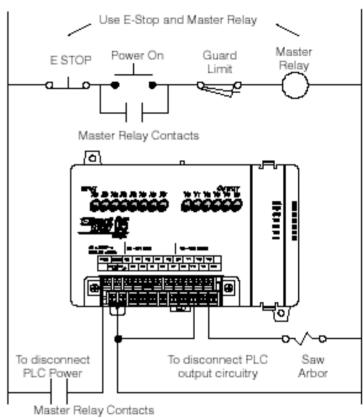


Emergency stop shuts off PLC and PLC loads.


## PLC INPUTS AND OUTPUTS

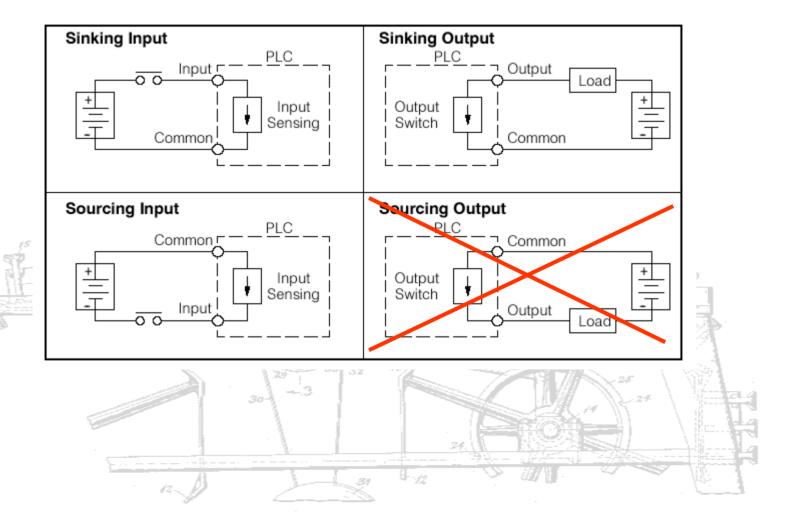

### SIGNAL INPUTS

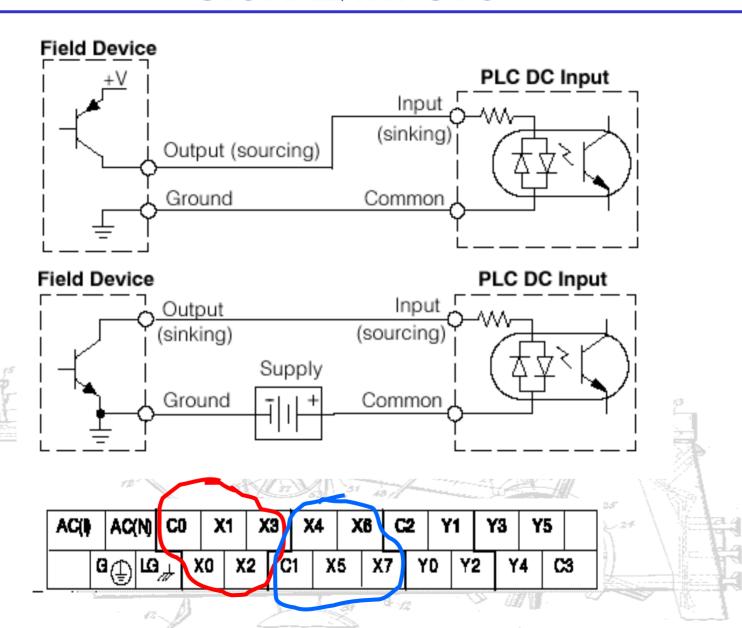

## SIGNAL INPUTS

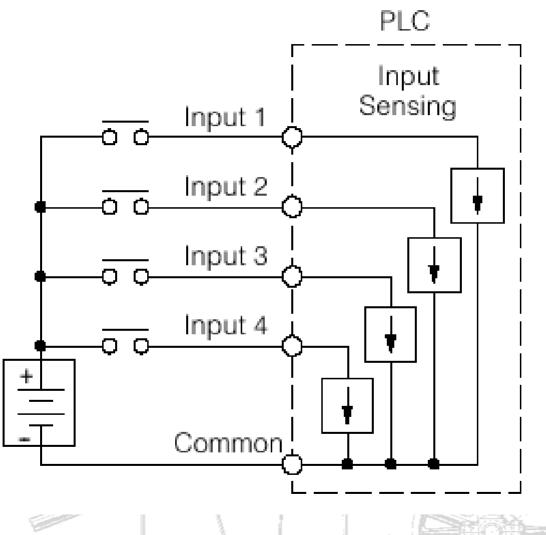


Multiple sinking inputs

### TYPICAL INPUT DEVICE

The tag indicates that the LOAD (PLC input) has a +DC common.

This is a sinking output.

Sinking output => sourcing input

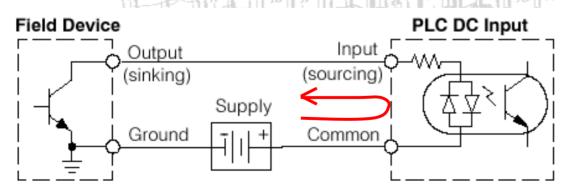




### **ANOTHER INPUT DEVICE**


Photosensor - comes in either NPN (sinking) or PNP (sourcing) outputs.



#### Emitters Cabled Hookup

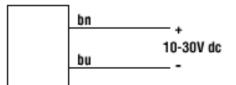
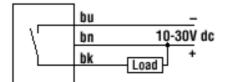
#### Receivers with NPN Outputs Cabled Hookup



#### Receivers with PNP Outputs Cabled Hookup

