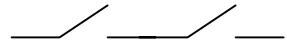
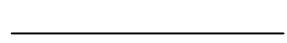
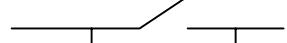
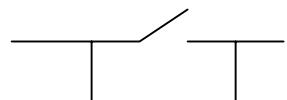
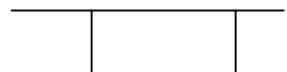


BOOLEAN ARITHMETIC

- 0 and 0 = 0 ($0 \cdot 0 = 0$) 
- 0 and 1 = 0 ($0 \cdot 1 = 0$) 
- 1 and 1 = 1 ($1 \cdot 1 = 1$) 
- 0 or 0 = 0 ($0 + 0 = 0$) 
- 0 or 1 = 1 ($0 + 1 = 1$) 
- 1 or 1 = 1 ($1 + 1 = 1$) 
- not 0 = 1 ($/0 = 1$) 

$$A \cdot /A = 1$$

$$A \cdot B = B \cdot A$$

$$A \cdot B + A \cdot C = A \cdot (B+C)$$


DIGITAL LOGIC EXPRESSIONS

**oCUT = (iPARTRDY•iCYLRETRACT
+ oCUT•/iCYLEXTEND)•/iESTOP**


oCUT = iPARDTRDY•iCYLRETRACT•/iESTOP
+ oCUT•/iCYLEXTEND•/iESTOP

When part is ready, cylinder is retracted, and emergency stop is not on, then cut while cylinder is not fully extended and emergency stop is not on.

THE SIMPLEST STATE MACHINE

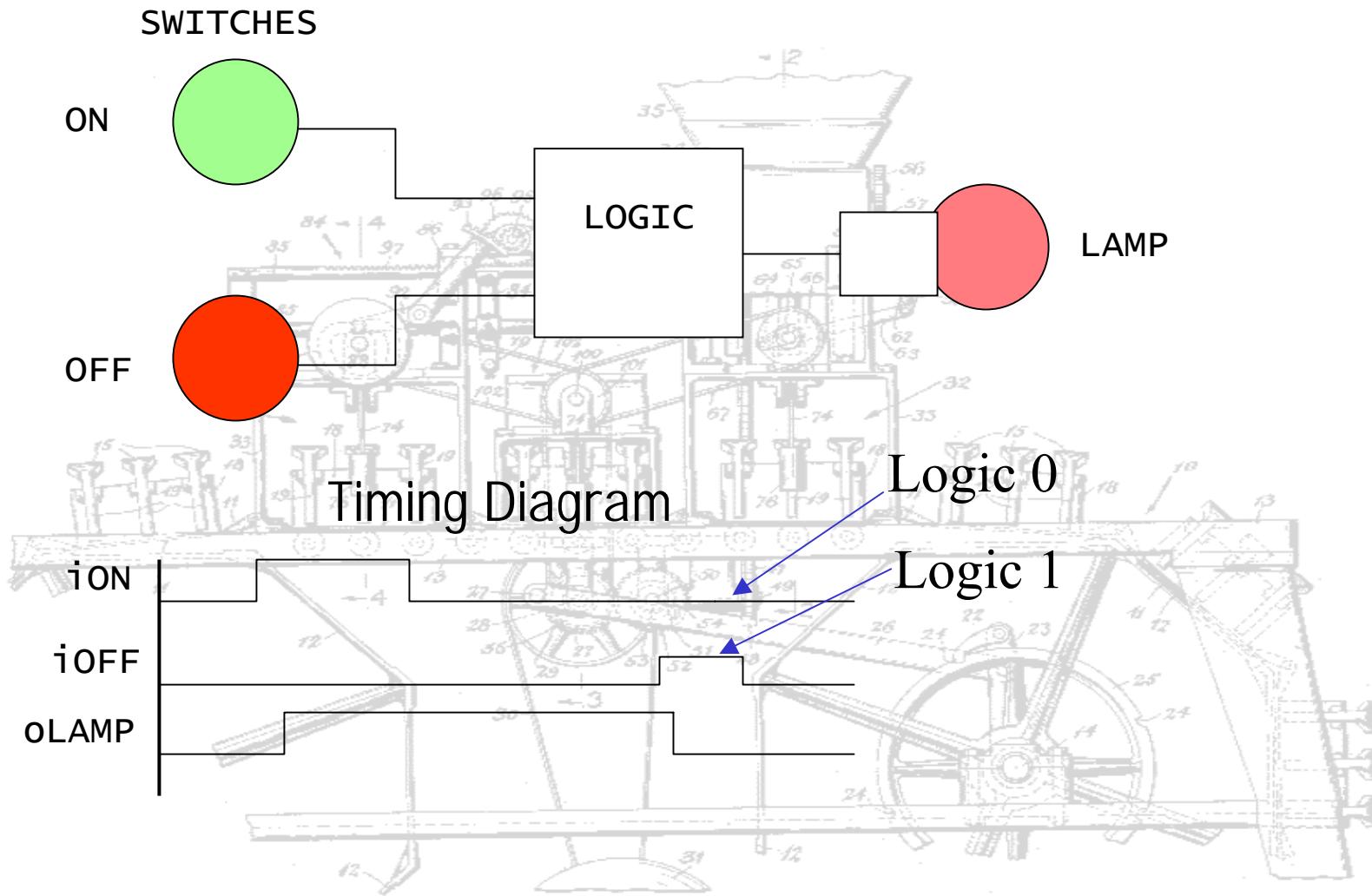

THE SIMPLEST STATE MACHINE

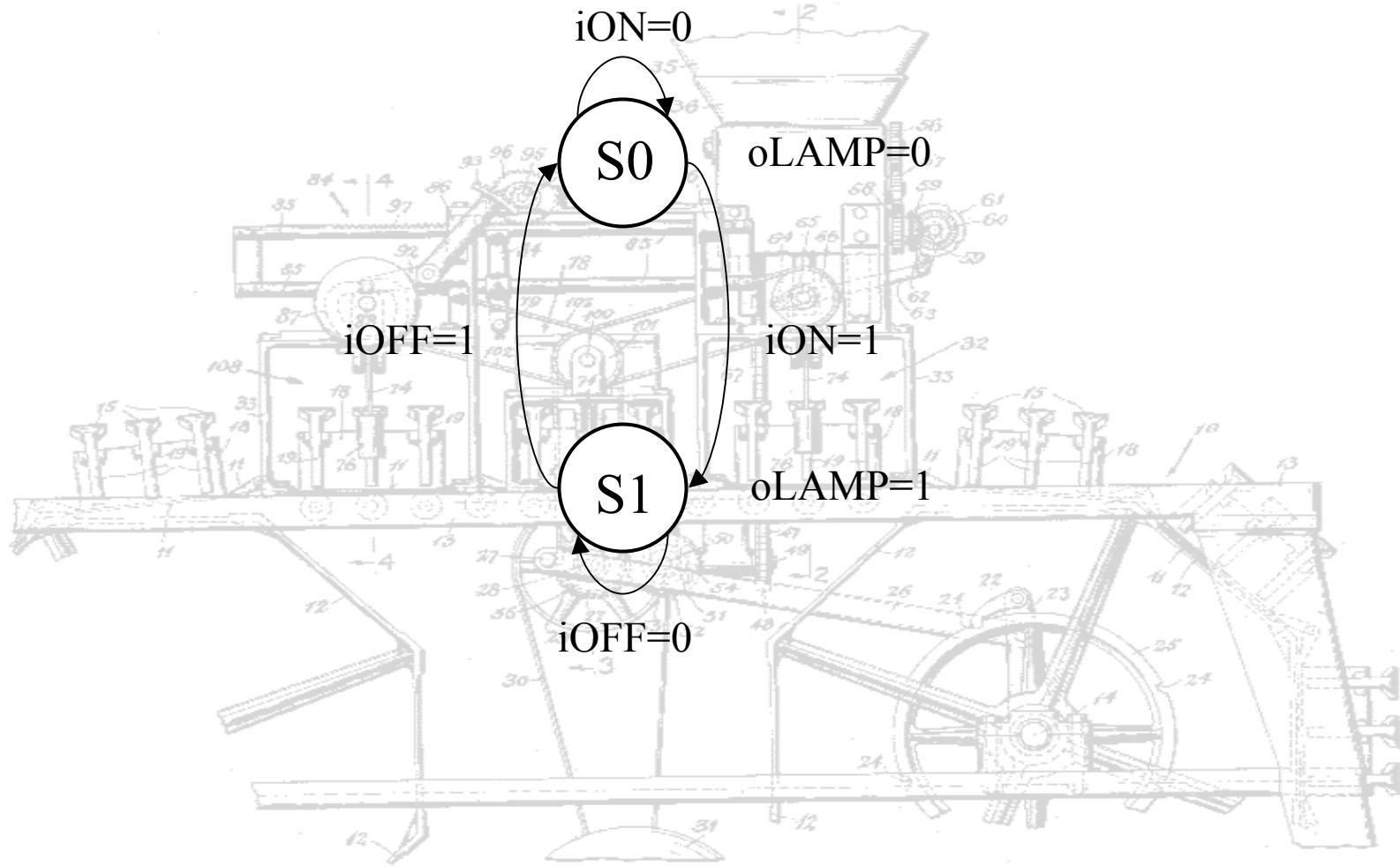

STATE TRANSITION TABLE

ion iOFF oLAMP
 (now)

oLAMP
 (Next)

0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

0

1

0

0

1

1

0

0

/ion•/iOFF•oLAMP

ion•/iOFF•/oLAMP

ion•/iOFF•oLAMP

ion•/iOFF•/oLAMP


ion•/iOFF•oLAMP

ion•/iOFF•/oLAMP

ion•/iOFF•oLAMP


ion•/iOFF•/oLAMP

ion•/iOFF•oLAMP

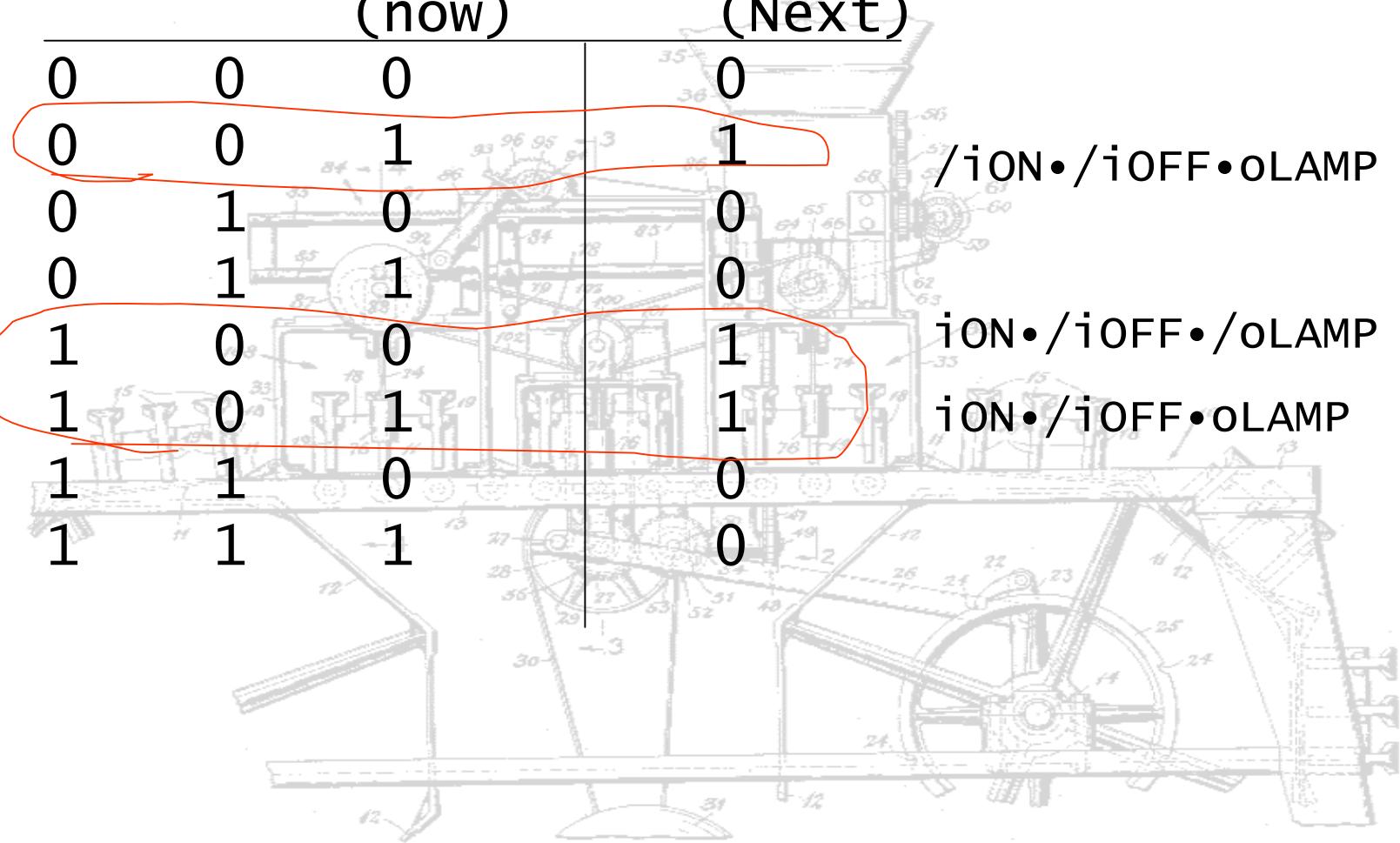


LOGIC EQ. & LADDER DIAGRAM
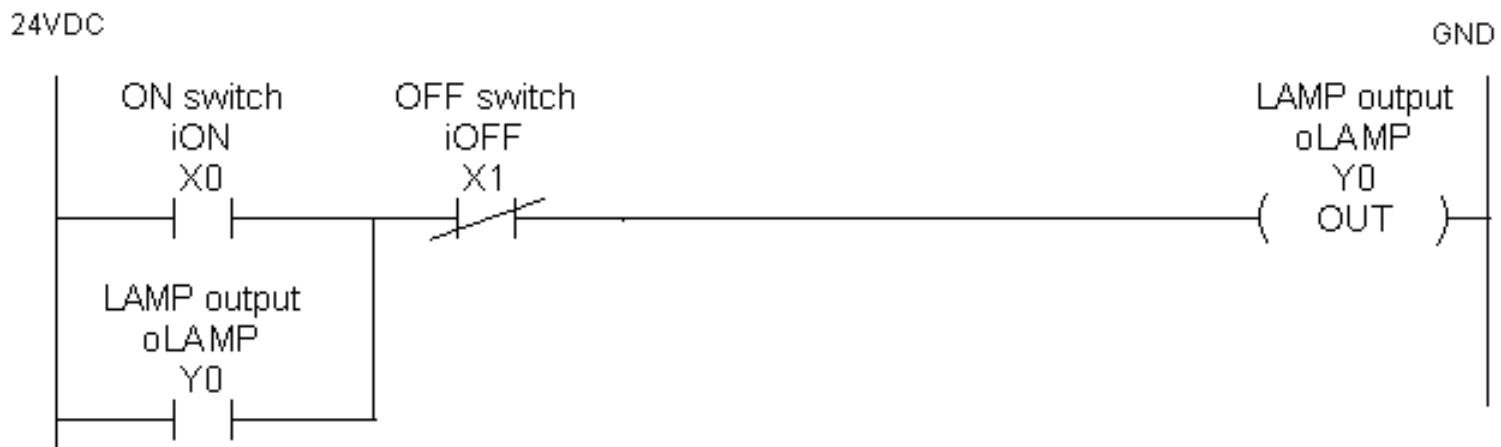
$$\begin{aligned} oLAMP &= /iON \cdot /iOFF \cdot oLAMP \\ &\quad + iON \cdot /iOFF \cdot /oLAMP \\ &\quad + iON \cdot /iOFF \cdot oLAMP \\ &= iON \cdot /iOFF \cdot (/oLAMP + oLAMP) \\ &\quad + /iOFF \cdot oLAMP \cdot (/iON + iON) \\ &= iON \cdot /iOFF + /iOFF \cdot oLAMP \\ &= /iOFF \cdot (iON + oLAMP) \end{aligned}$$



ANOTHER EXAMPLE

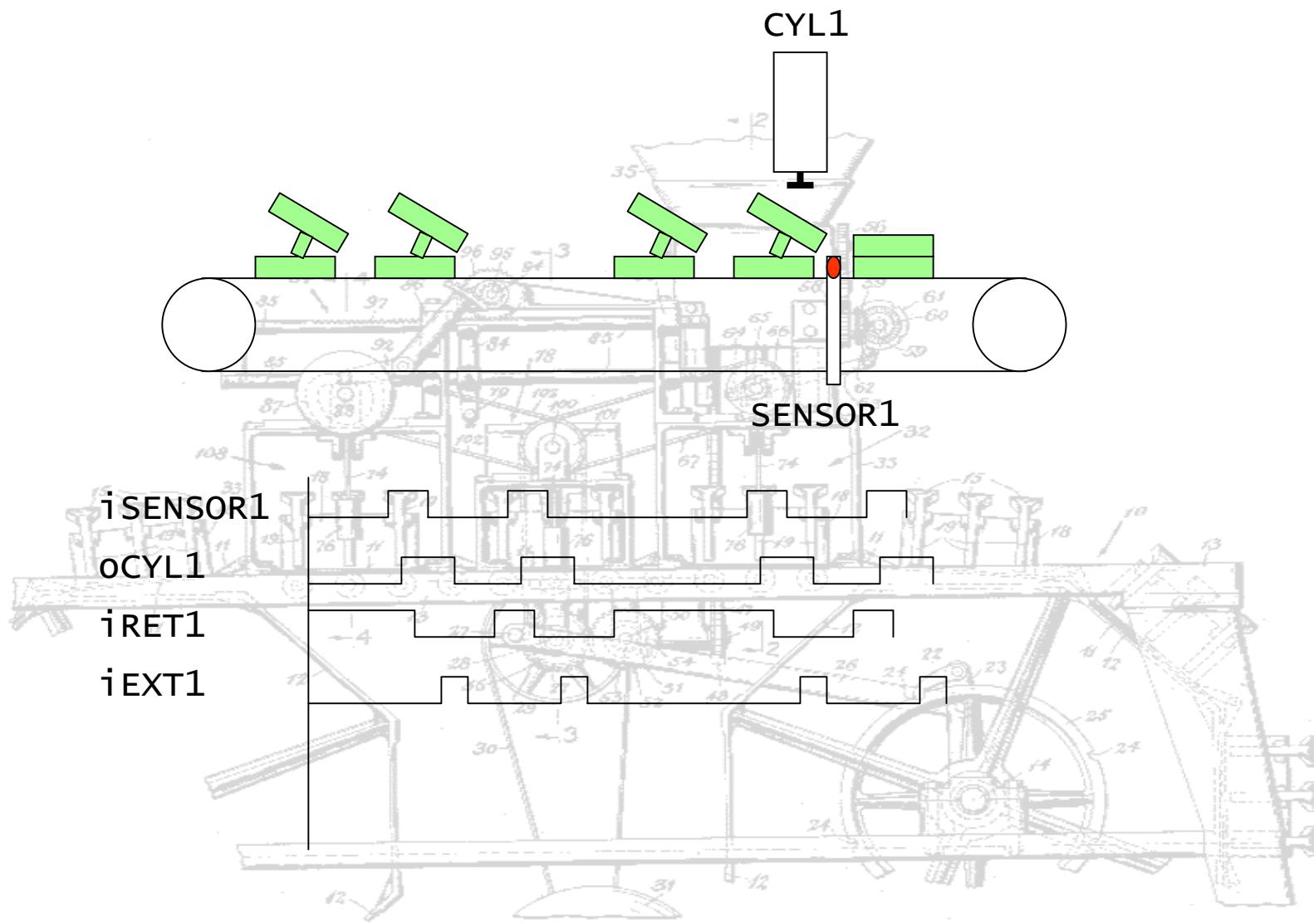

EXAMPLE #2

iSENSOR	iRET	iEXT	oCYL(curr)	oCYL (next)	
0	0	0	0	0	
0	0	0	1	1	
0	0	1	0	0	
0	0	1	1	0	
0	1	0	0	0	
0	1	0	1	0	
0	1	1	0	0	
0	1	1	1	0	
0	1	1	1	0	
1	0	0	0	1	$/iRET \cdot /iEXT \cdot oCYL$
1	0	0	1	1	
1	0	1	0	0	
1	0	1	1	0	
1	1	0	0	1	$+ iSENSOR \cdot /iEXT$
1	1	0	1	1	
1	1	0	0	0	
1	1	1	0	1	
1	1	1	1	0	
1	1	1	0	0	
1	1	1	1	0	
1	1	1	1	0	

EXAMPLE#2 LADDER LOGIC

$$oCYL = iSENSOR \cdot /iRET$$

$$+ /iRET \cdot /iEXT \cdot oCYL$$

$$= (iSENSOR + /iEXT \cdot oCYL) \cdot /iRET$$

