
CONTROL OF MOTION

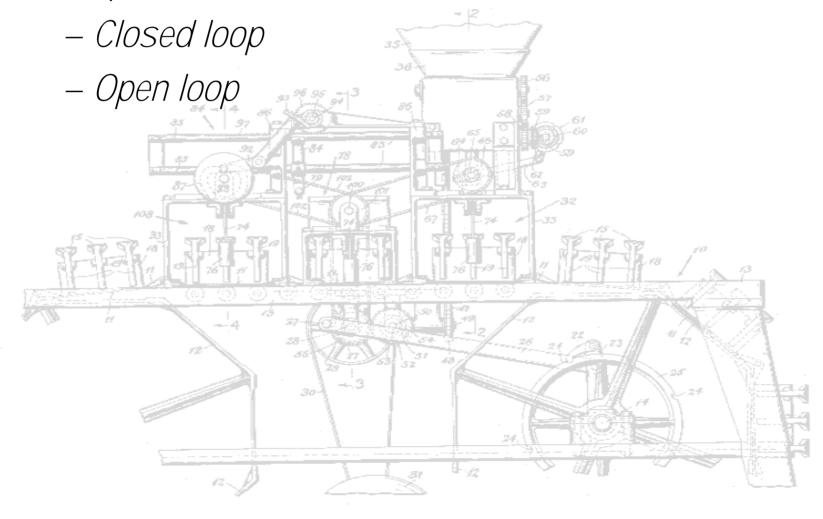- On/Off Control (bang-bang)
- Proportional Control



ON/OFF CONTROL

- Boolean Arithmetic
- Pneumatic logic elements
- Electric Control
 - relays
 - Programmable Logic Controllers (PLC)

BOOLEAN ARITHMETIC

• 0 and 0 = 0
$$(0 \cdot 0 = 0)$$

• 0 and
$$1 = 0$$
 $(0 \cdot 1 = 0)$

• 1 and 1 = 1
$$(1 \cdot 1 = 1)$$
 ———

• 0 or
$$0 = 0$$
 $(0 + 0 = 0)$

• 0 or
$$1 = 1 (0 + 1 = 1)$$

• not
$$0 = 1$$
 $(/0 = 1)$

$$A \cdot /A = 1$$

$$A \cdot B = B \cdot A$$


$$A \cdot B + A \cdot C = A \cdot (B+C)$$

DIGITAL LOGIC EXPRESSIONS

When part is ready, cylinder is retracted, and emergency stop is not on, then cut while cylinder is not fully extended and emergency stop is not on.


PNEUMATIC LOGIC ELEMENTS

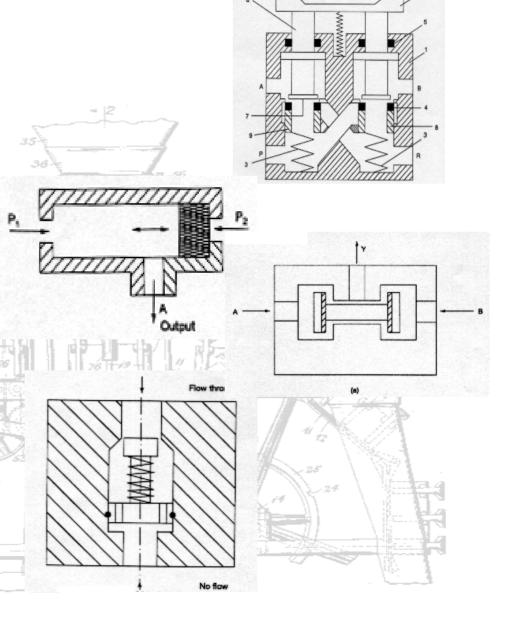- Directional control valve (p.235-242)
- Shuttle valve OR function
- Twin pressure valve
 AND function
- Other functions
 - Check valve
 - Speed control valve
 - Time delay valve




PNEUMATIC SCHEMATICS

Not actuated

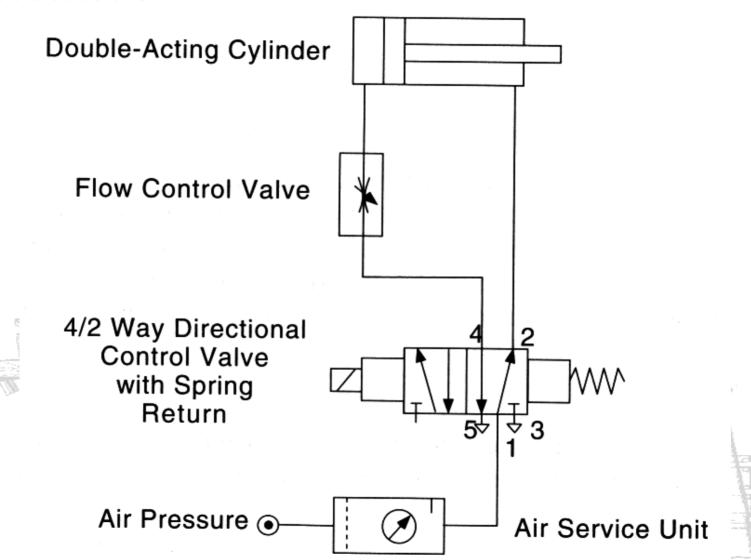


PNEUMATIC SCHEMATICS

Actuated

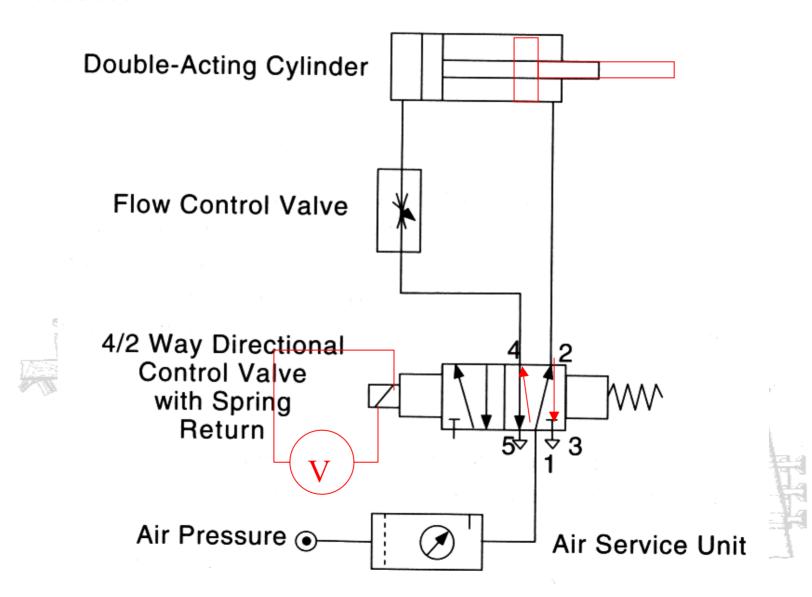


EXAMPLE PNEUMATIC CIRCUIT

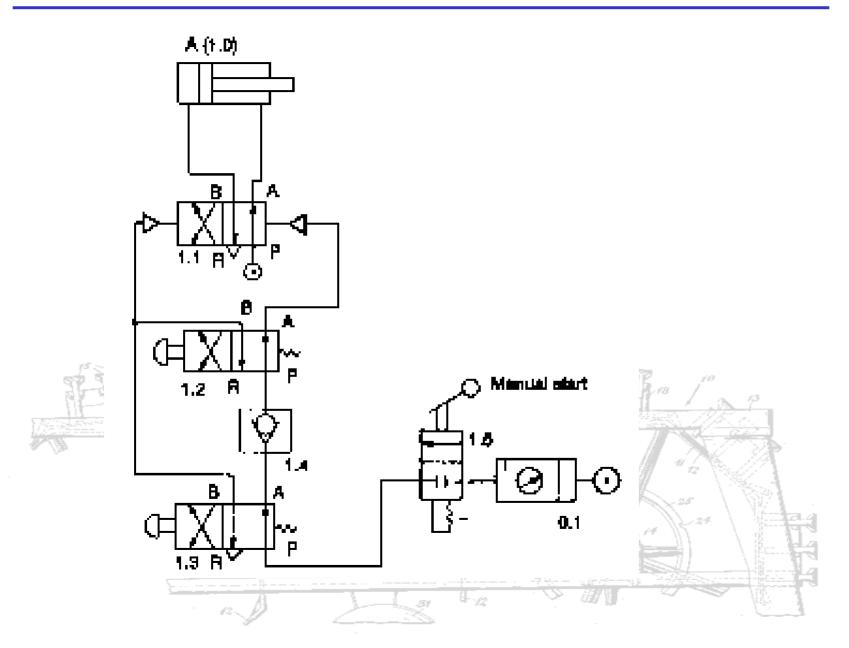


ELECTRIC LOGIC CONTROL


- Input and Output
- Ladder diagrams

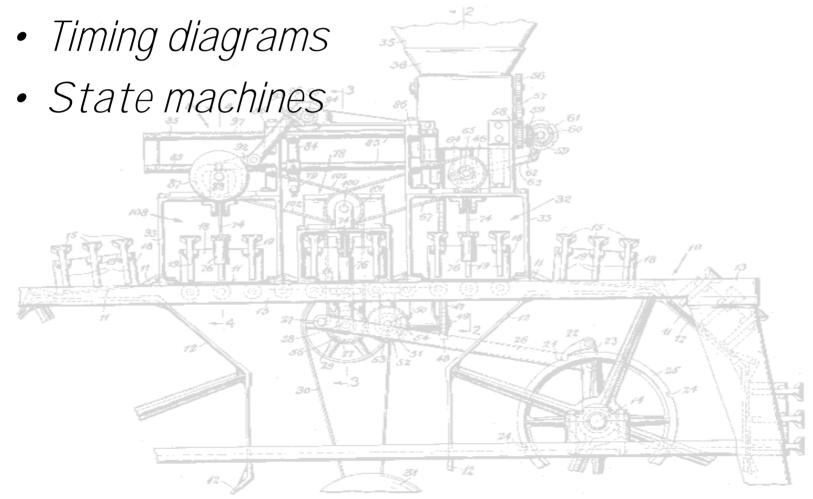

I/O ACTIVITY LEVELS

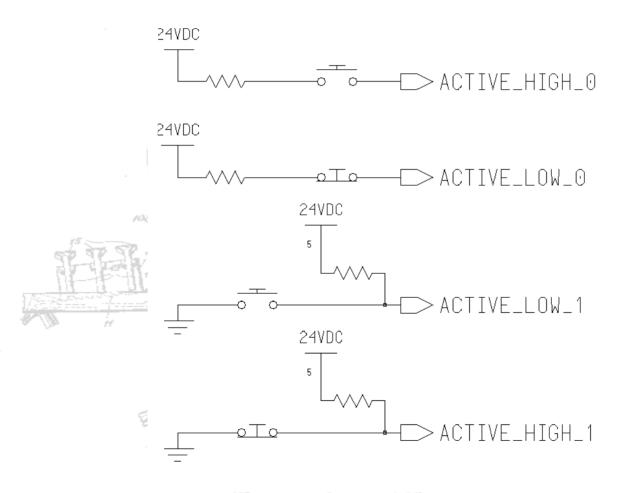- Active High active level is logic 1 (+V)
- Active Low active level is logic O (GND)



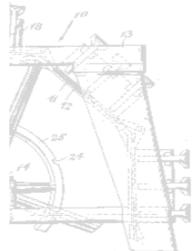

LADDER DIAGRAMS

