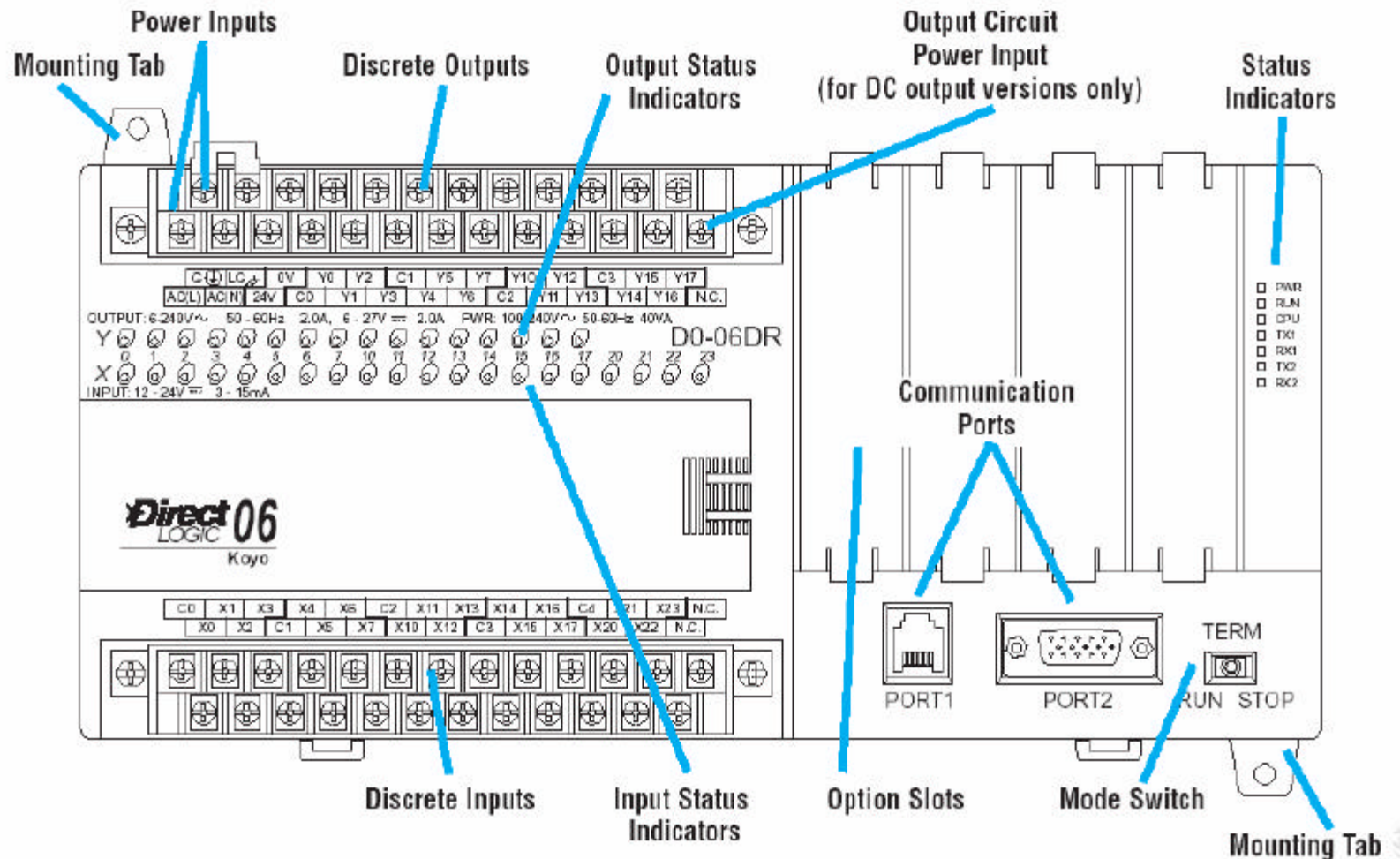


# PLC Front Panel





# PLC Wiring



- Power Inputs
- Signal Inputs
- Control Outputs



# PLC Isolation

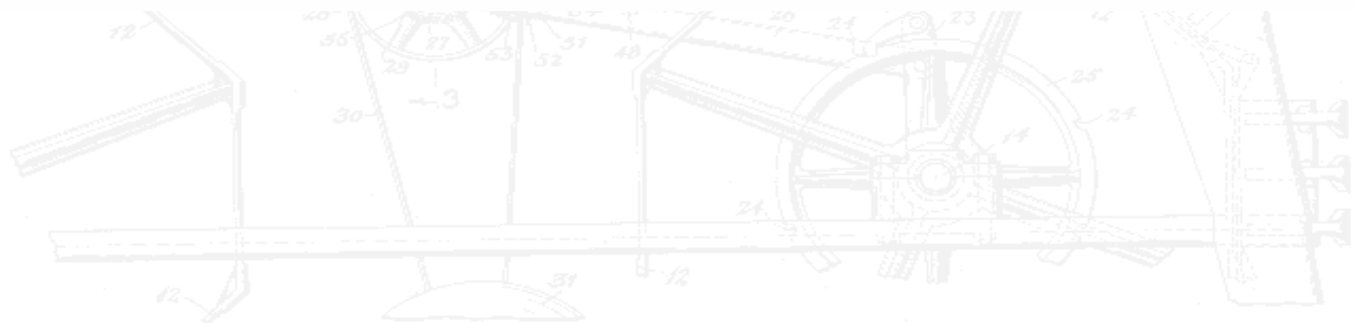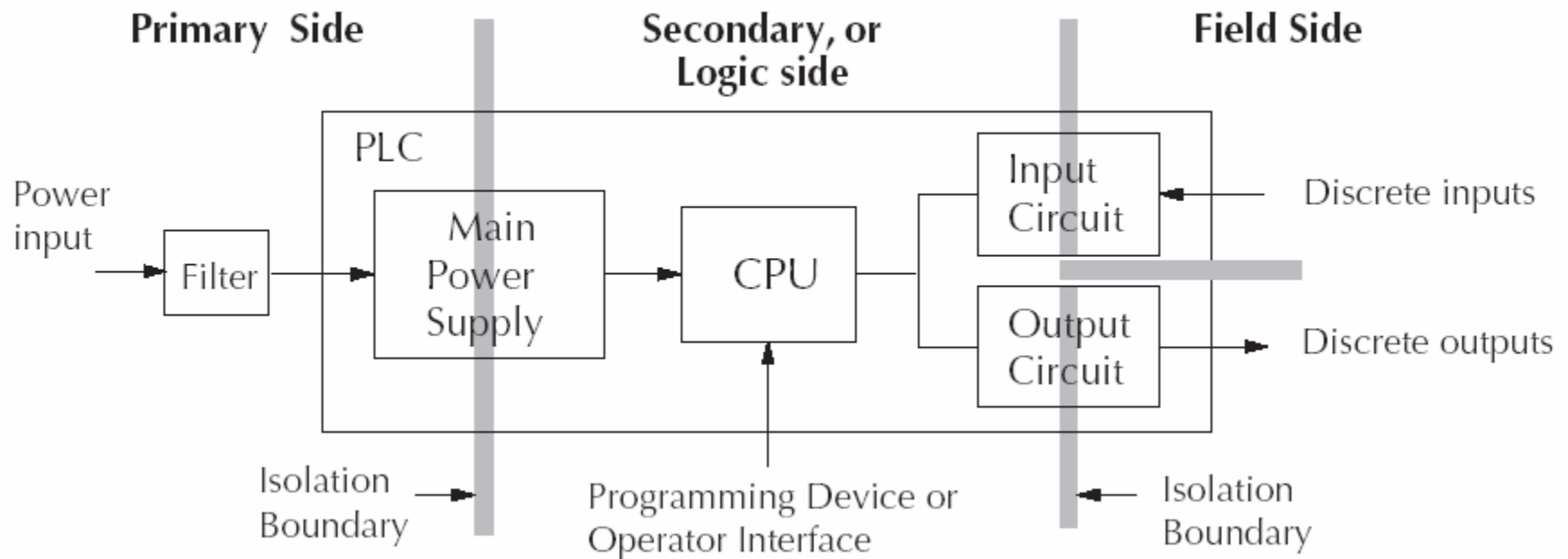


# Power Wiring

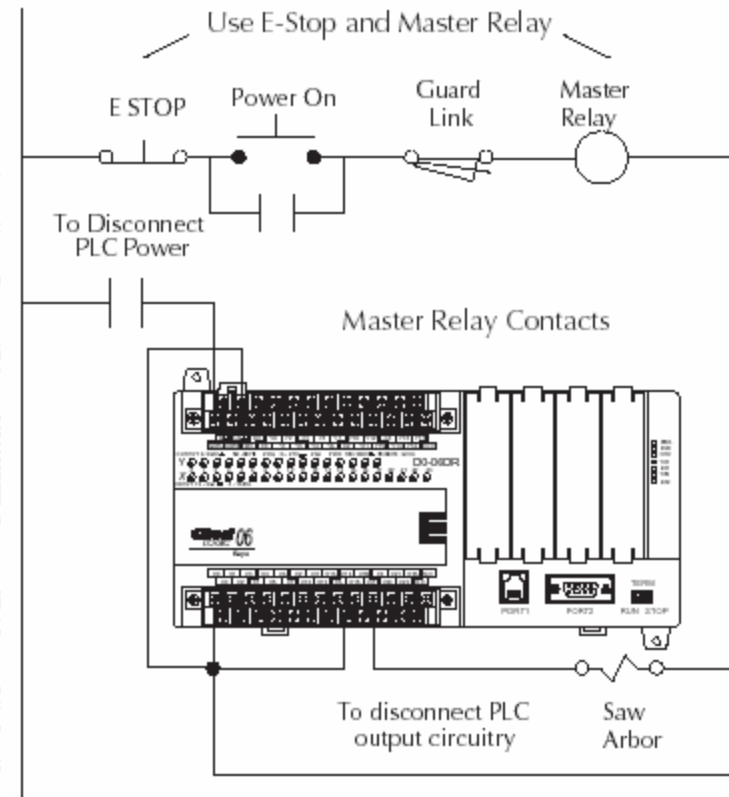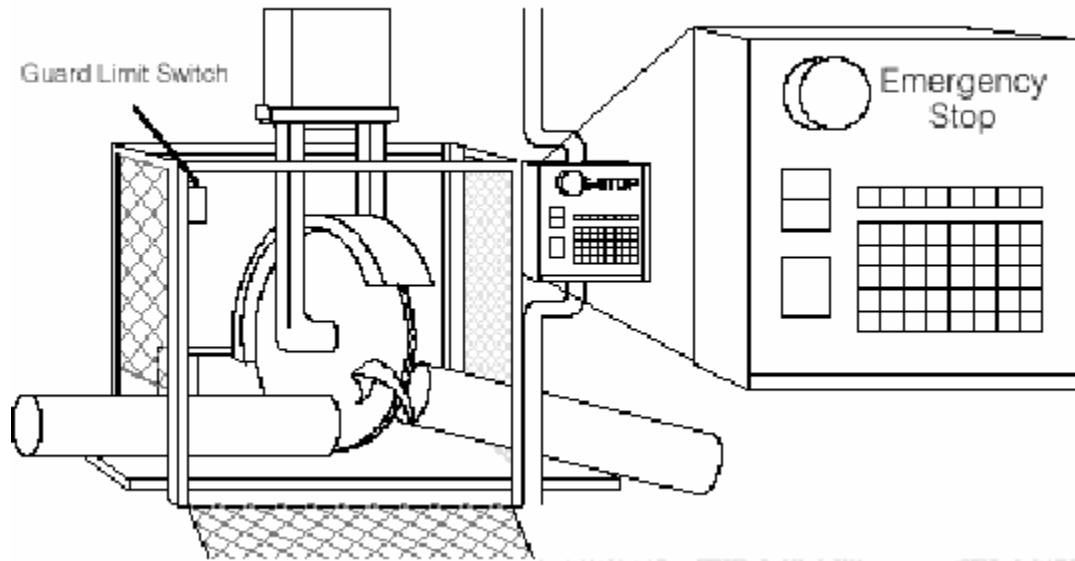



- Three levels of protection:
  - PLC logic - shutdown sequence
  - PLC output power disconnect
  - E-Stop shutdown of all energy sources

# PLC Inputs and Outputs

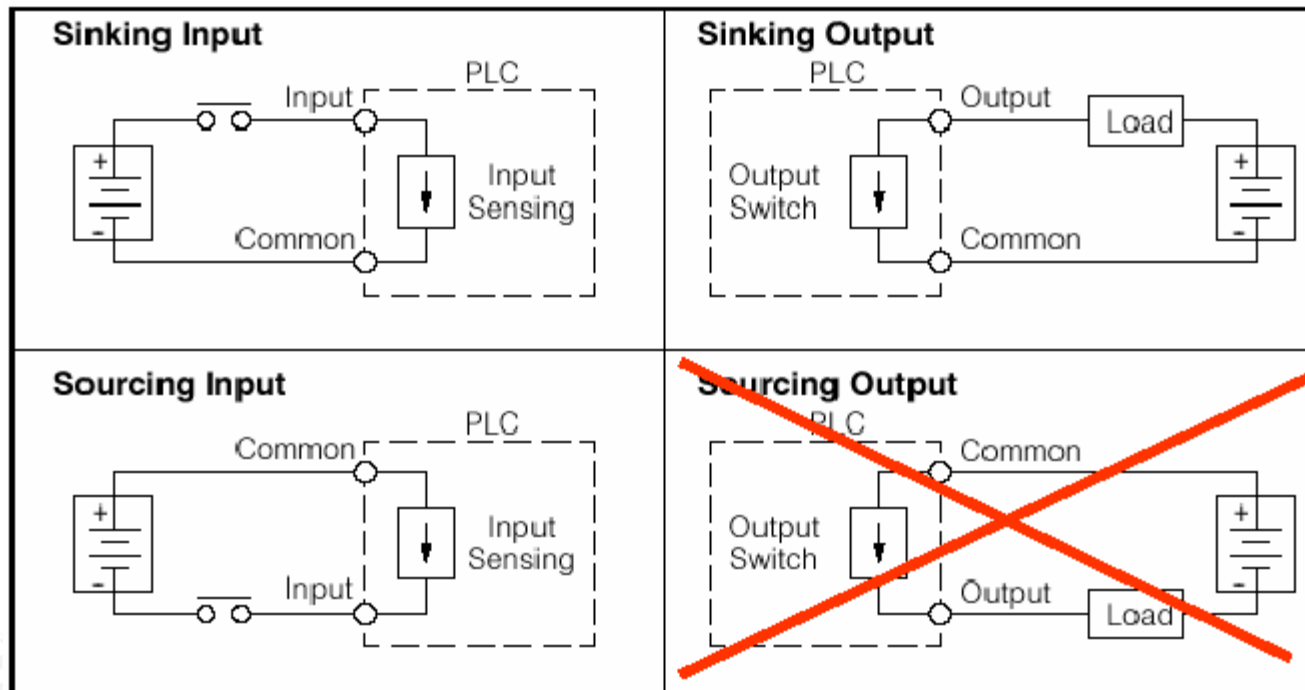


- Sinking = drawing current
- Sourcing = supplying current
- Sinking output connects to sourcing input
- Sourcing output connects to sinking input

# DL06 Signal Inputs

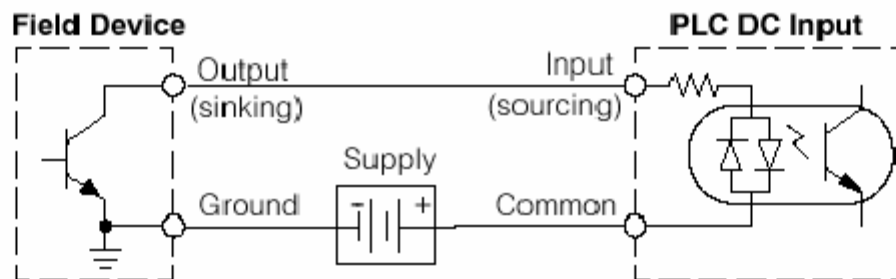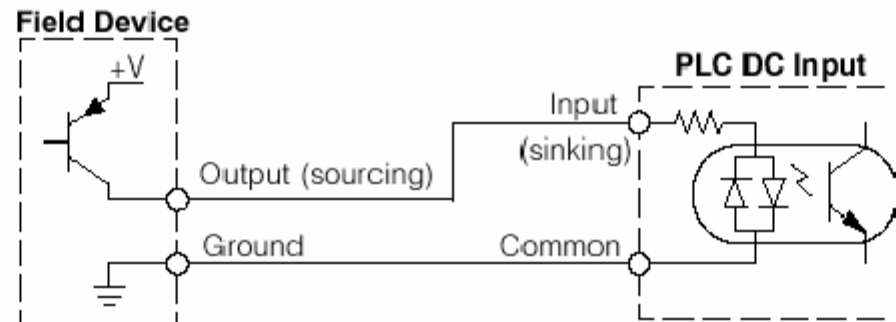

C0	X1	X3	X4	X6	C2	X11	X13	X14	X16	C4	X21	X23	N.C.
X0	X2	C1	X5	X7	X10	X12	C3	X15	X17	X20	X22	N.C.	

# Signal Inputs

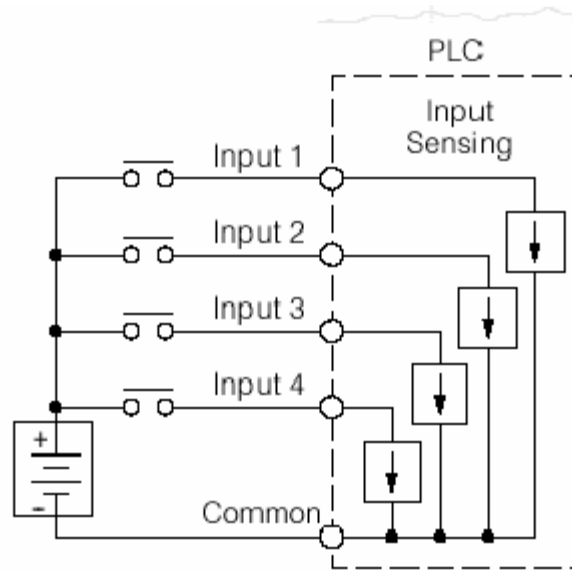


*Multiple sinking inputs*


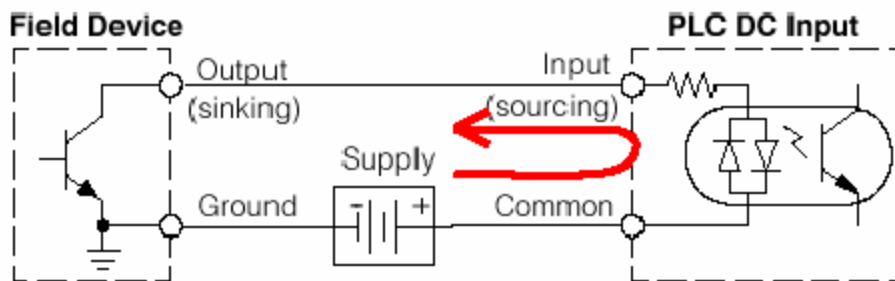
# Typical Input Device


- The tag indicates that the LOAD (PLC input has a +DC common
  - this is a sinking output
  - Sinking output => sourcing input





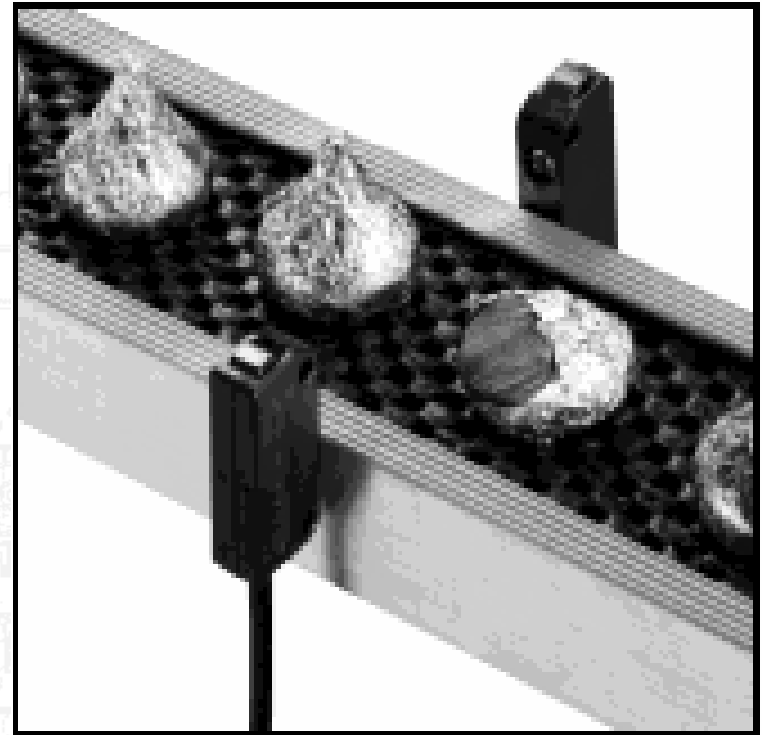
# Another Input Device


- Photosensor – comes in either NPN (sinking) or PNP (sourcing)




**Emitters**  
**Cabled Hookup**

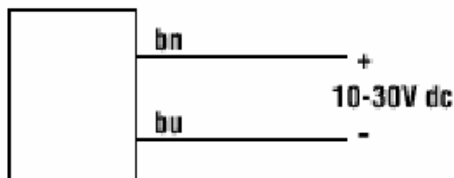


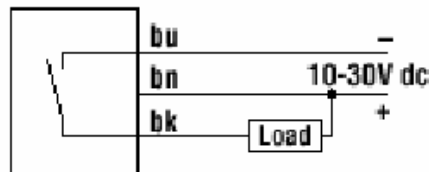
**Receivers with NPN Outputs**  
**Cabled Hookup**



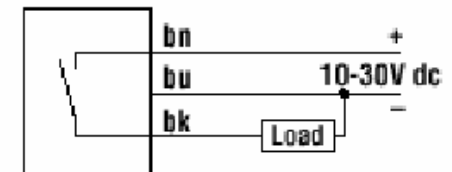**Receivers with PNP Outputs**  
**Cabled Hookup**





# DC Control Outputs

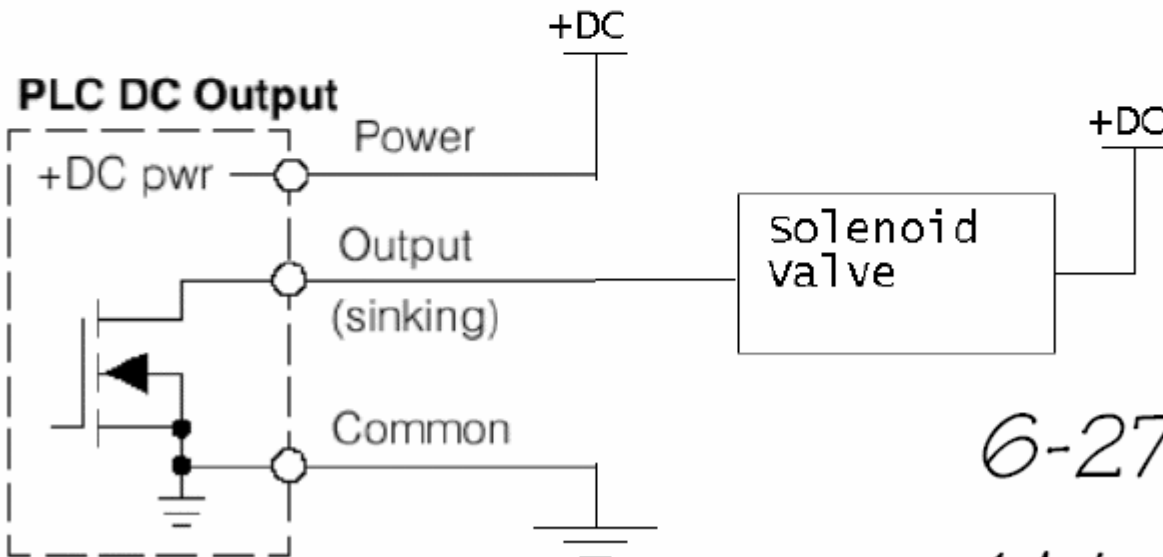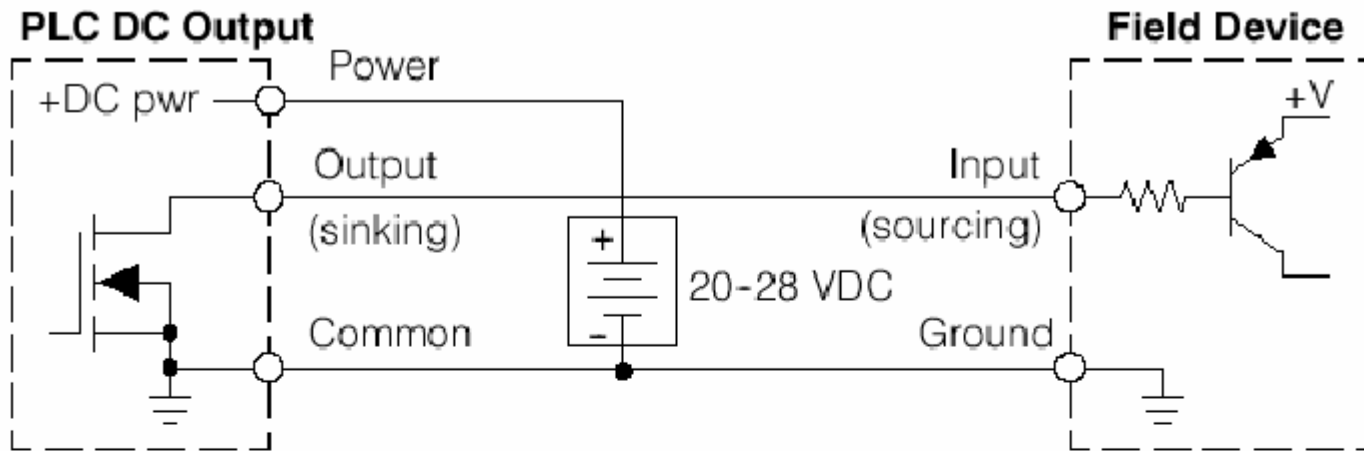

6-27VDC  
1A/output

# DC Control Outputs

0V	Y0	Y2	C1	Y5	Y7	Y10	Y12	C3	Y15	Y17
C0	Y1	Y3	Y4	Y6	C2	Y11	Y13	Y14	Y16	+V

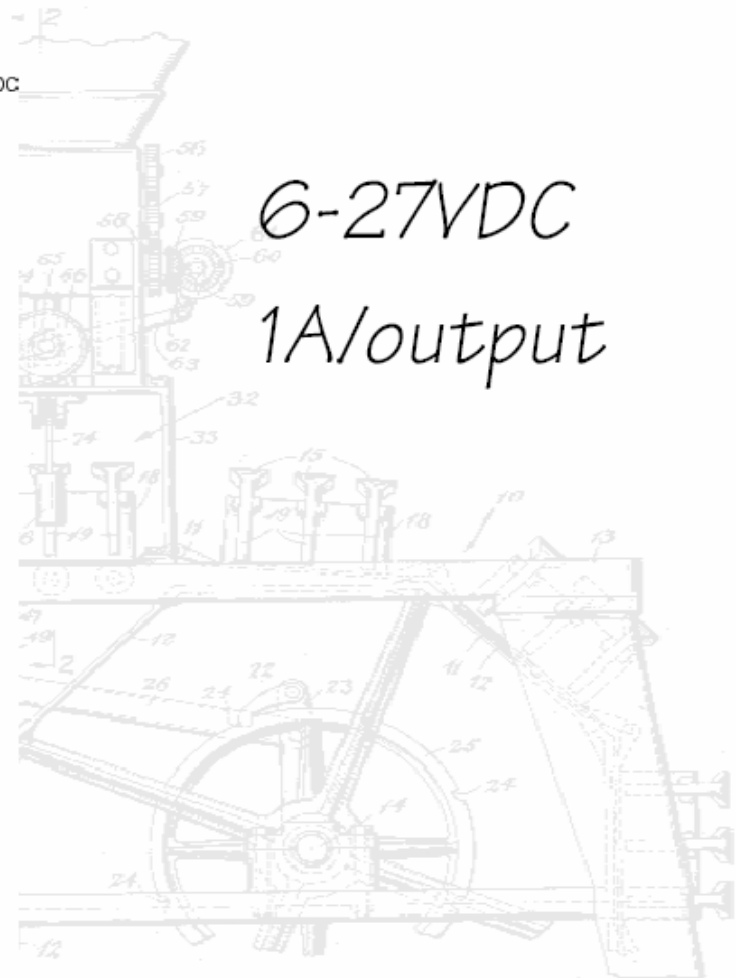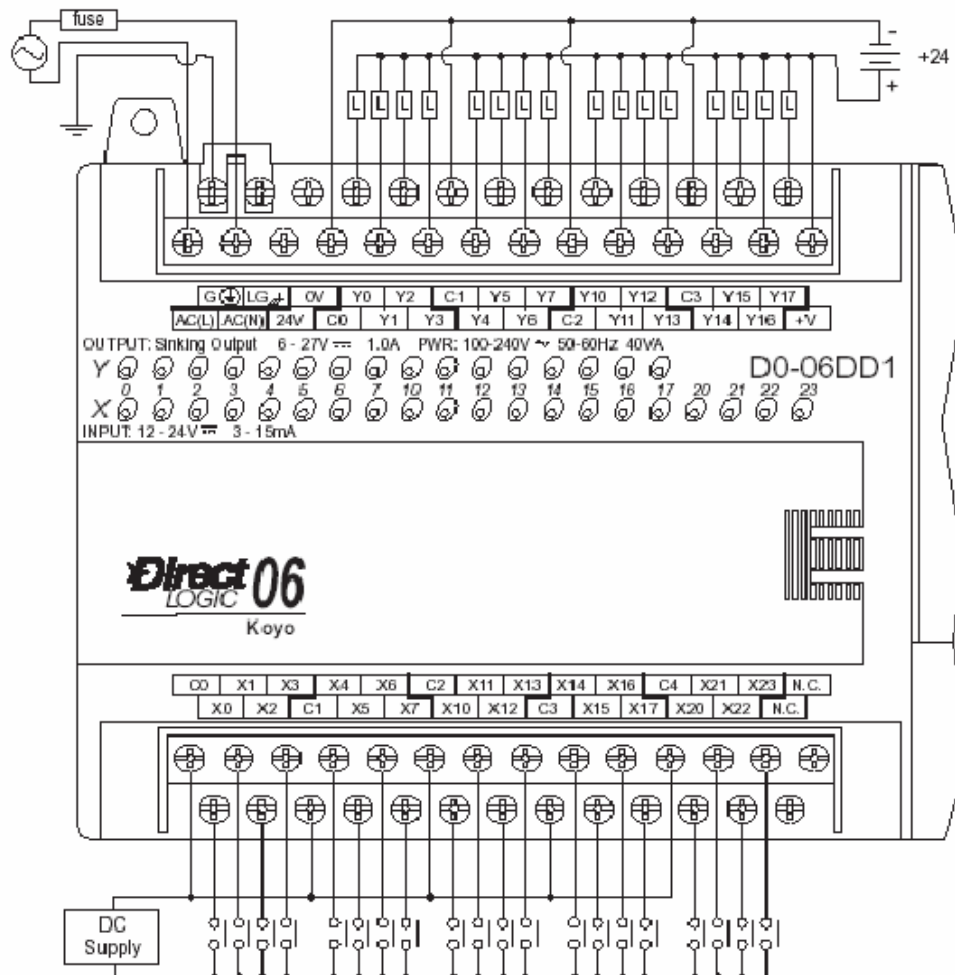

# Wiring Methods

---

