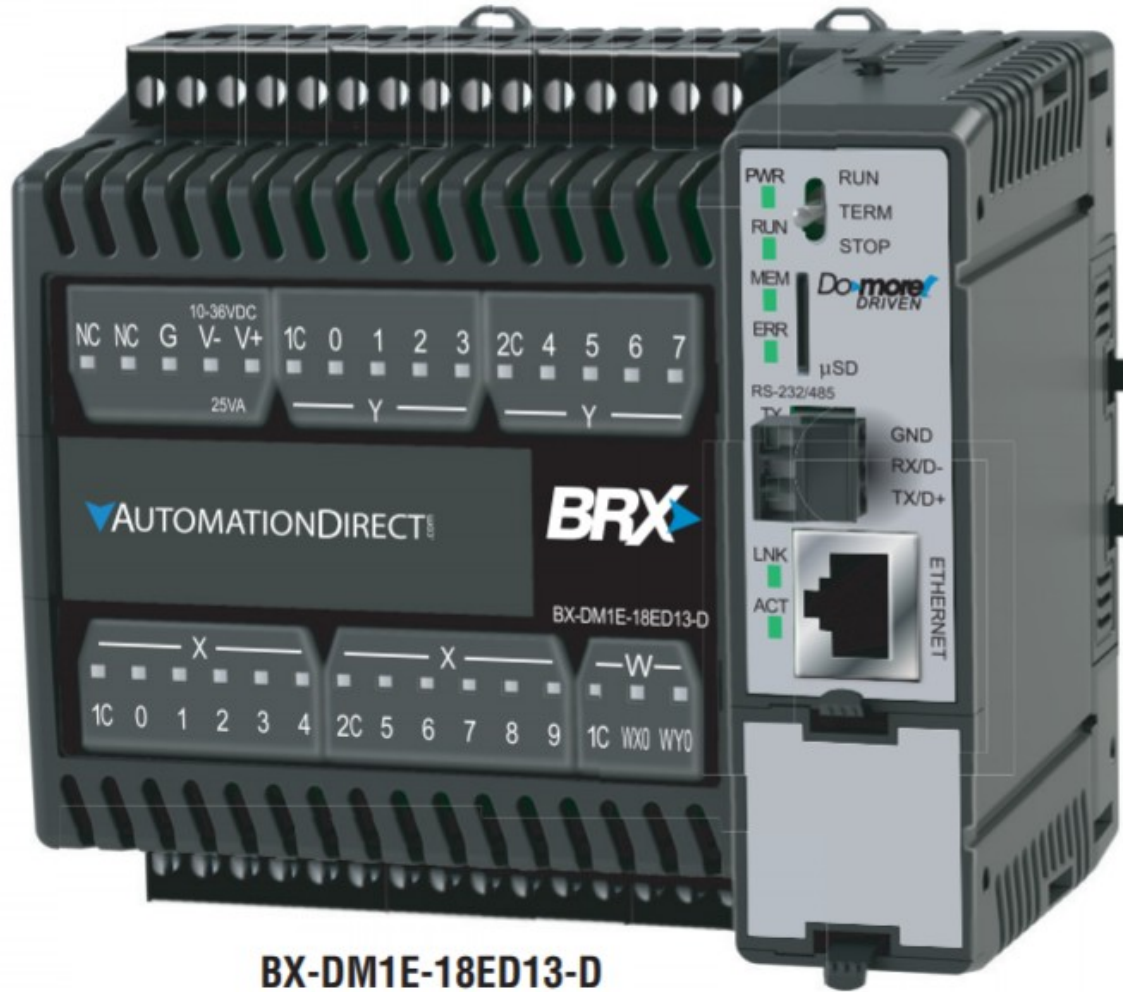


PLC Front Panel




PLC Wiring


- Power Inputs
- Signal Inputs
- Control Outputs




PLC Isolation

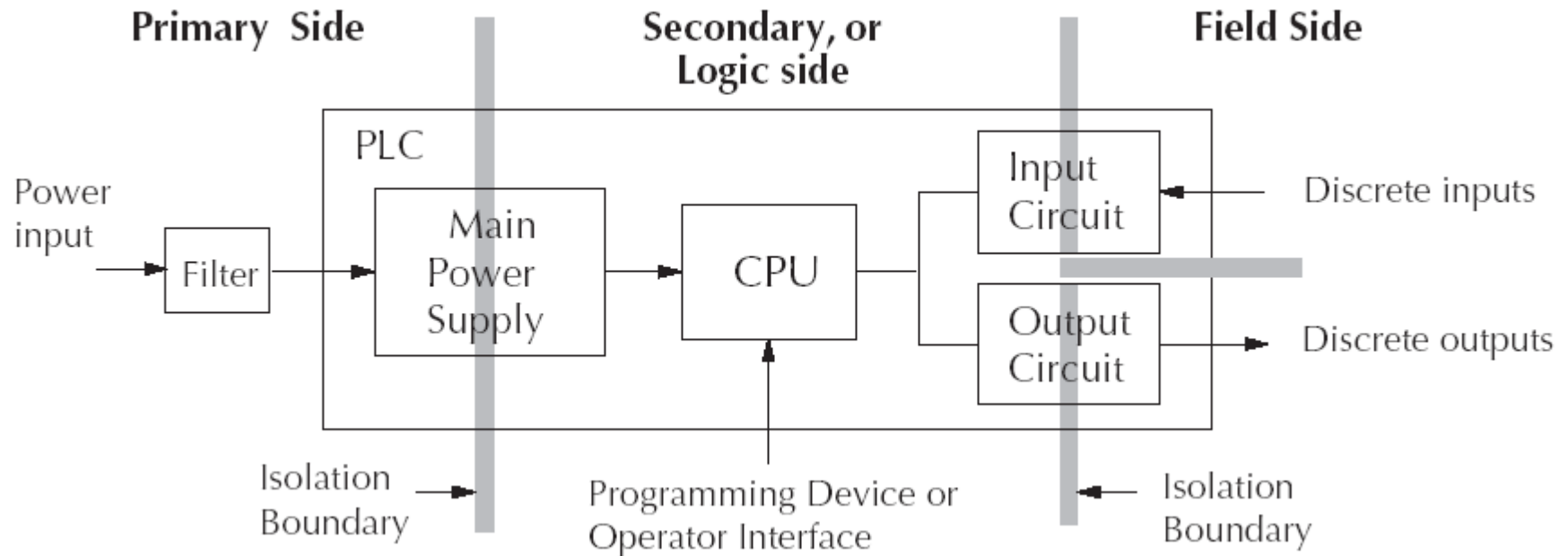


Safety Shutdown

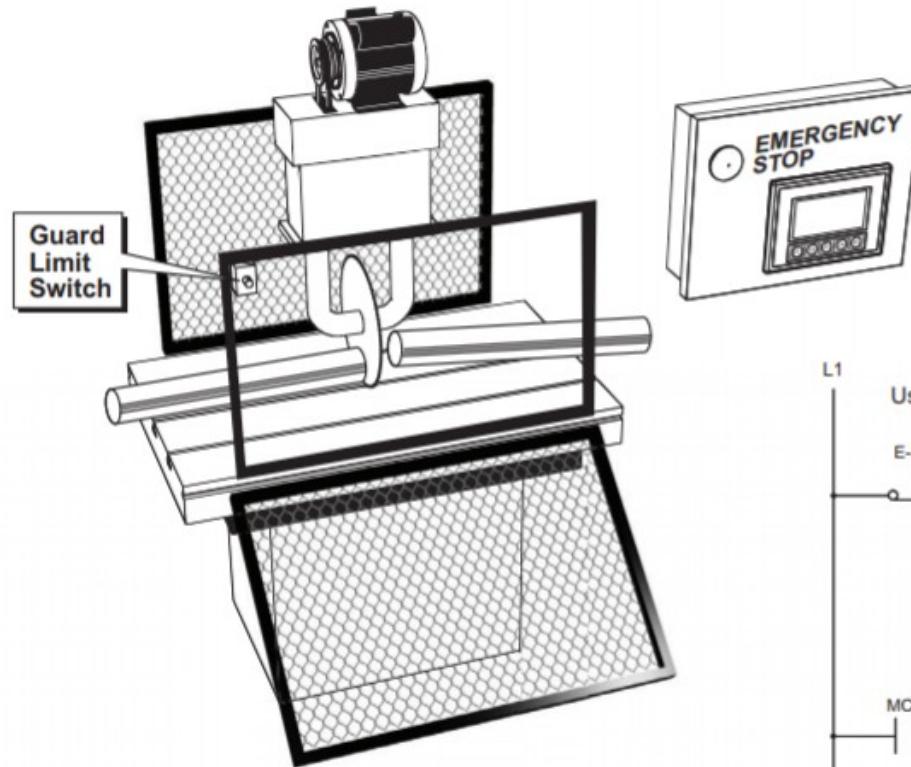

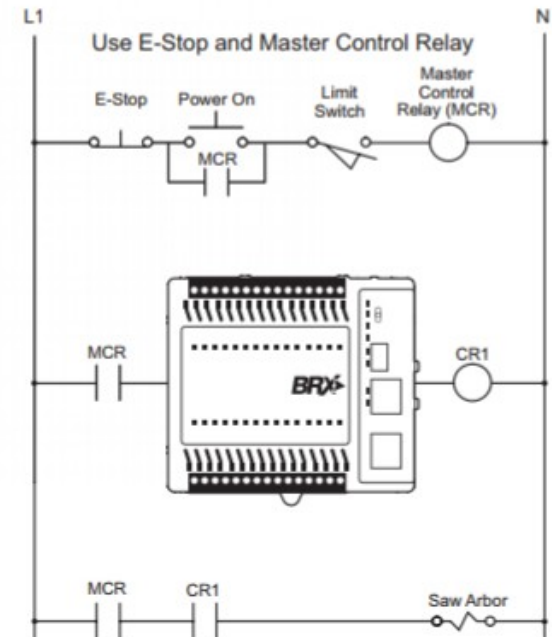
- Three levels of protection:
 - PLC logic - shutdown sequence
 - PLC output power disconnect
 - E-Stop shutdown of all energy sources



Power Wiring



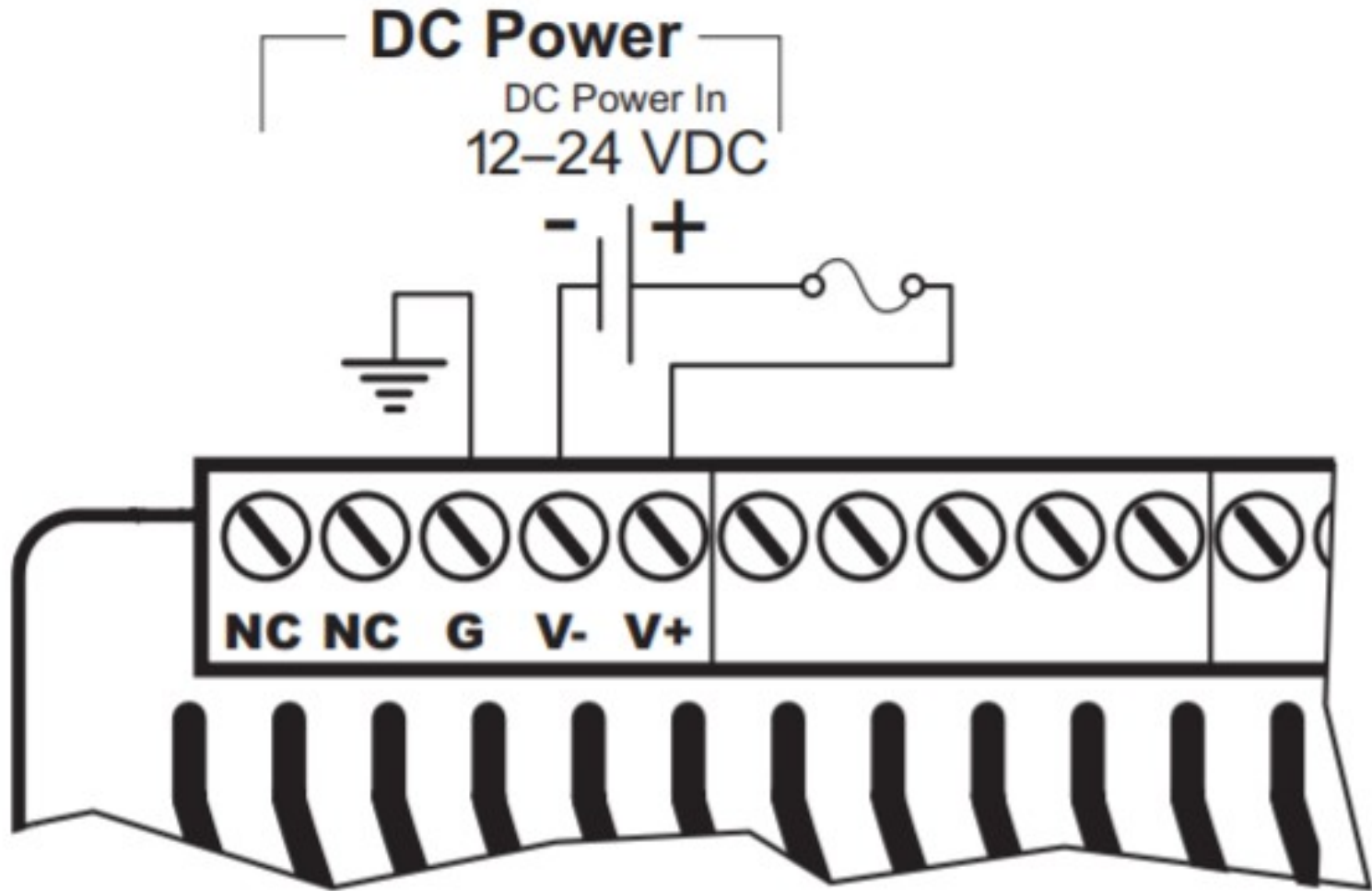


Sinking and Sourcing

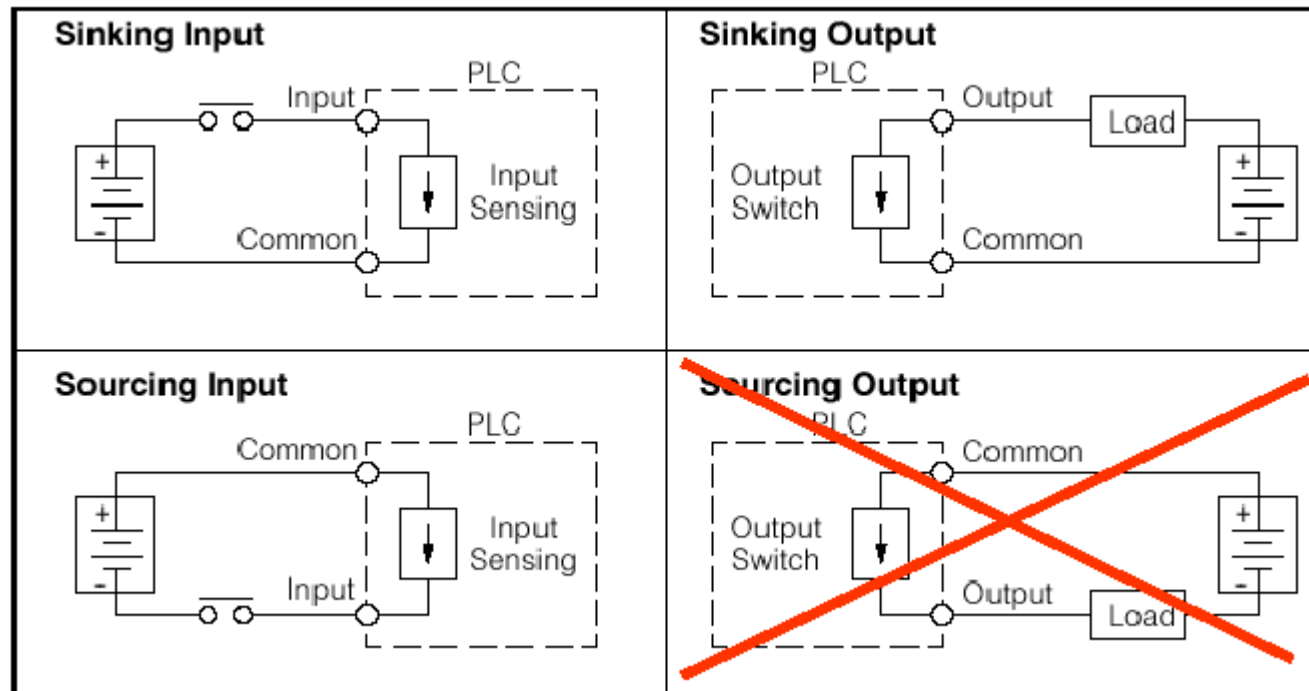


- Sinking = drawing current
- Sourcing = supplying current
- Sinking output connects to sourcing input
- Sourcing output connects to sinking input

PLC Signal Inputs

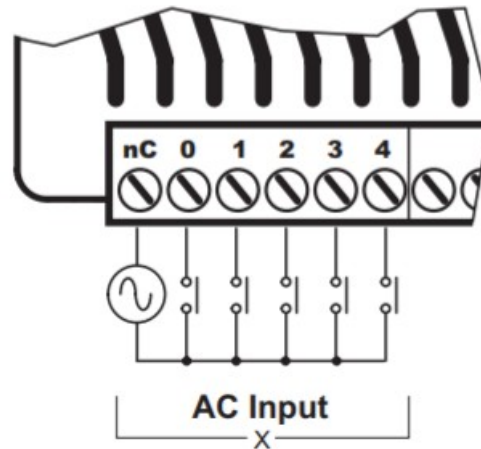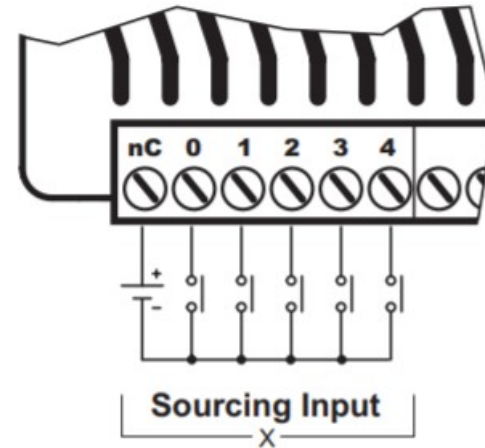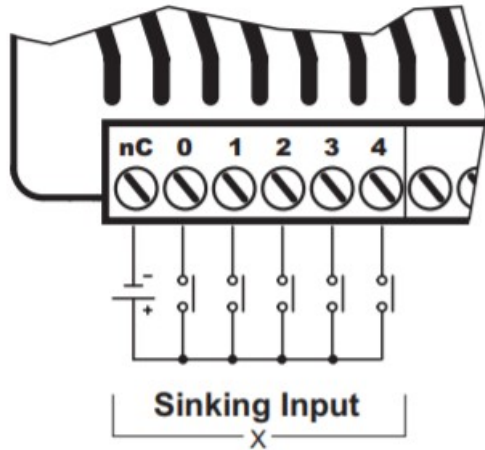


Signal Inputs

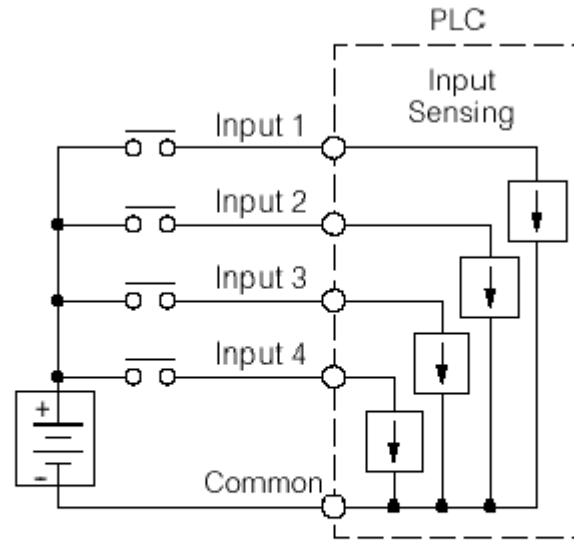



Multiple sinking inputs

Typical Input Device

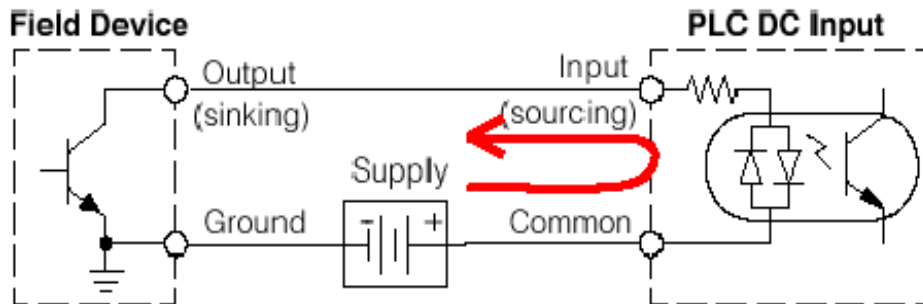- The tag indicates that the LOAD (PLC input) has a +DC common
 - this is a sinking output
 - Sinking output => sourcing input



DC Control Outputs

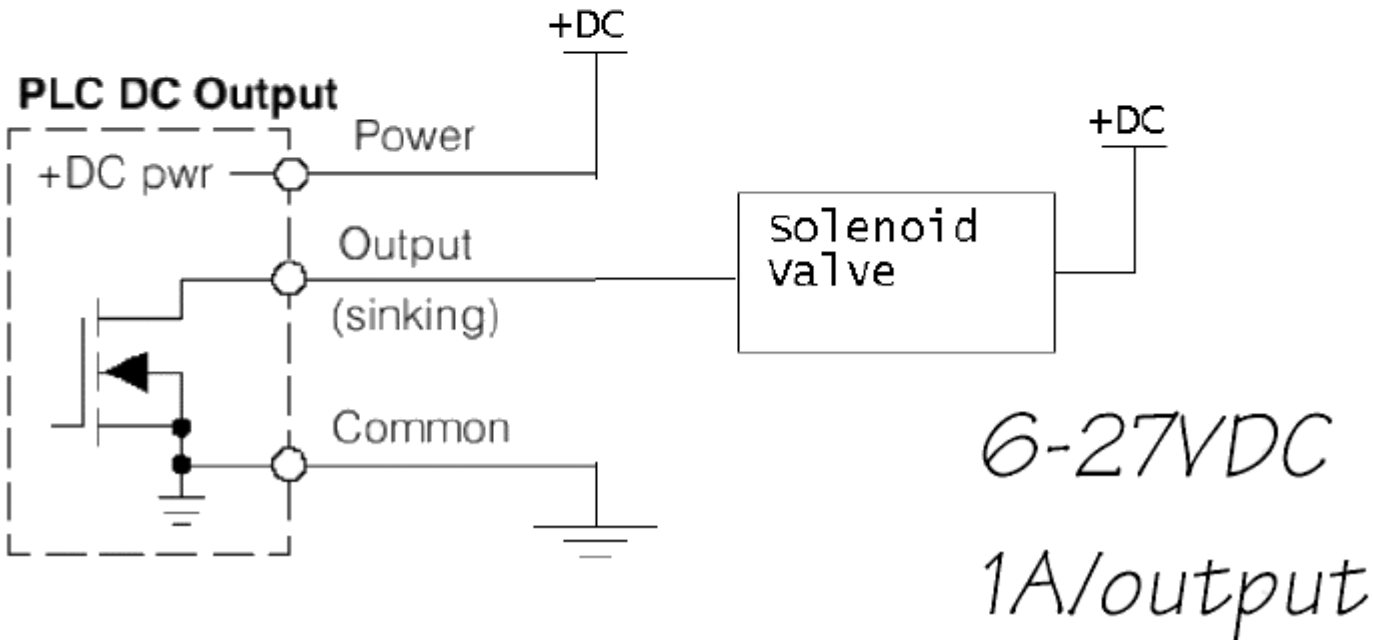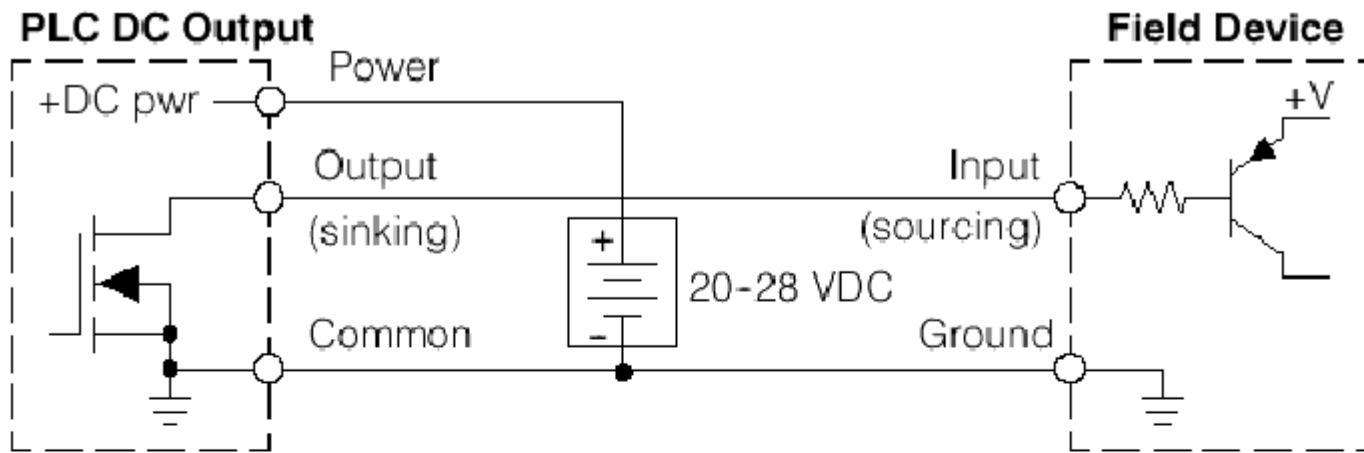

DC Control Outputs

