
ENGR480 In-Class Exercise 2026-11-06

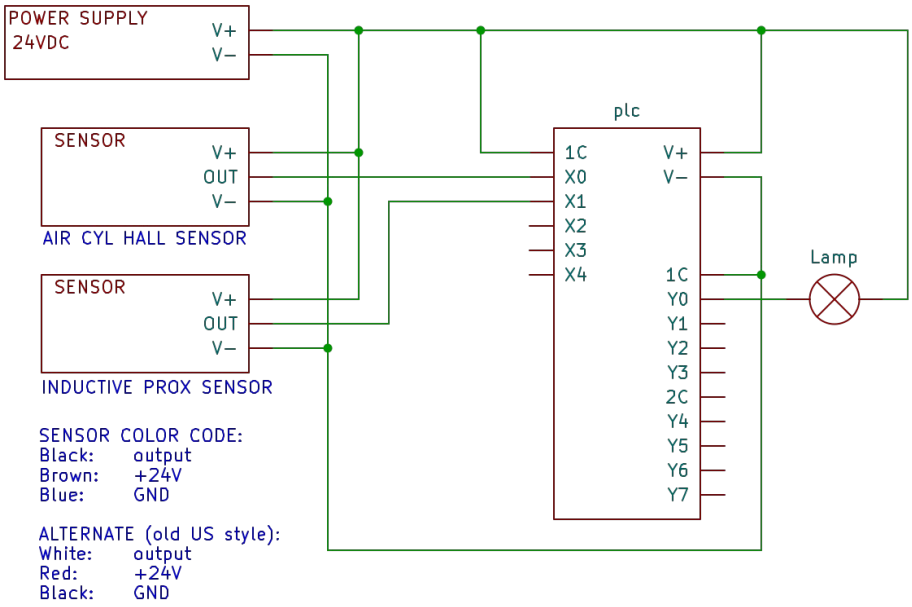You will be wiring an air cylinder Hall sensor, an inductive proximity sensor, and a normally-open (green) momentary pushbutton switch to the PLC, using the terminal blocks for tidiness.



The ladder logic in your PLC is this:

