Example – Light Switch

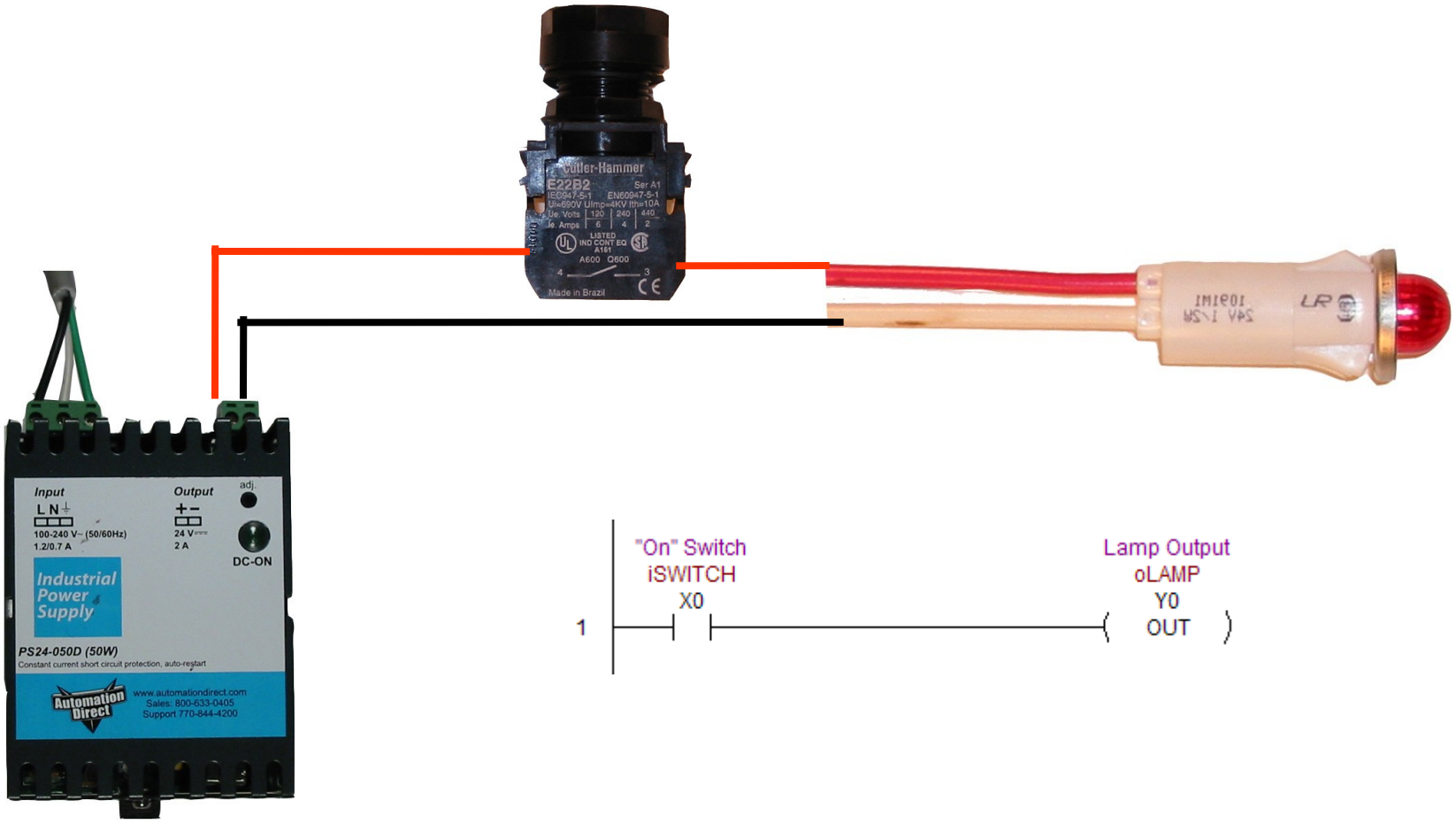

Example – Light Relay

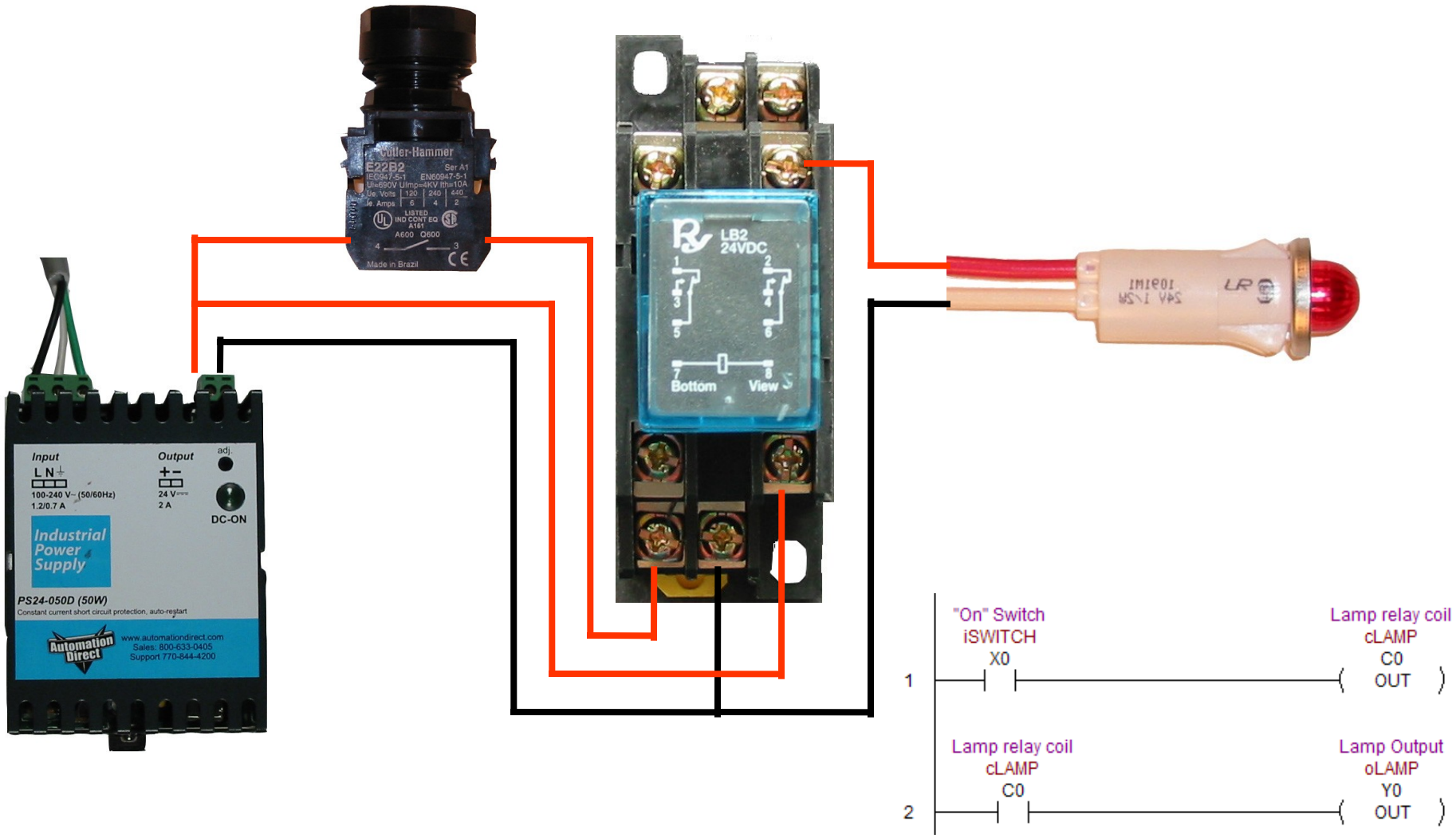
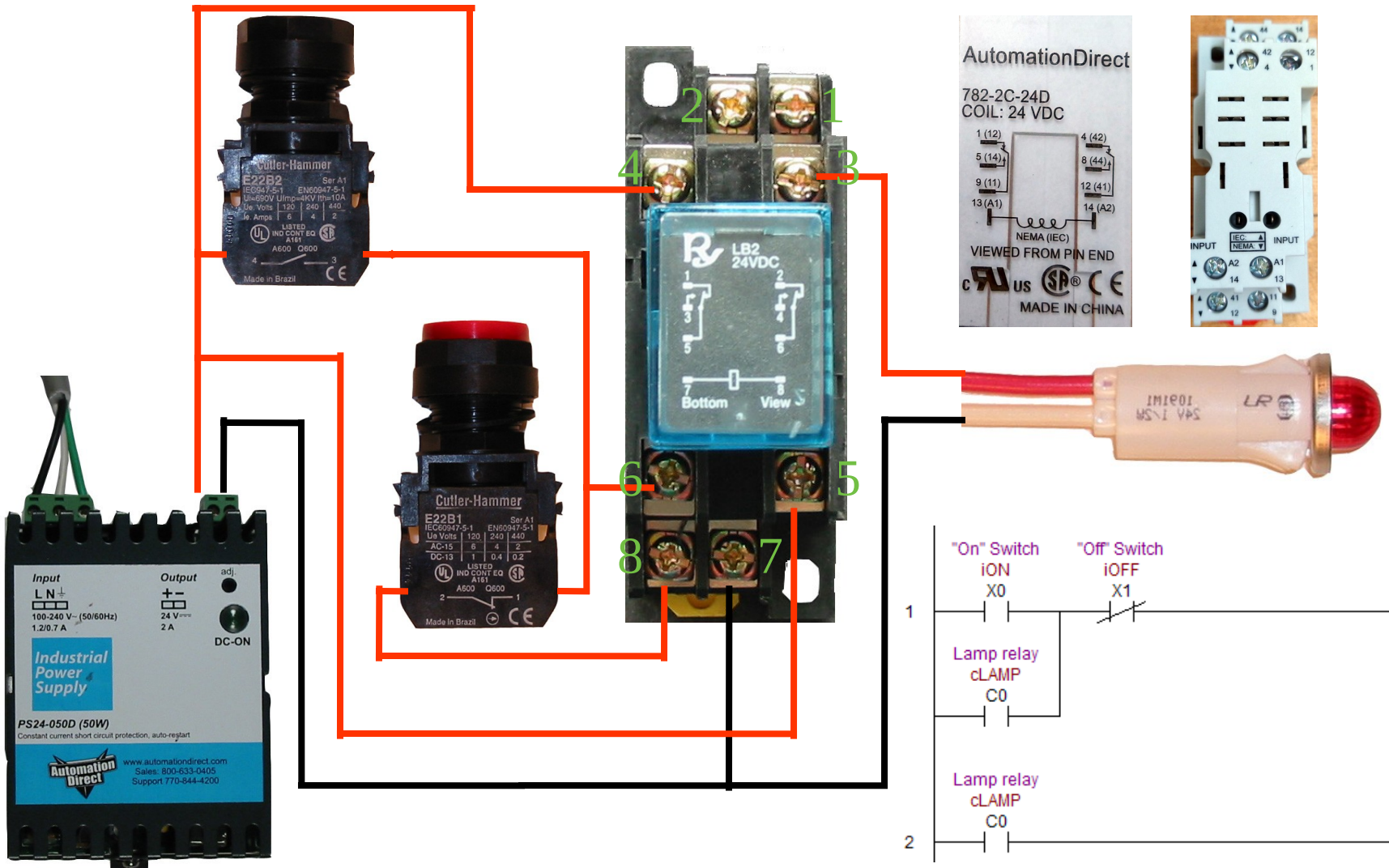
Example – Latching Relay Logic